



CSE251: Electronic Devices and Circuits


Lecture 3
Operational Amplifier I

Prepared By:
Shadman Shahid (SHD)

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: shadman9085@gmail.com




The Circuit Abstraction

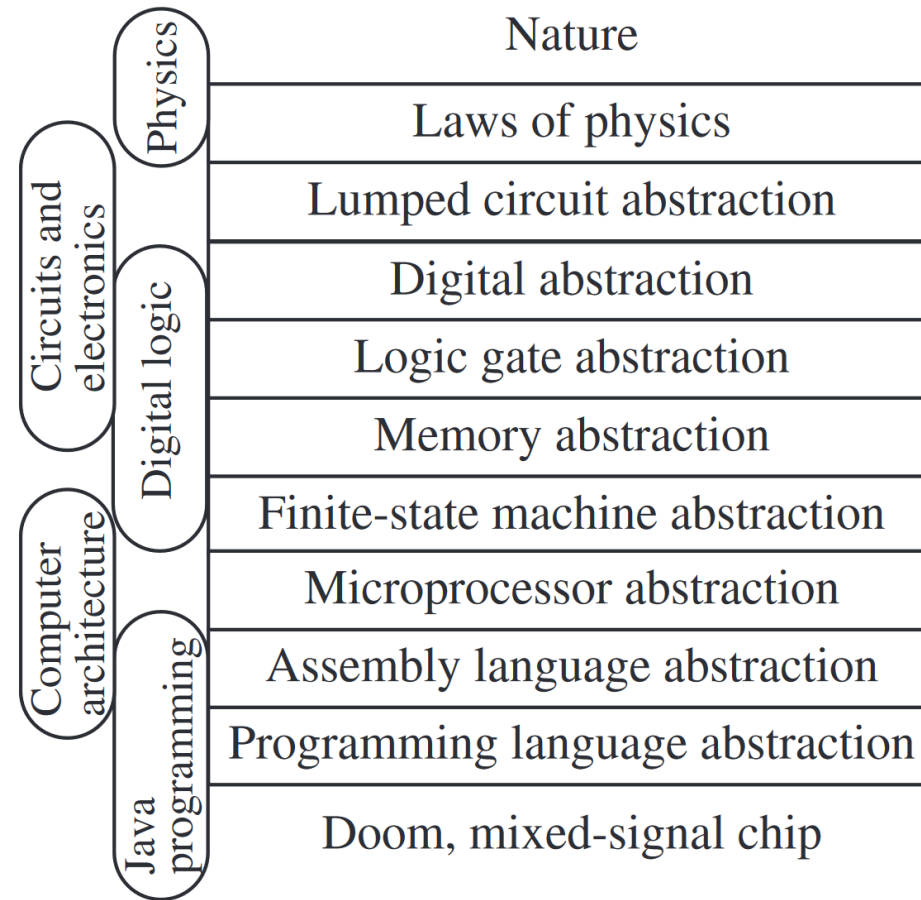

Sequence of courses and the abstraction layers

Operational Amplifiers

Textbook

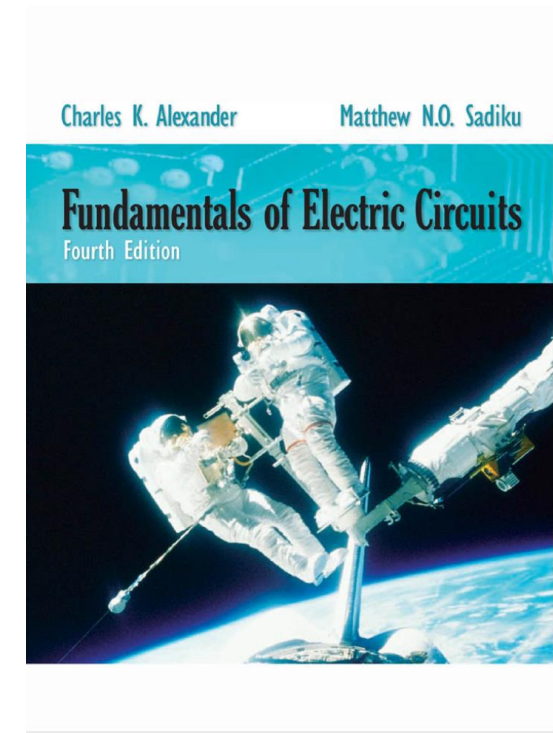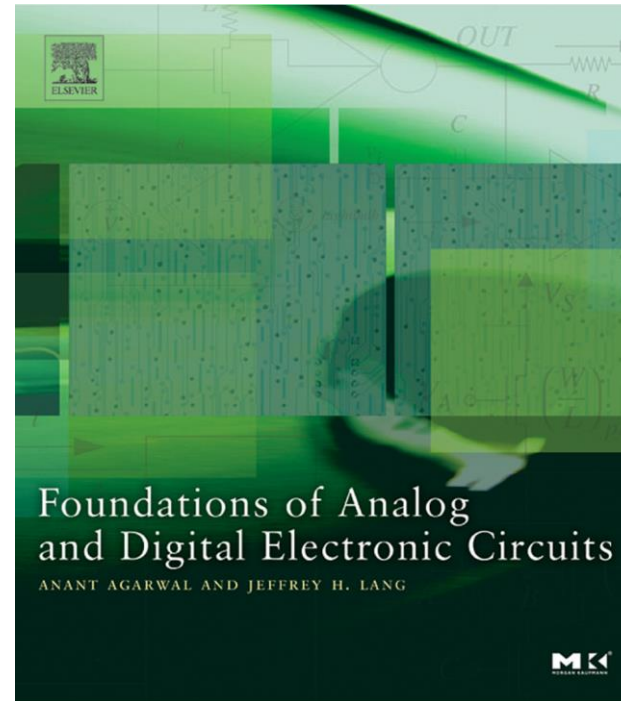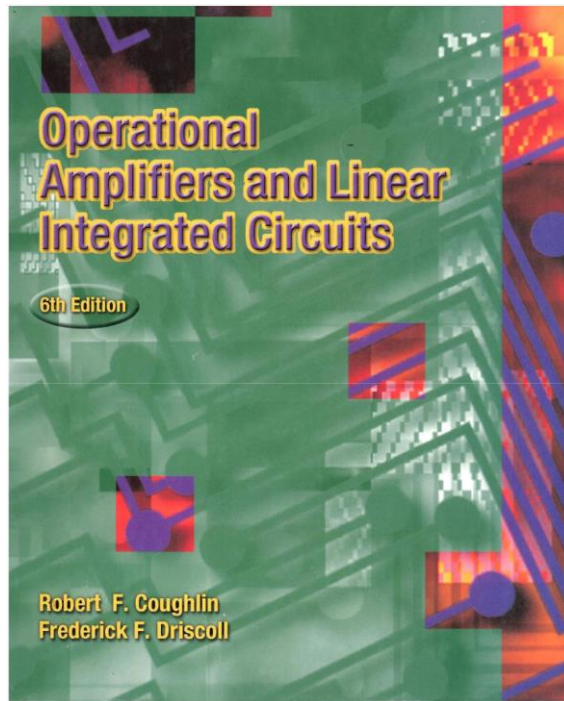

Operational Amplifier

- **Operational:**


Mathematical Operations

- **Amplifier:**

Amplifies input signal/voltage.

Voltage Transfer Characteristics (VTC)

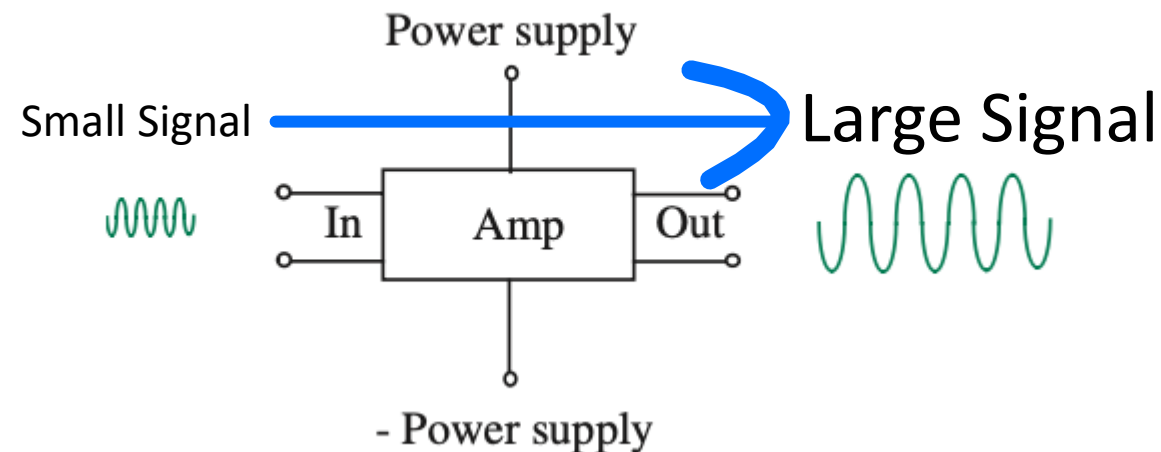Shows how the **output voltage** varies with the **input voltage** $V_{Out}(V_{In})$




Operational Amplifier: Amplification

Voltage Transfer Characteristics (VTC)

Shows how the **output voltage** varies with the **input voltage** $V_{\text{Out}}(V_{\text{In}})$

$V_{\text{In}}(\text{V})$	$V_{\text{Out}}(\text{V})$
0.5	5
1.0	10
1.5	15
2.5	25
3.5	35

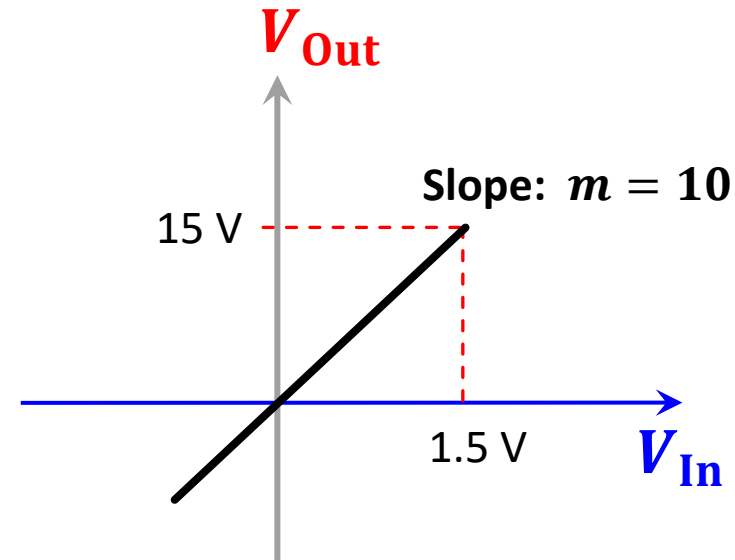


Amplification: VTC

Voltage Transfer Characteristics (VTC)

- Shows how the **output voltage** varies with the **input voltage** $V_{Out}(V_{In})$
- y —axis $\rightarrow V_{Out}$
- x —axis $\rightarrow V_{In}$

- Slope: $m = \frac{\Delta V_{Out}}{\Delta V_{In}} = \frac{V_{Out}}{V_{In}}$


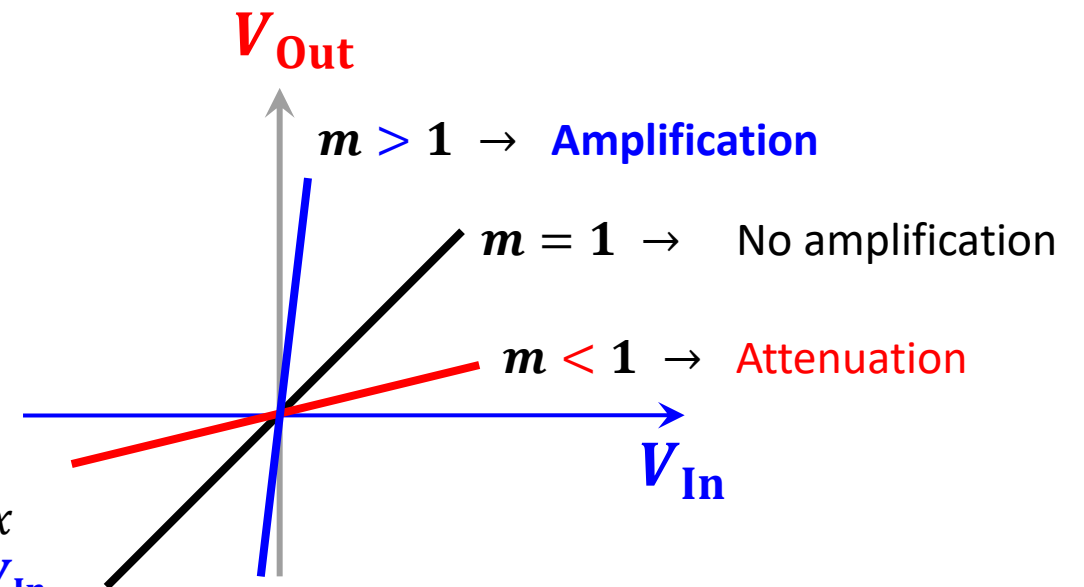
Since the line passes through origin: $y = m \cdot x$
 $V_{Out} = m \cdot V_{In}$



LINEAR RELATION (AMPLIFICATION)

Amplification: VTC

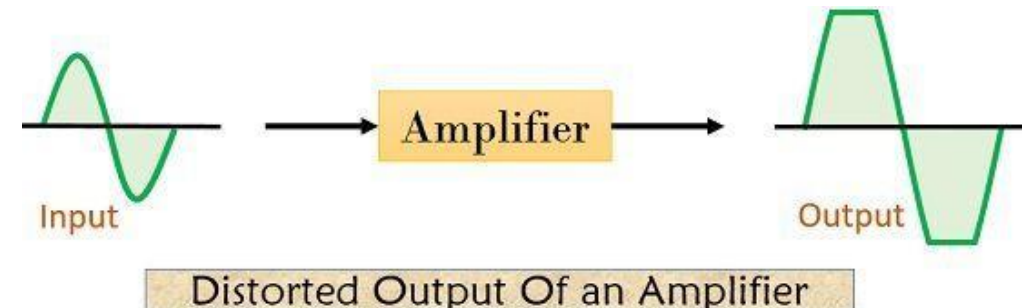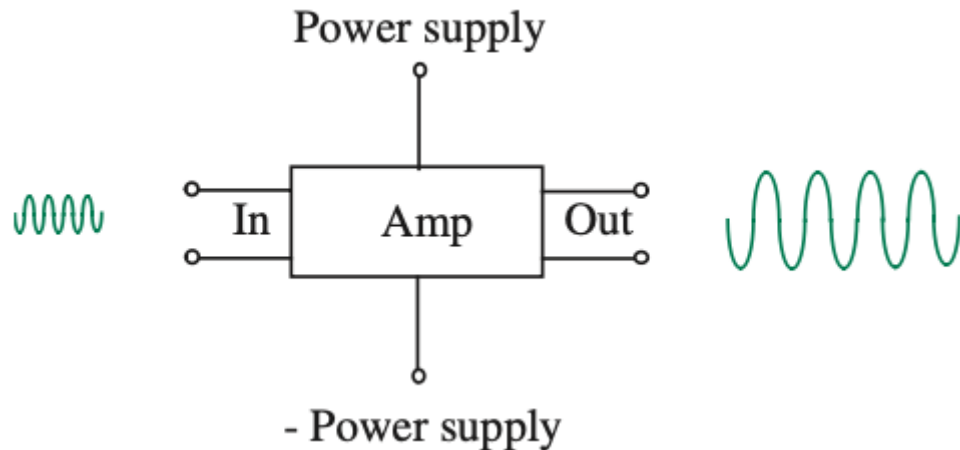- **Linear Amplification** only takes place within a [valid input range](#).
- Otherwise output will be distorted - - Saturation



The limiting factor of **linear amplification** is determined by the **power supply** to the amplifier

Amplification: VTC - Saturation


$$V_{\text{Out}} = m \cdot V_{\text{In}} : \text{When } -50\mu < V_{\text{In}} < 50\mu$$

$m \rightarrow 10^5$: Gain / Amplification

Non-Linear characteristics

If $V_{\text{In}} < -50\mu$: Negative Saturation



$$\Rightarrow V_o = -5$$

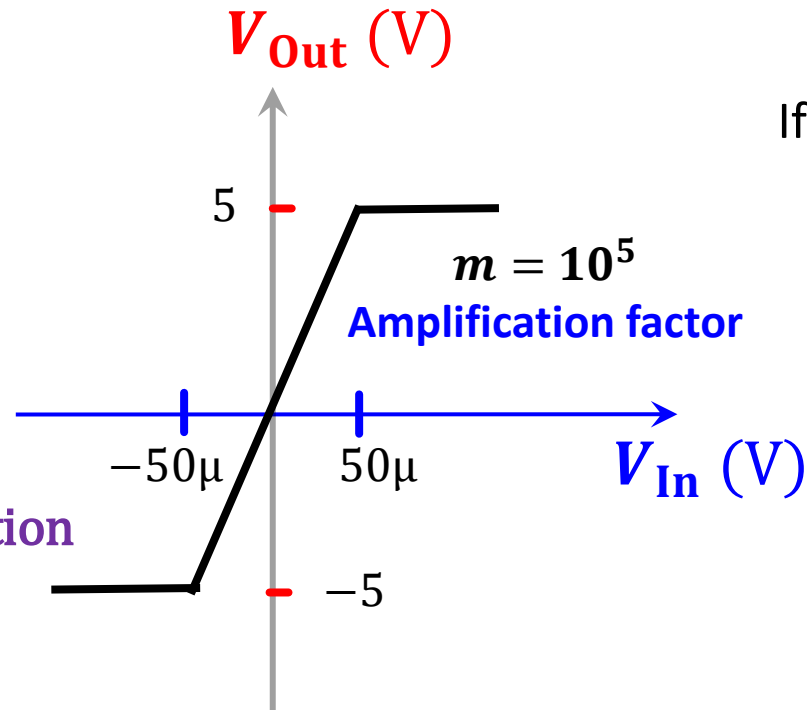


If $V_{\text{In}} > 50\mu$: Positive Saturation

$$\Rightarrow V_o = 5$$

Amplification: VTC

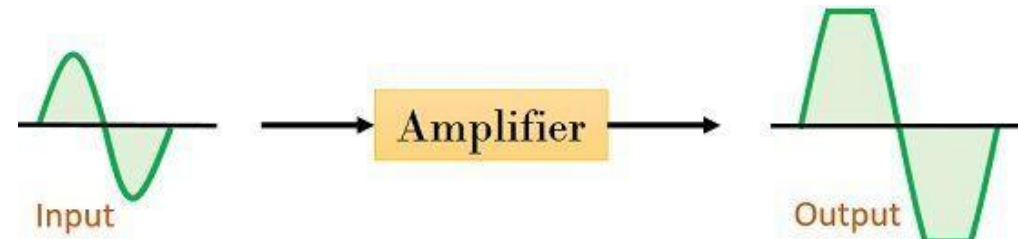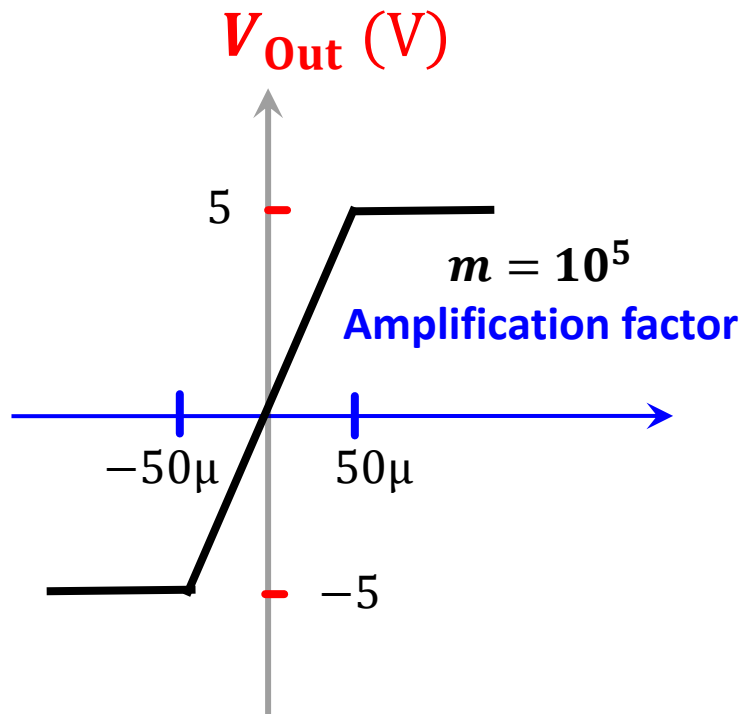


Distorted Output Of an Amplifier

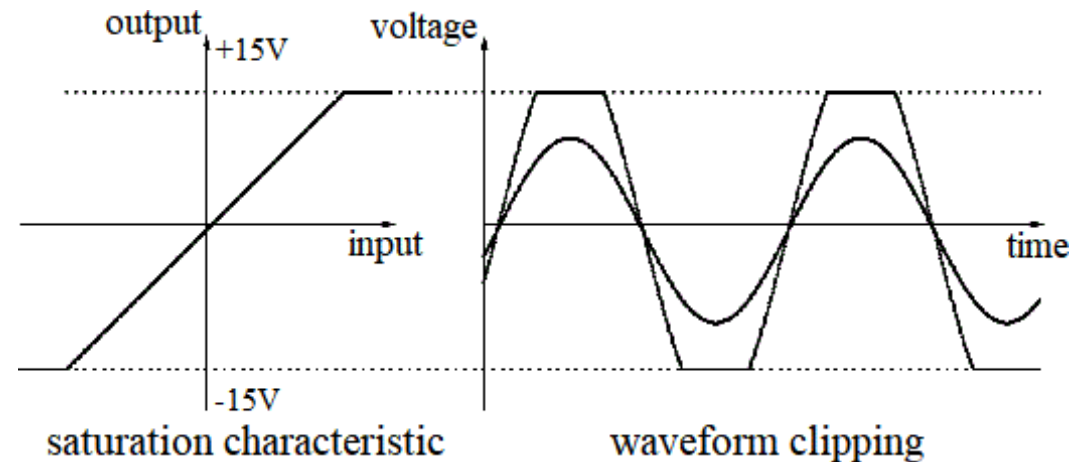


Operational Amplifier

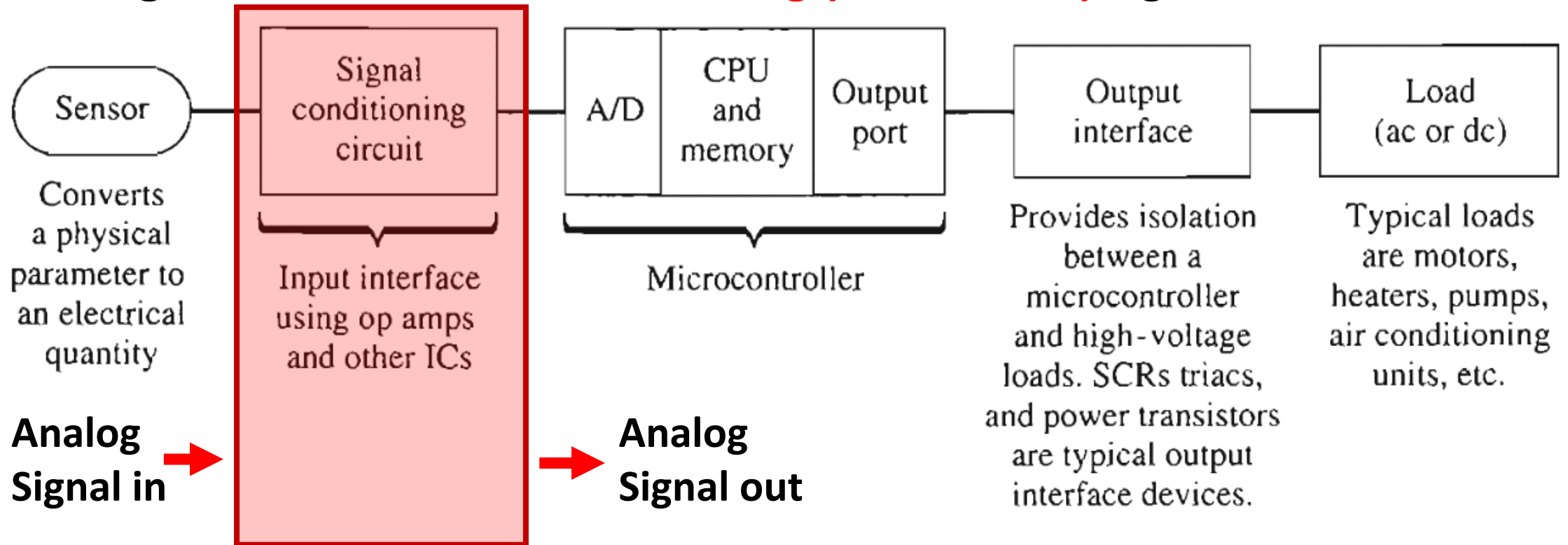Analog Electronics: Deals with **analog (continuous)** signals.



- The word operational in operational-amplifier originally stood for mathematical operations

Circuit Symbols and terminal

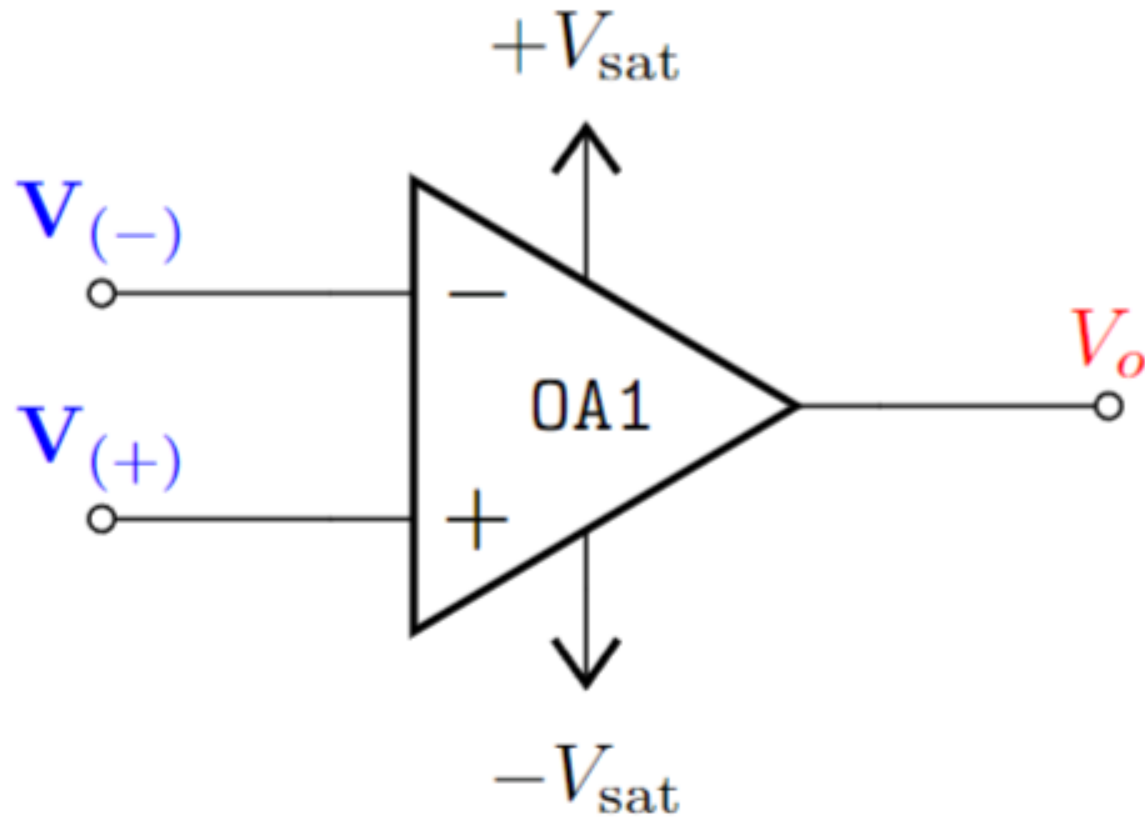

Circuit Symbols and Terminals

Difference Amplifier – Amplifies the voltage difference between two terminals.

$V_{(+)}$ Non-inverting terminal voltage

$V_{(-)}$ Inverting terminal voltage


V_d Differential input voltage

$+V_{\text{sat}}$ Positive Saturation Voltage


$-V_{\text{sat}}$ Negative Saturation Voltage

V_o Output Voltage

$$V_d = V_{(+)} - V_{(-)}$$

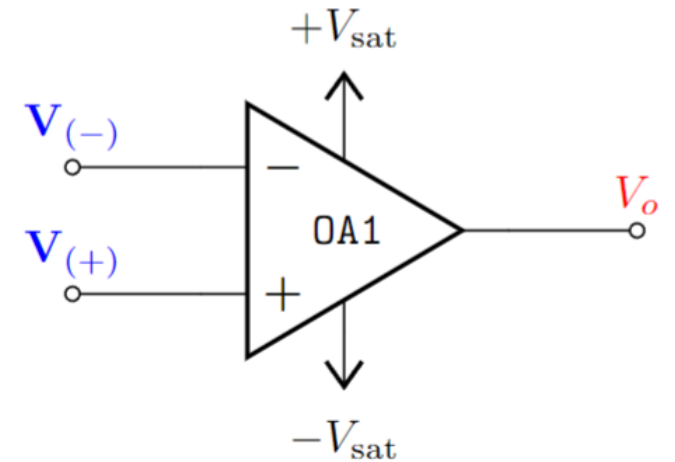


Voltage Transfer Characteristics (VTC)

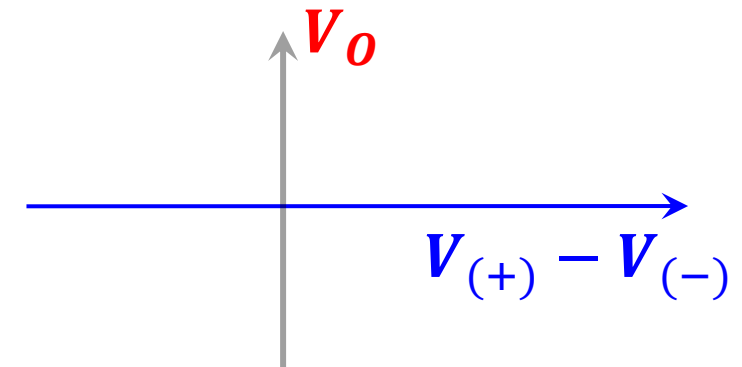


Circuit Symbols and Terminals

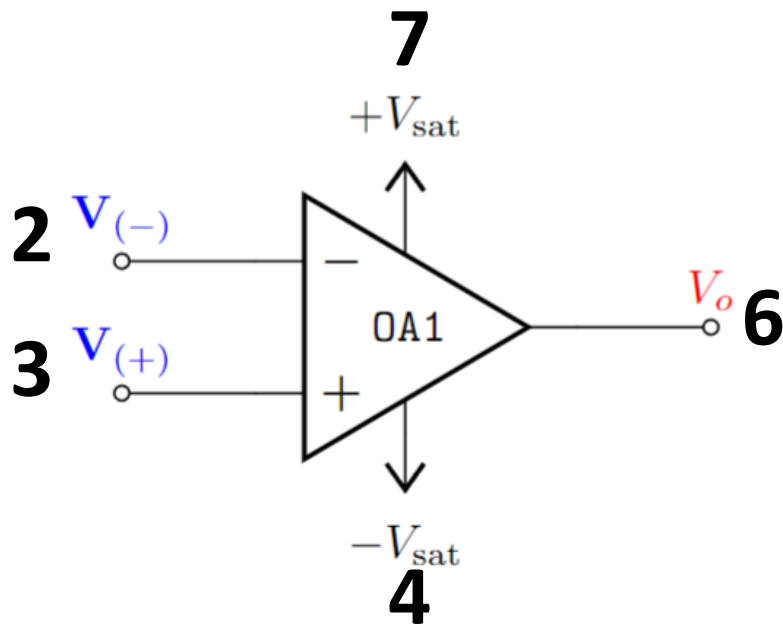
Difference Amplifier – Amplifies the voltage difference between two terminals.



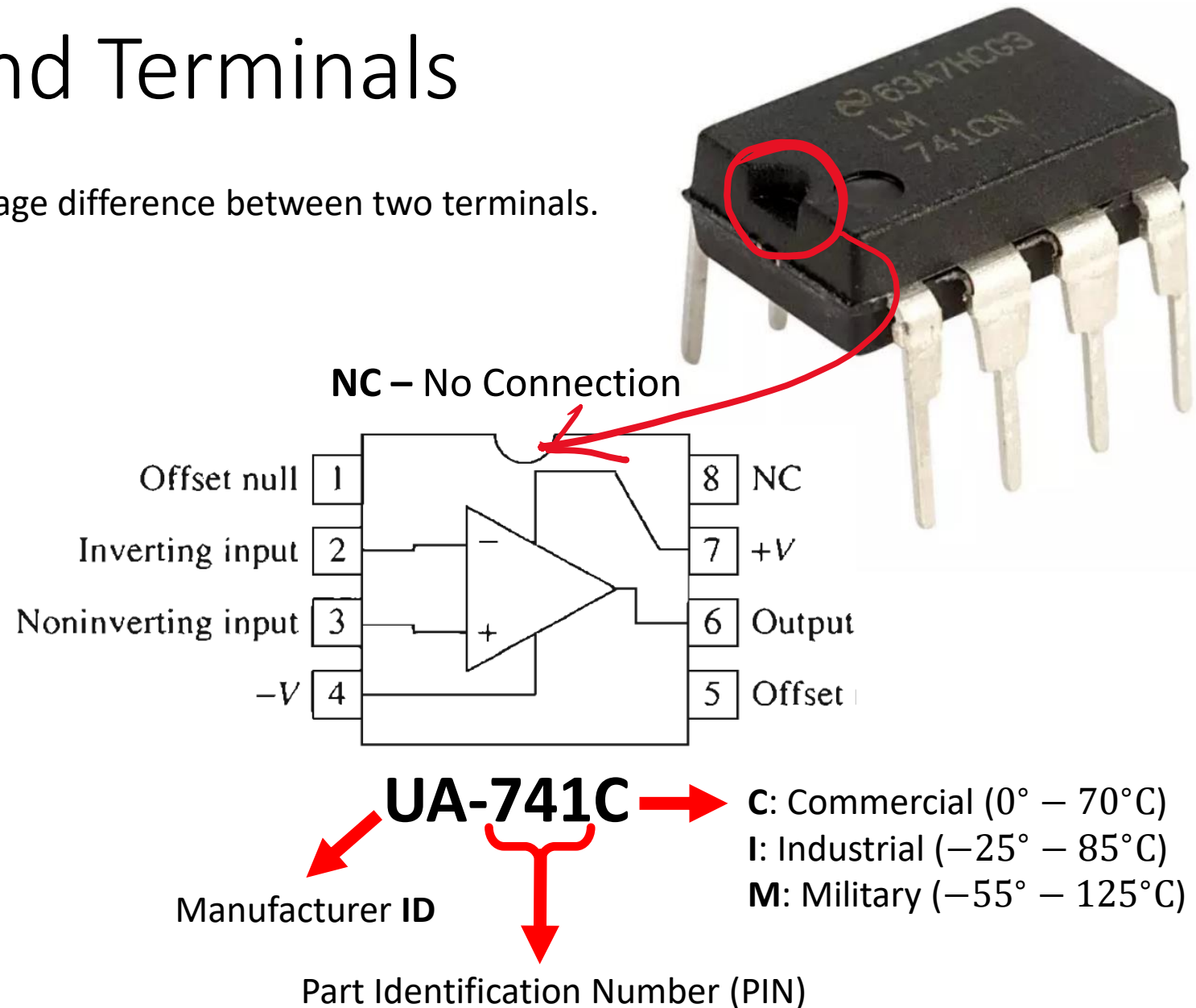Circuit symbol for the general-purpose op amp. Pin numbering is that for an **8-pin mini-DIP package**



Circuit Symbols and Terminals

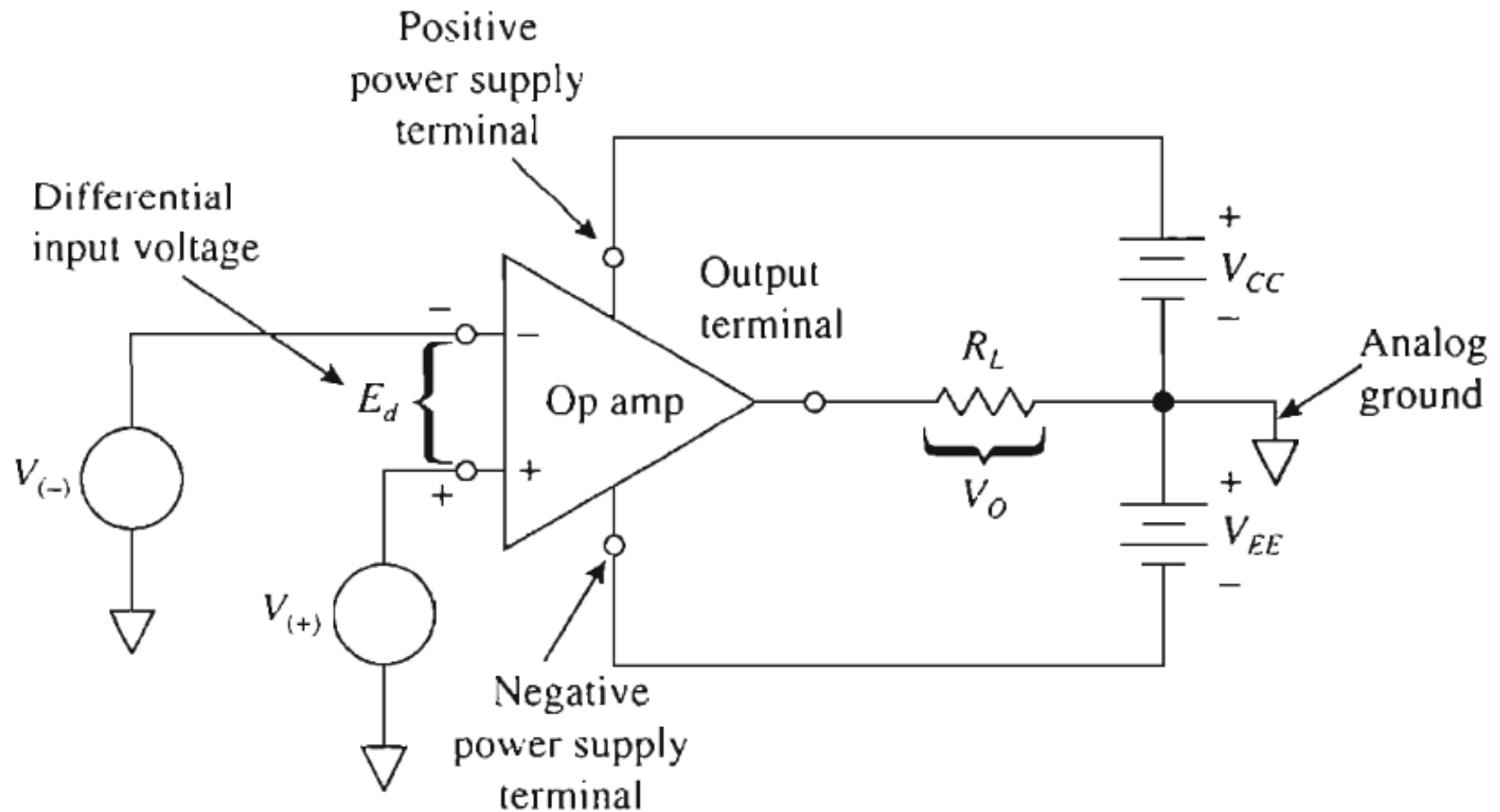

Op-Amp VTC: Modes of operation

Voltage Transfer Characteristics (VTC)

Positive saturation:

If $V_d > \frac{+V_{\text{sat}}}{A}$: **Positive**

$$\Rightarrow V_o = +V_{\text{sat}}$$


Linear Region

$V_o = AV_d$: When V_d is very small
 $-V_{\text{sat}} < V_o = AV_d < +V_{\text{sat}}$

Negative saturation:


If $V_d < \frac{-V_{\text{sat}}}{A}$: **Negative**

$$\Rightarrow V_o = -V_{\text{sat}}$$

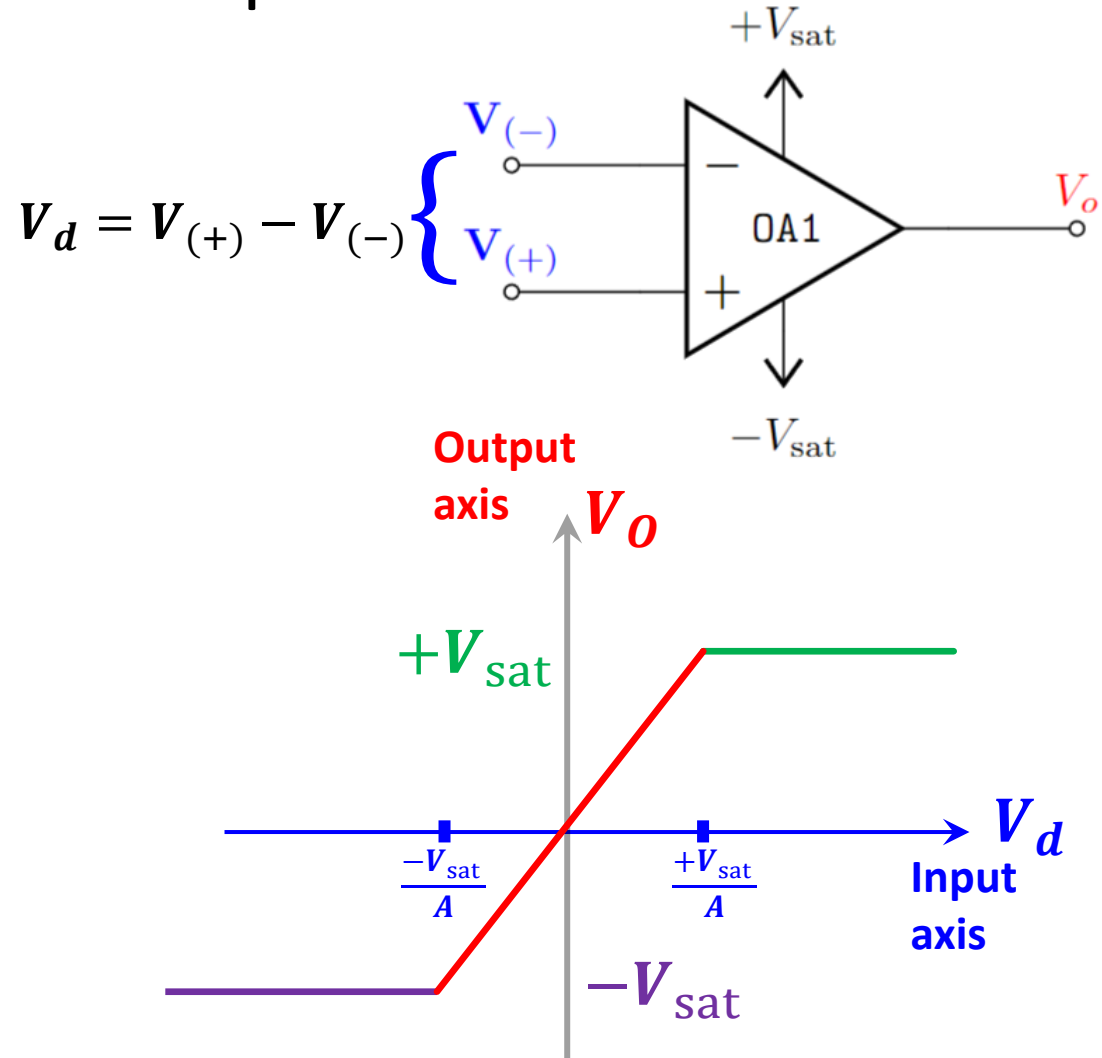


Some op-amp circuits

Find v_o

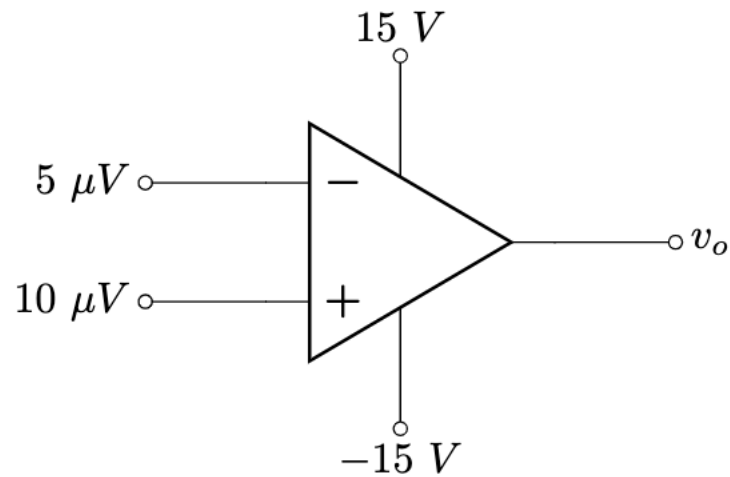


$$A = 2 \times 10^5$$

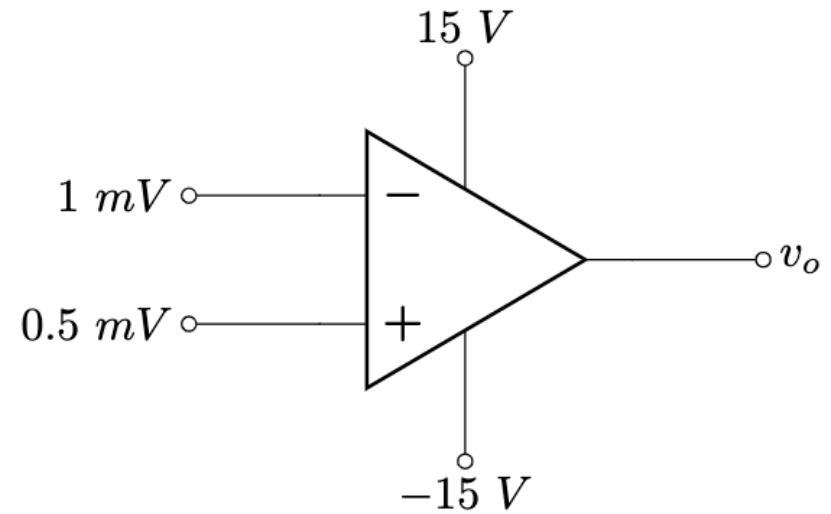

$$A = 2 \times 10^5$$

Example 1

- Find v_o

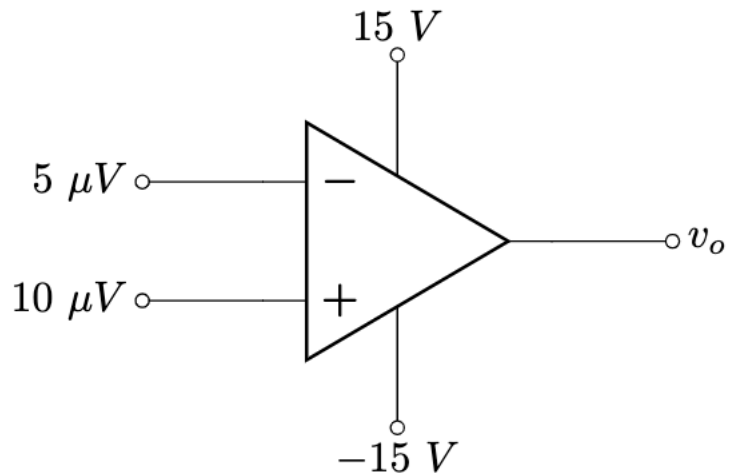

$$A = 2 \times 10^5$$

Solution:

$$V_d = V_{(+)} - V_{(-)} = (10 - 5)\ \mu\text{V} = 5\ \mu\text{V}$$


$$AV_d = (2 \times 10^5) \times (5 \times 10^{-6})\ \text{V} = 1\ \text{V}$$

$$\text{Since } -15\ \text{V} < AV_d < +15\ \text{V}$$

$$V_o = AV_d = 1\ \text{V}$$

Example 2

- Find v_o

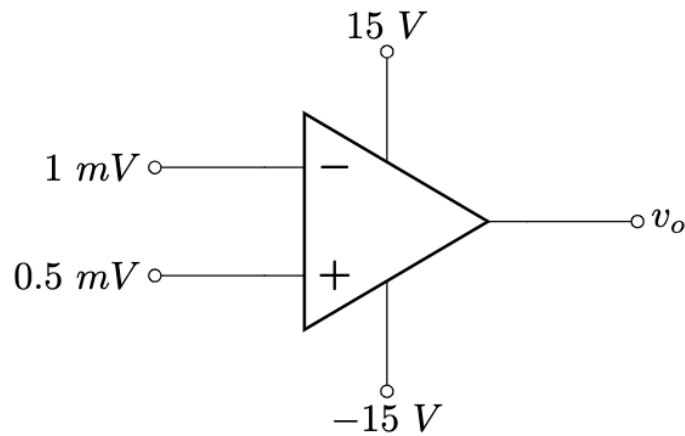

$$A = 2 \times 10^5$$

Solution:

$$V_d = V_{(+)} - V_{(-)} = (0.5 - 1) \text{ mV} = -0.5 \text{ mV}$$


$$AV_d = (2 \times 10^5) \times (-0.5 \times 10^{-3}) \text{ V} = -100 \text{ V}$$


Since $-15 \text{ V} > AV_d$

$$V_o = AV_d = -15 \text{ V}$$

Op-Amp Internal configuration



Voltage controlled voltage Source

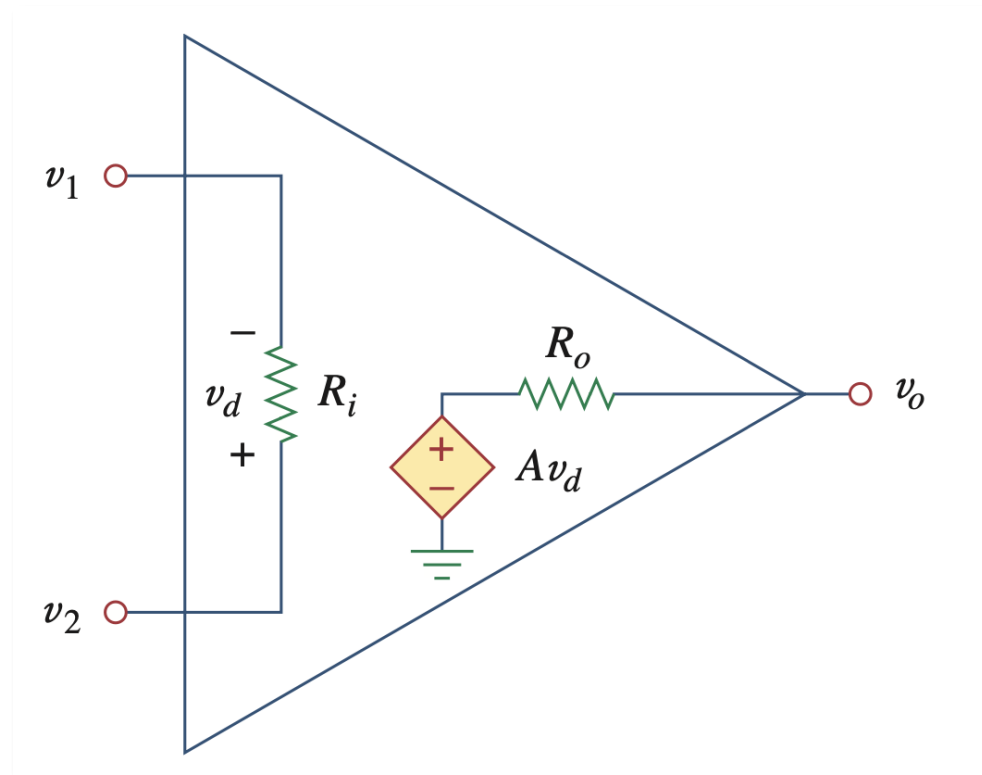

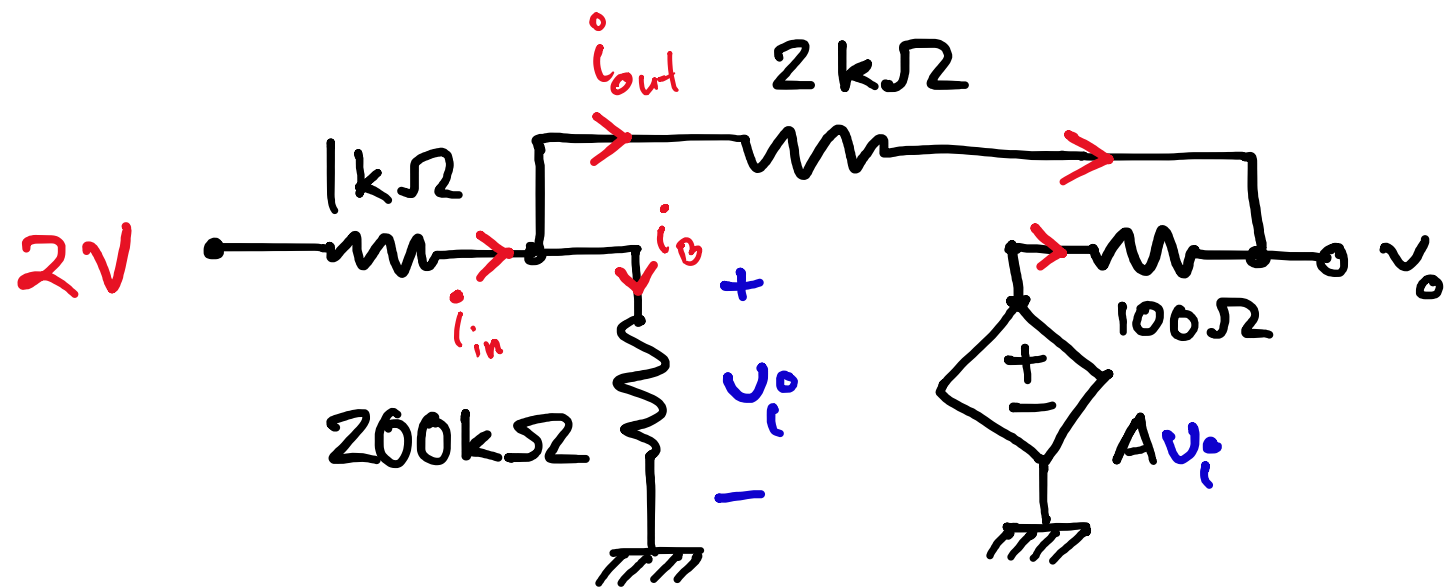

$$A = 2 \times 10^5$$


Op-Amp Internal Circuit

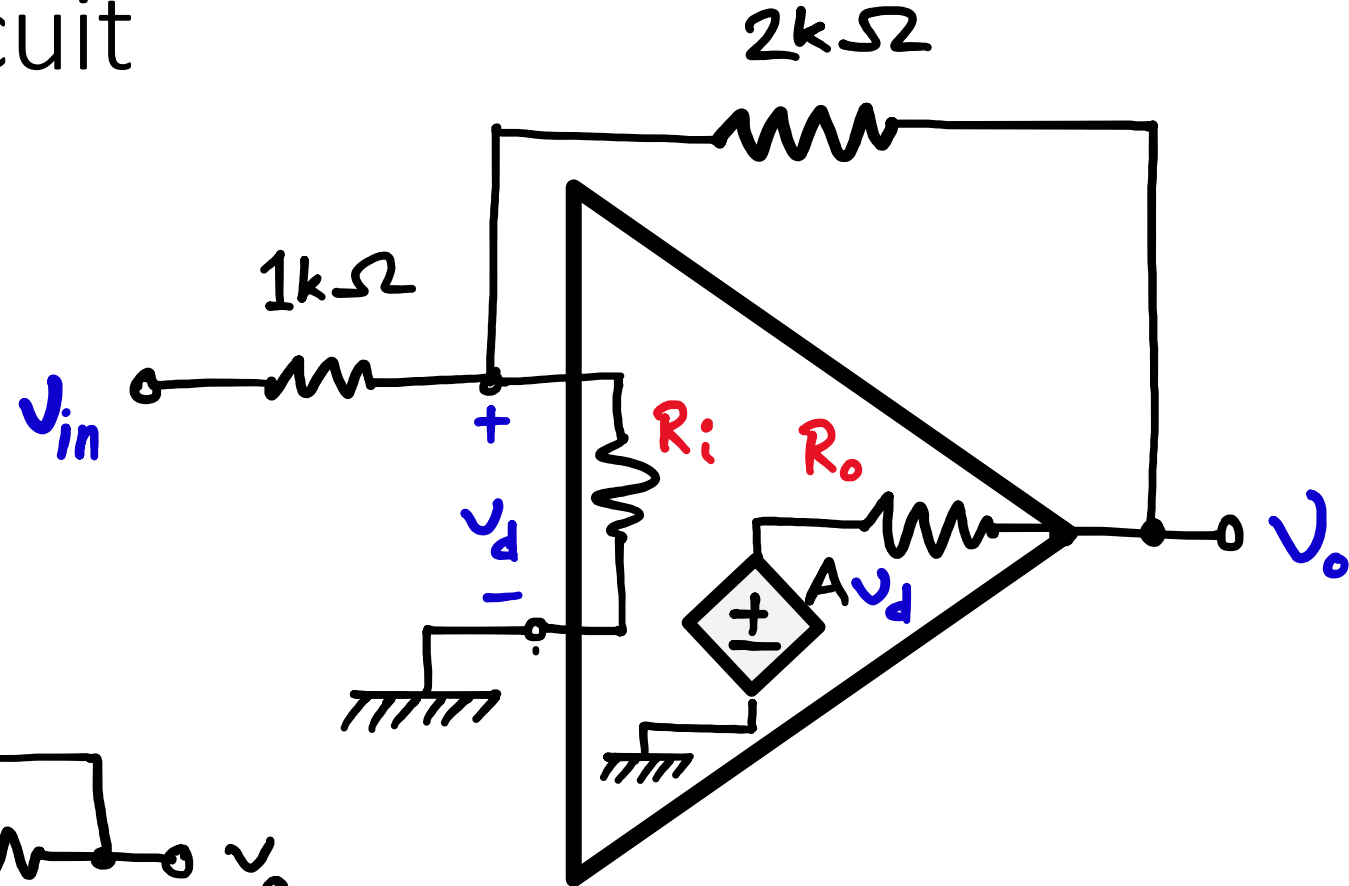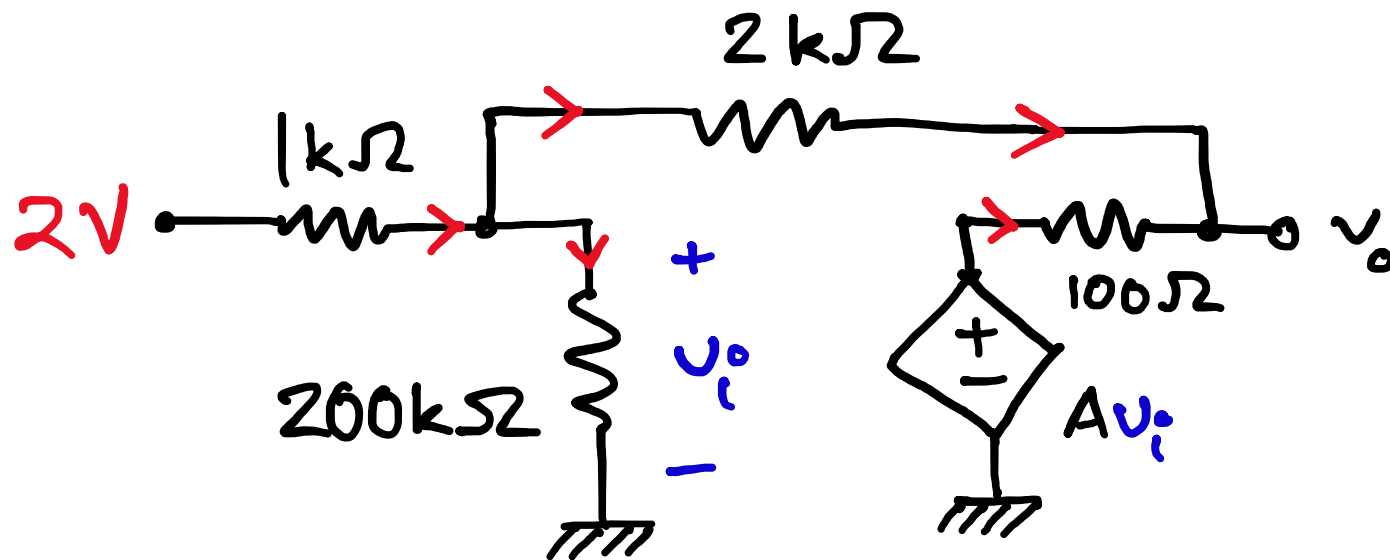

Important parameters of an Op-amp

- **Input resistance:** R_i
- **Output resistance:** R_o
- **Voltage (Differential/OL) Gain:** A/A_{OL} **Slope of VTC**
- **Positive Saturation Voltage:** $+V/V_{CC}/V_{sat}$
- **Negative Saturation Voltage:** $-V/V_{EE}/-V_{sat}$

Parameter	Typical Range	Ideally
A	$10^4 - 10^8$	∞
R_i	$100\text{ k}\Omega - 10^{10}\text{ k}\Omega$	∞
R_o	$0.01\text{ k}\Omega - 0.1\text{ k}\Omega$	0

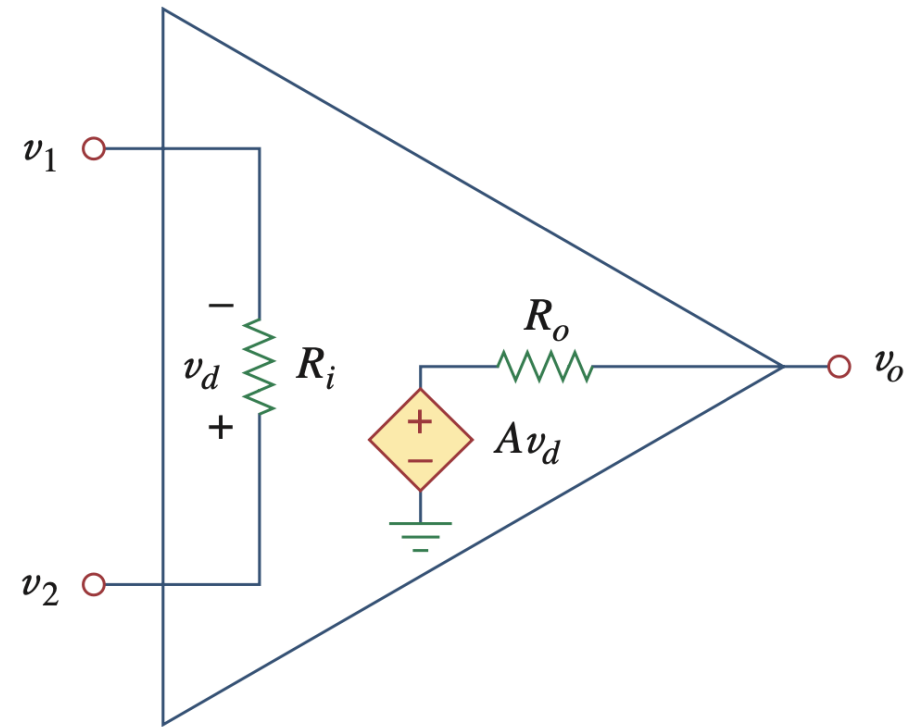

Some more circuits with OP AMP



Find i_F and v_o .

Here,

$$R_i = 200 \text{ k}\Omega$$

$$R_o = 0.1 \text{ k}\Omega$$

$$A = 2 \times 10^5$$

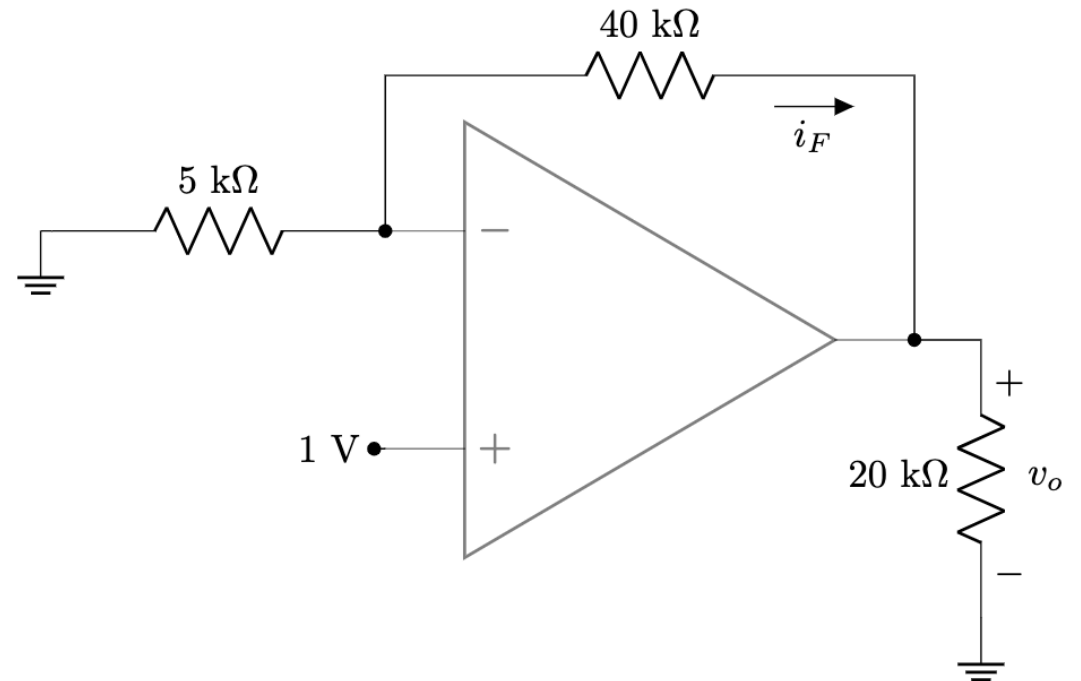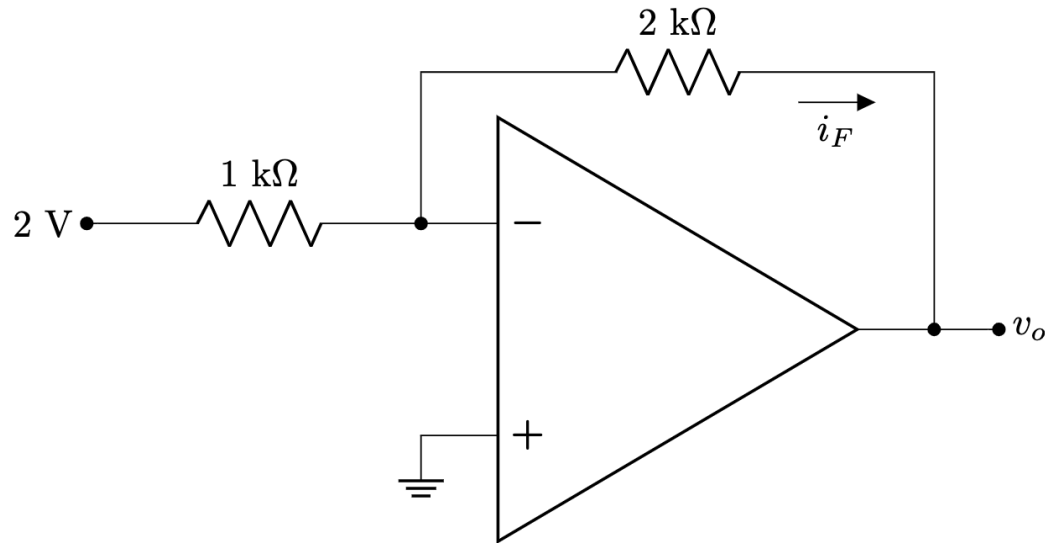

Example – Inverting Amplifier


Find i_F and v_o .

Here,

$$R_i = 200 \text{ k}\Omega$$

$$R_o = 0.1 \text{ k}\Omega$$

$$A = 2 \times 10^5$$

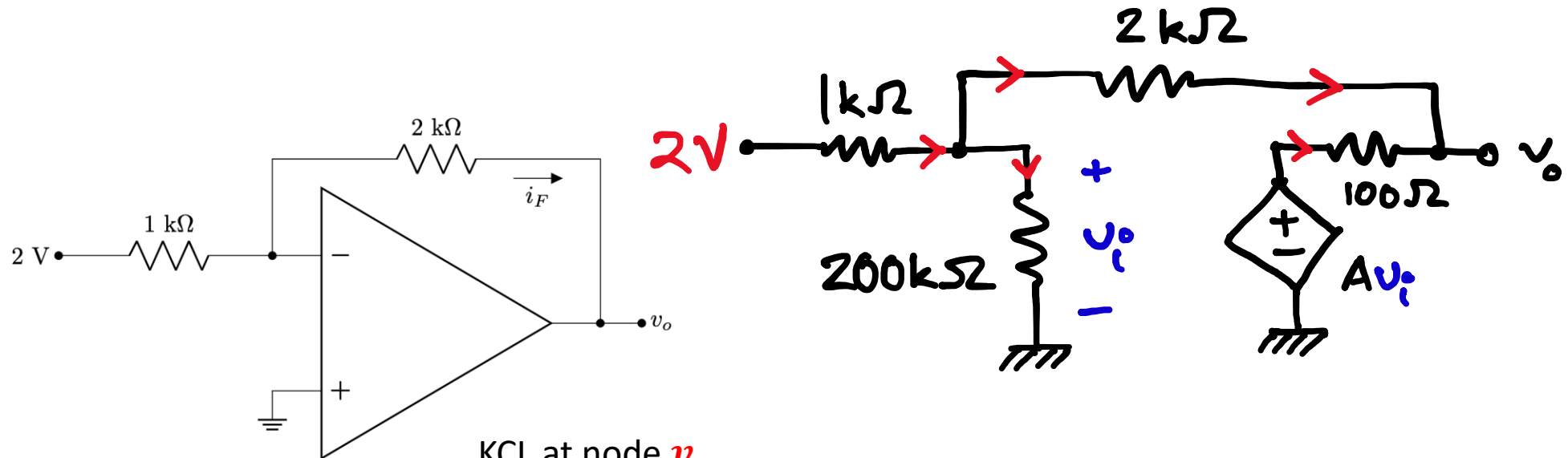

KCL at node v_i

$$\frac{2 - v_i}{1} = \frac{v_i - v_o}{2} + \frac{v_i}{200}$$

$$\frac{301}{200}v_i - \frac{1}{2}v_o = 2$$

KCL at node v_o

$$\frac{v_i - v_o}{2} + \frac{Av_i - v_o}{0.1} = 0$$



$$(2 \times 10^6 + 0.5)v_i - 10.5v_o = 0$$

$$\begin{aligned} v_i &= -21 \mu\text{V} \\ v_o &= -3.999 \text{ V} \\ i_F &= 2 \text{ mA} \end{aligned}$$

Characteristics of an Ideal Op-amp

Parameter	Typical Range	Ideally
A	$10^4 - 10^8$	∞
R_i	$100\text{ k}\Omega - 10^{10}\text{ k}\Omega$	∞
R_o	$0.01\text{ k}\Omega - 0.1\text{ k}\Omega$	0


VTC

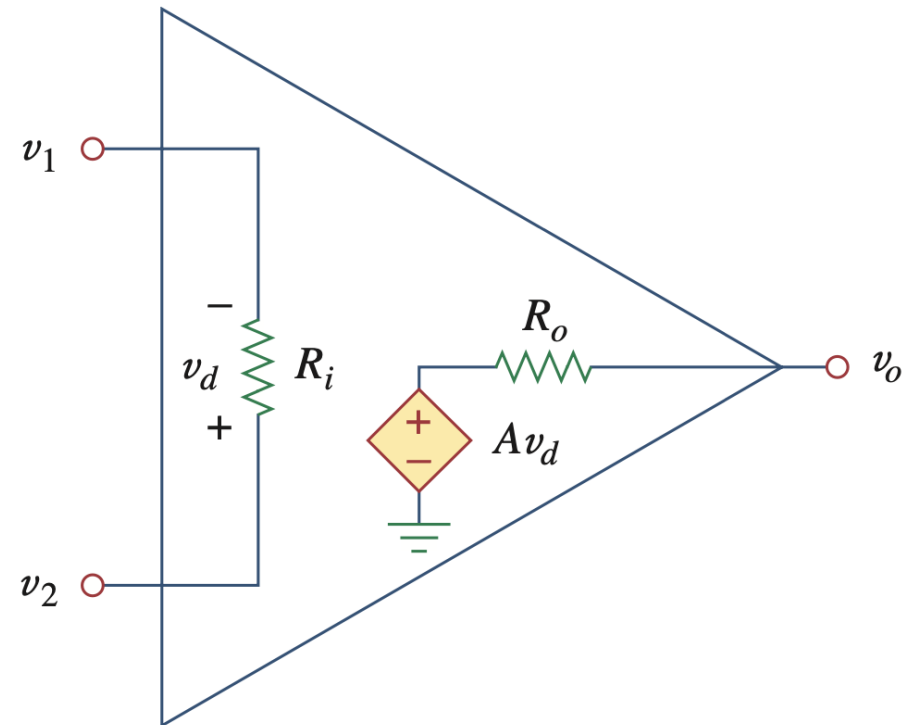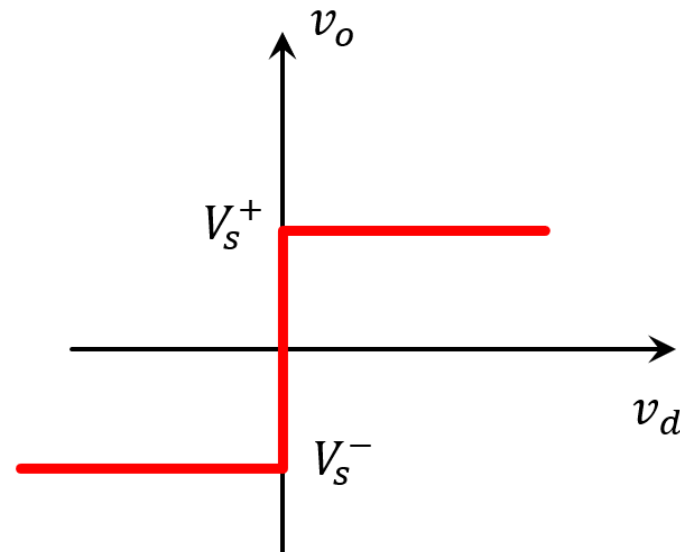

Types of Op-Amp configuration

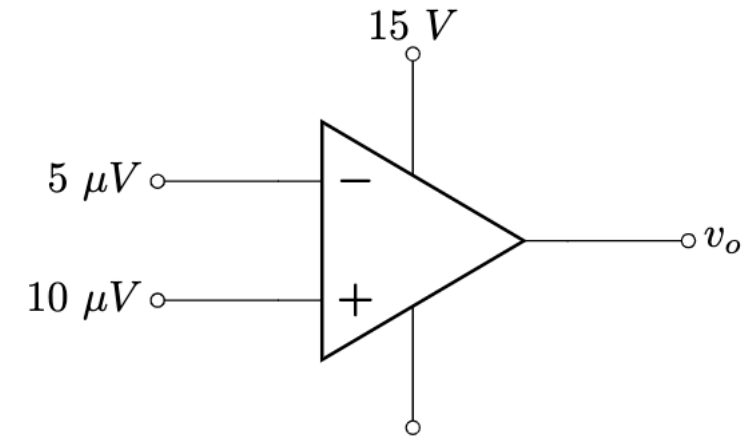
1. Open loop configuration:

No physical connection between input and output



2. Closed loop configuration:

Feedback from output terminal

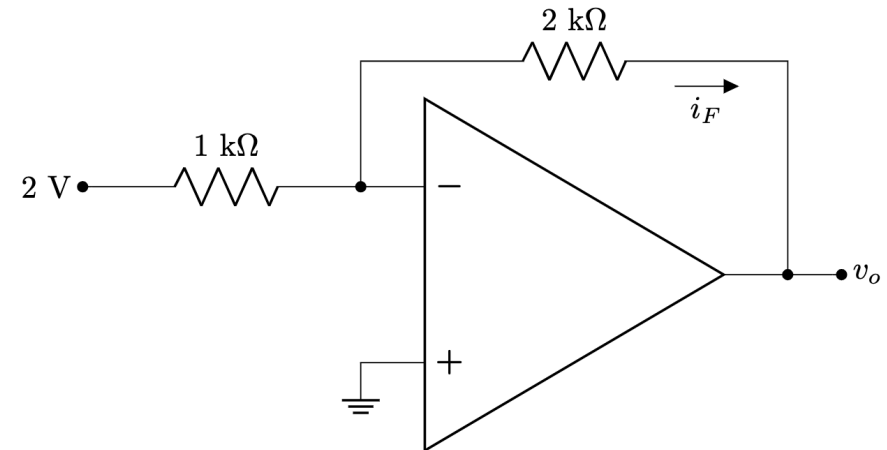

Open Loop Configuration → Ideal Op Amp

Voltage Transfer Characteristics (VTC)

Positive saturation:


$$\Rightarrow V_O = +V_{\text{sat}}$$

Linear Region

$$-V_{\text{sat}} < V_O = AV_d < +V_{\text{sat}}$$

Negative saturation:



$$\Rightarrow V_O = -V_{\text{sat}}$$

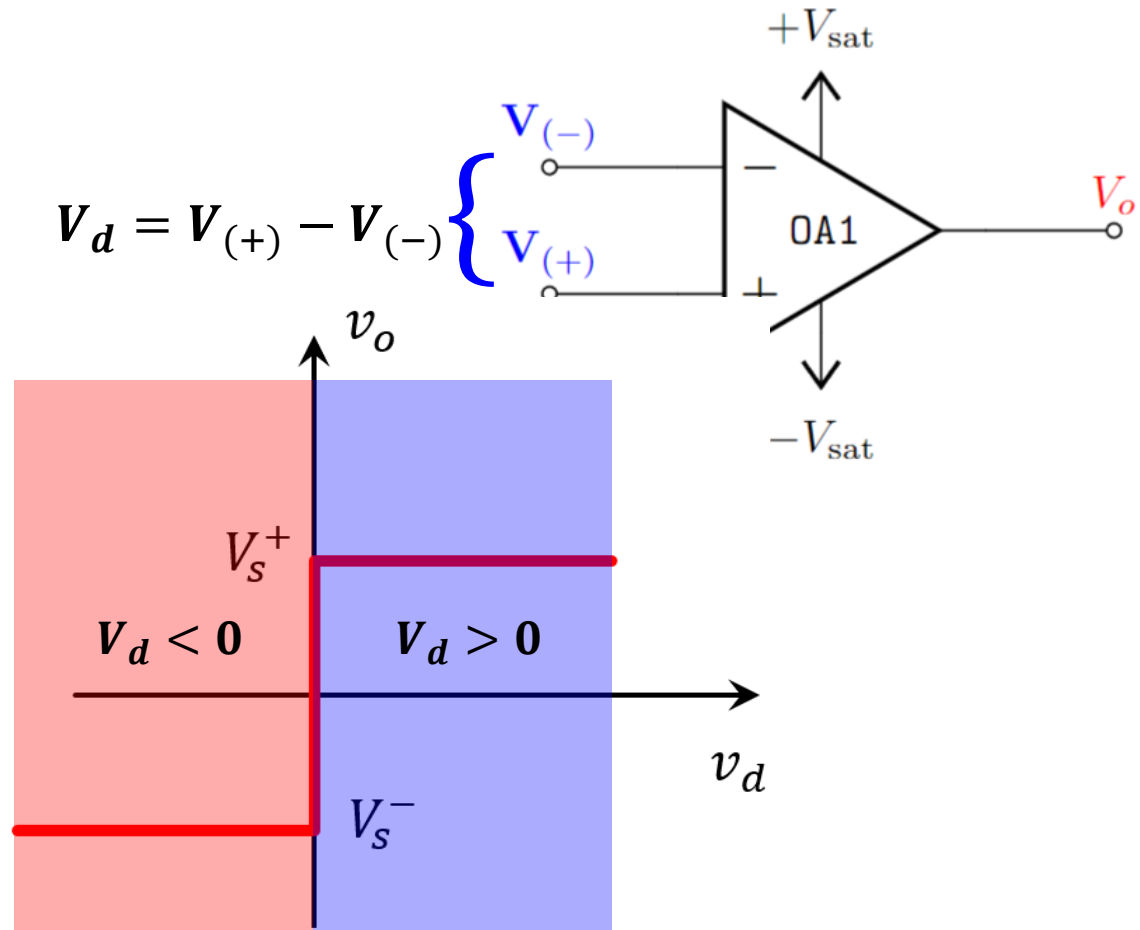

$A \rightarrow \infty$: Open Loop Gain

Open Loop Configuration: Comparator

Level Crossing Detector / Comparator

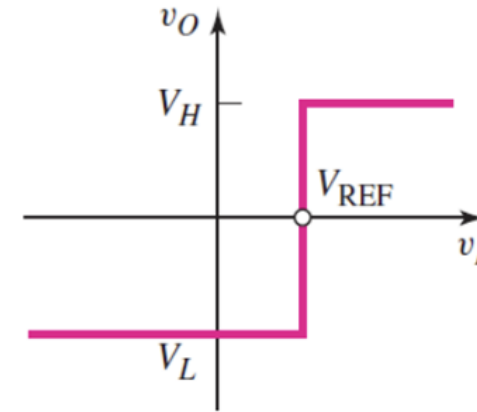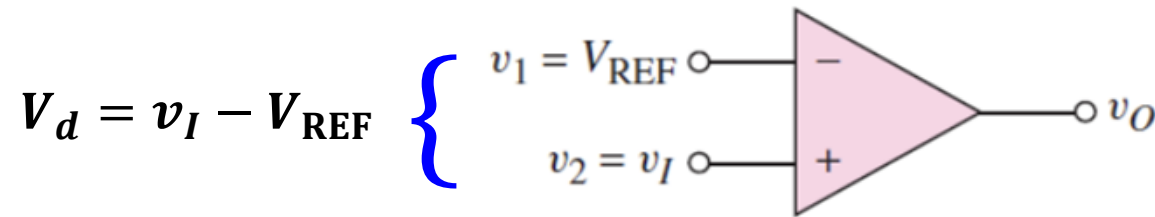


$$V_d = v_I - V_{\text{REF}} > 0 \quad \Rightarrow \quad v_O = V_H$$

$$v_I > V_{\text{REF}} \quad \Rightarrow \quad v_O = V_H$$

Open Loop Configuration: Comparator

Level Crossing Detector / Comparator

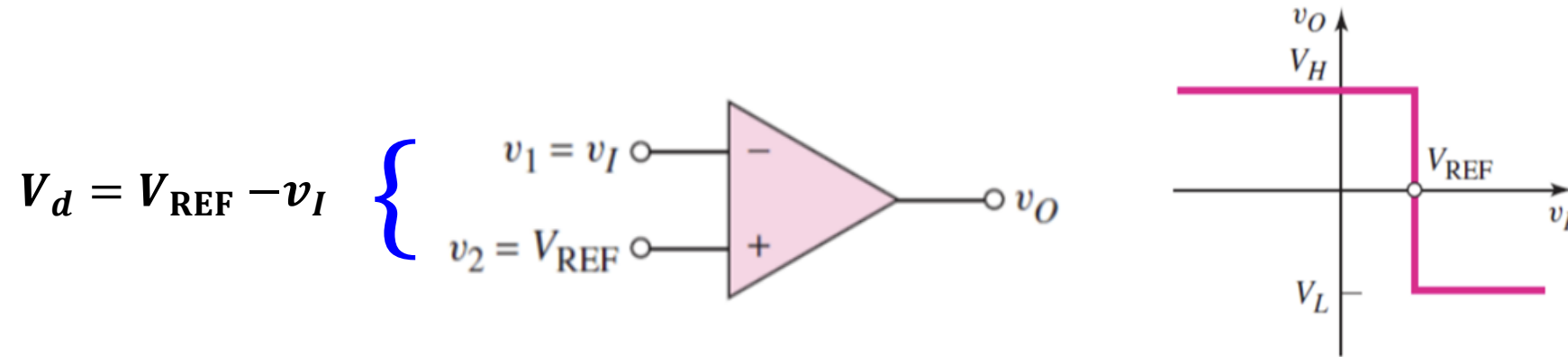

$$V_d = V_{\text{REF}} - v_I > 0 \quad \Rightarrow \quad v_O = V_H$$

$$v_I < V_{\text{REF}} \quad \Rightarrow \quad v_O = V_H$$

Open Loop Configuration: Comparator

Level Crossing Detector / Comparator

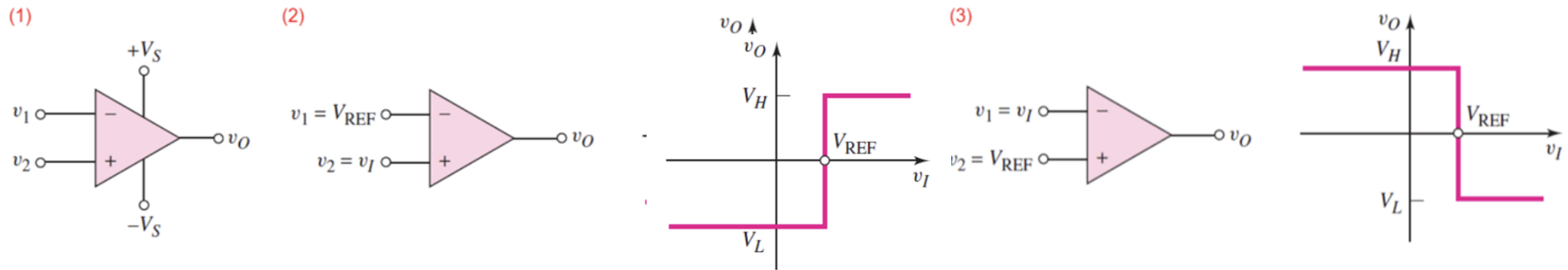





Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit

Open Loop Configuration: Comparator

Zero Crossing Detector

Compare values with a reference and pin value to $+V_{sat}$ if voltage is above or to below that.

Non-inverting configuration

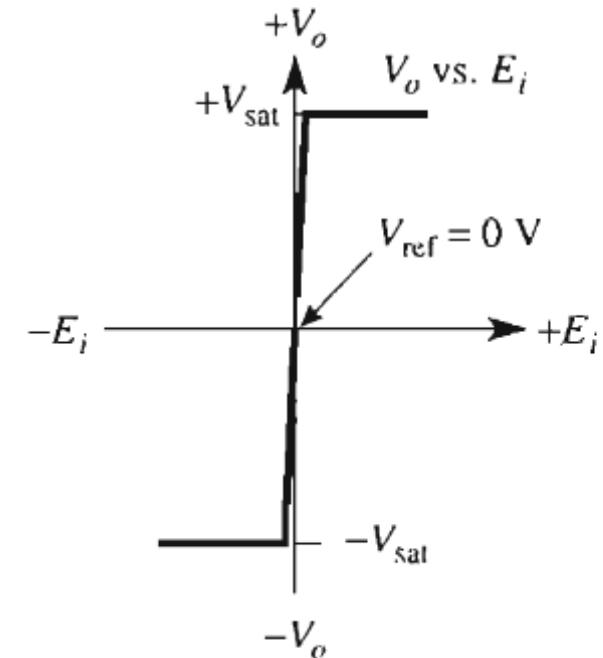
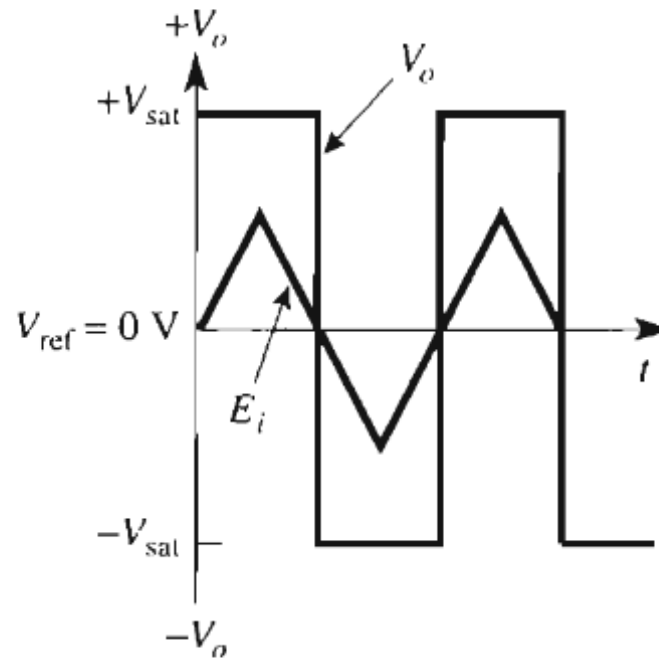
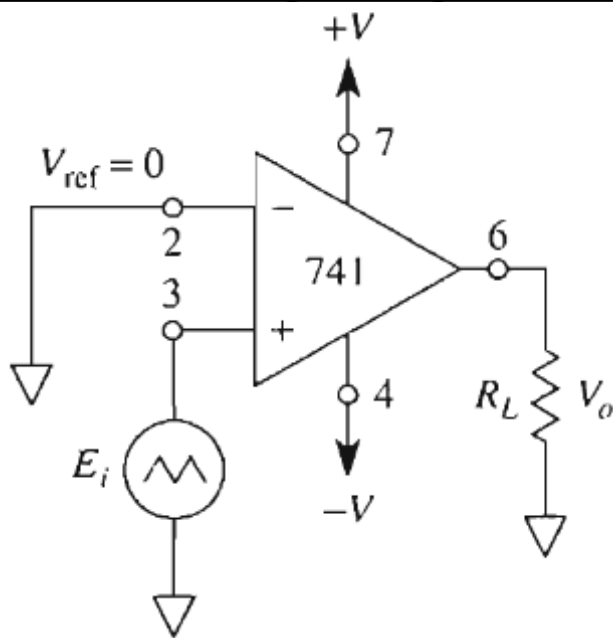


(a) Noninverting: When E_i is above V_{ref} , $V_o = +V_{sat}$.

Open Loop Configuration: Comparator

Zero Crossing Detector

Inverting configuration

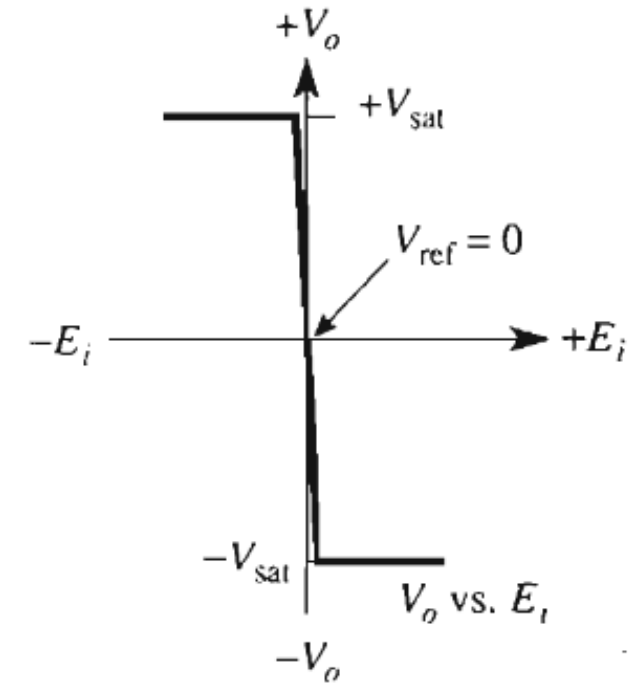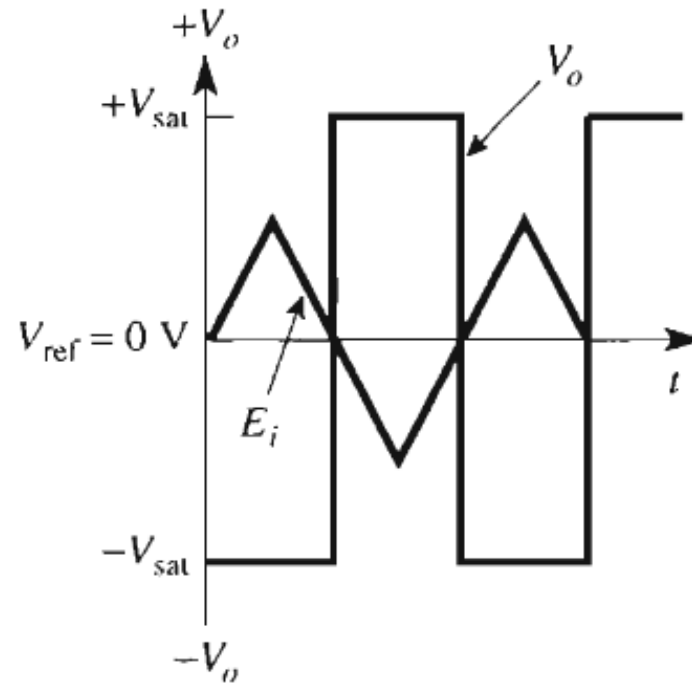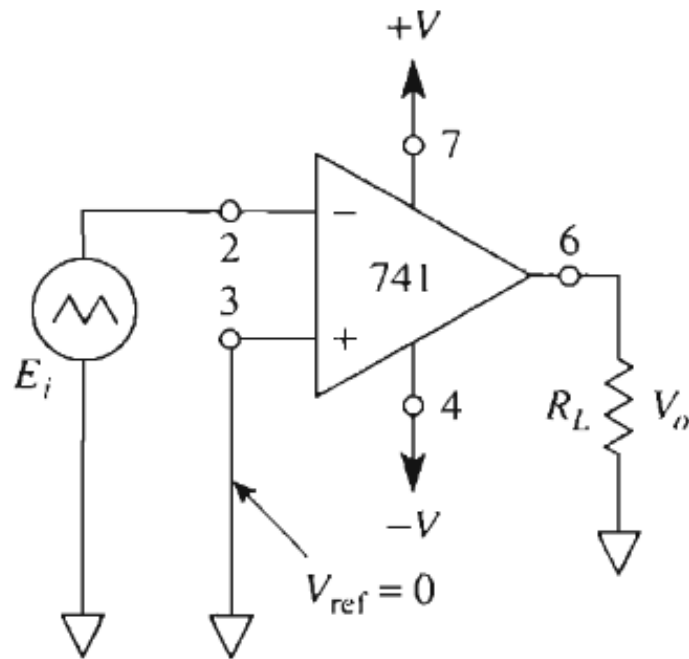

(b) Inverting: When E_i is above V_{ref} , $V_o = -V_{sat}$.

Comparator Application - Smoke Detectors


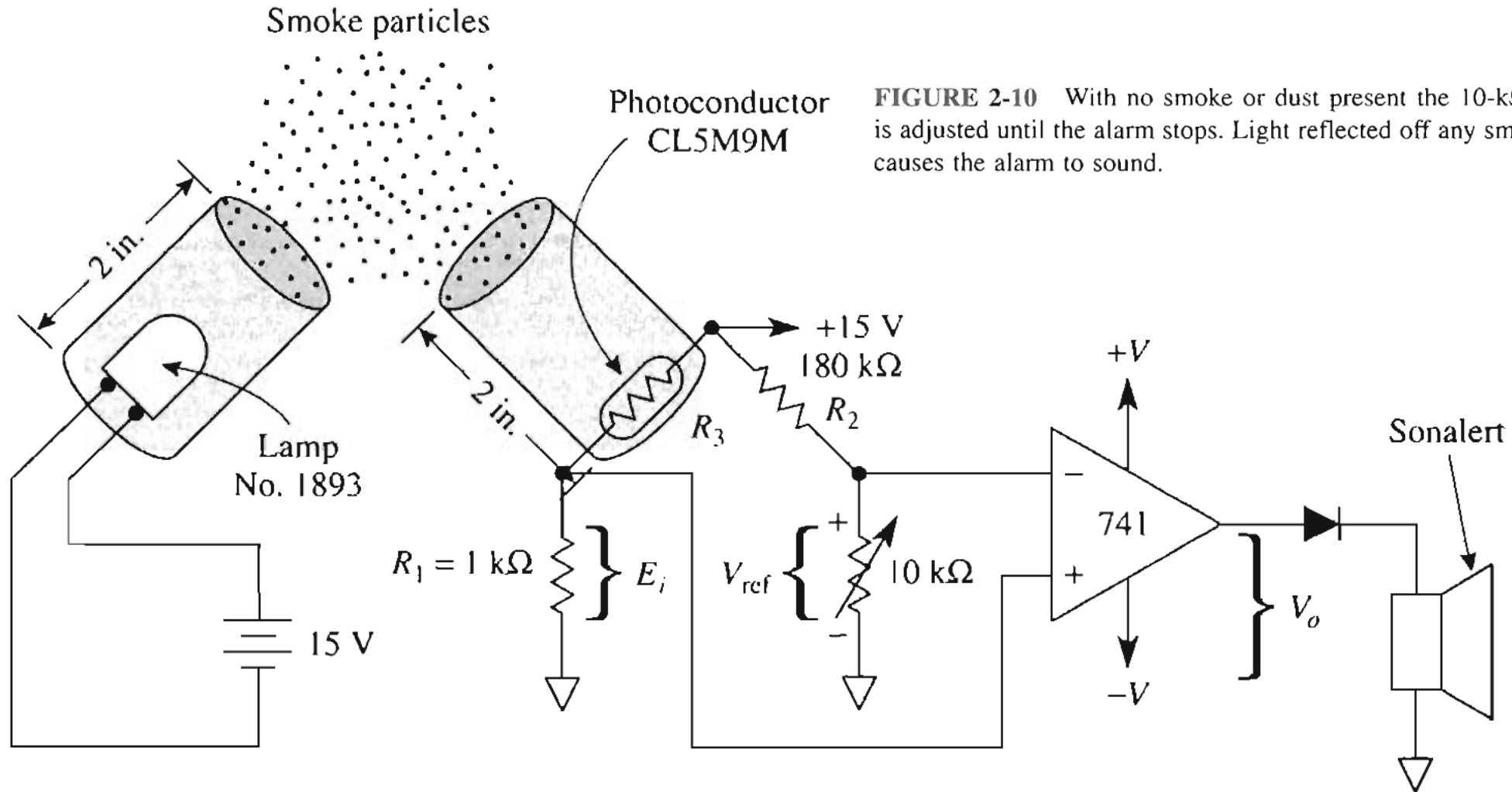



FIGURE 2-10 With no smoke or dust present the 10-k Ω sensitivity control is adjusted until the alarm stops. Light reflected off any smoke or dust particles causes the alarm to sound.

Comparator Application Smoke Detectors

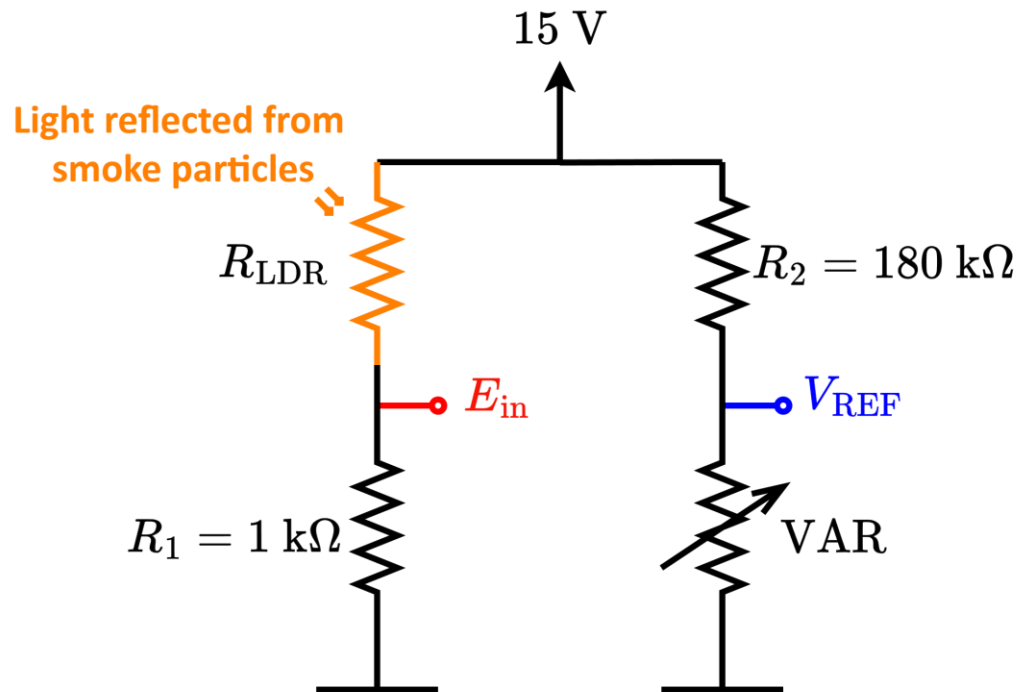Input Voltage E_{in} from the light reflected off the smoke



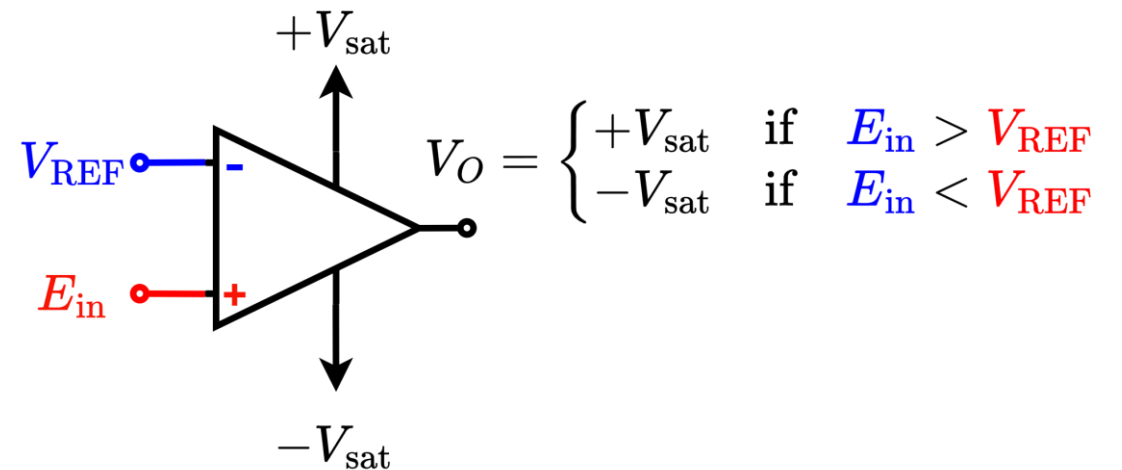
Reference voltage V_{REF} adjusted via the variable resistor (VAR)




Comparator Application - Smoke Detectors

Light from lamp is reflected from dust particles (if any) to the photoconductor.

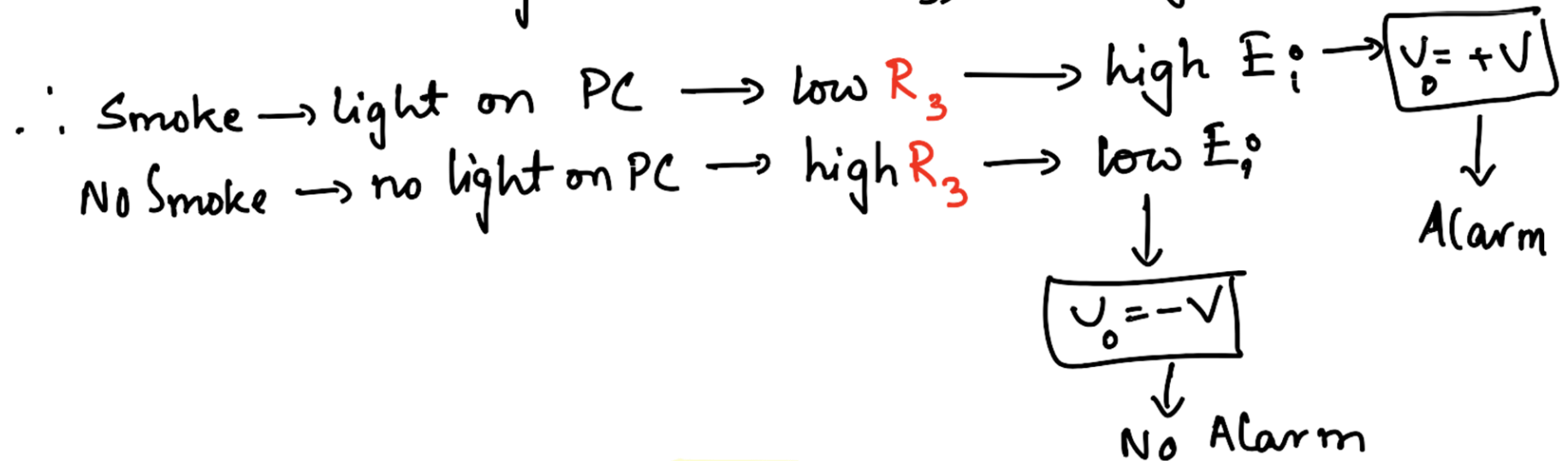Photoconductor: Low Resistance (R_3) if light incidents.
PC High Resistance (R_3) if no light incidents.




Comparator Application – Automatic AC

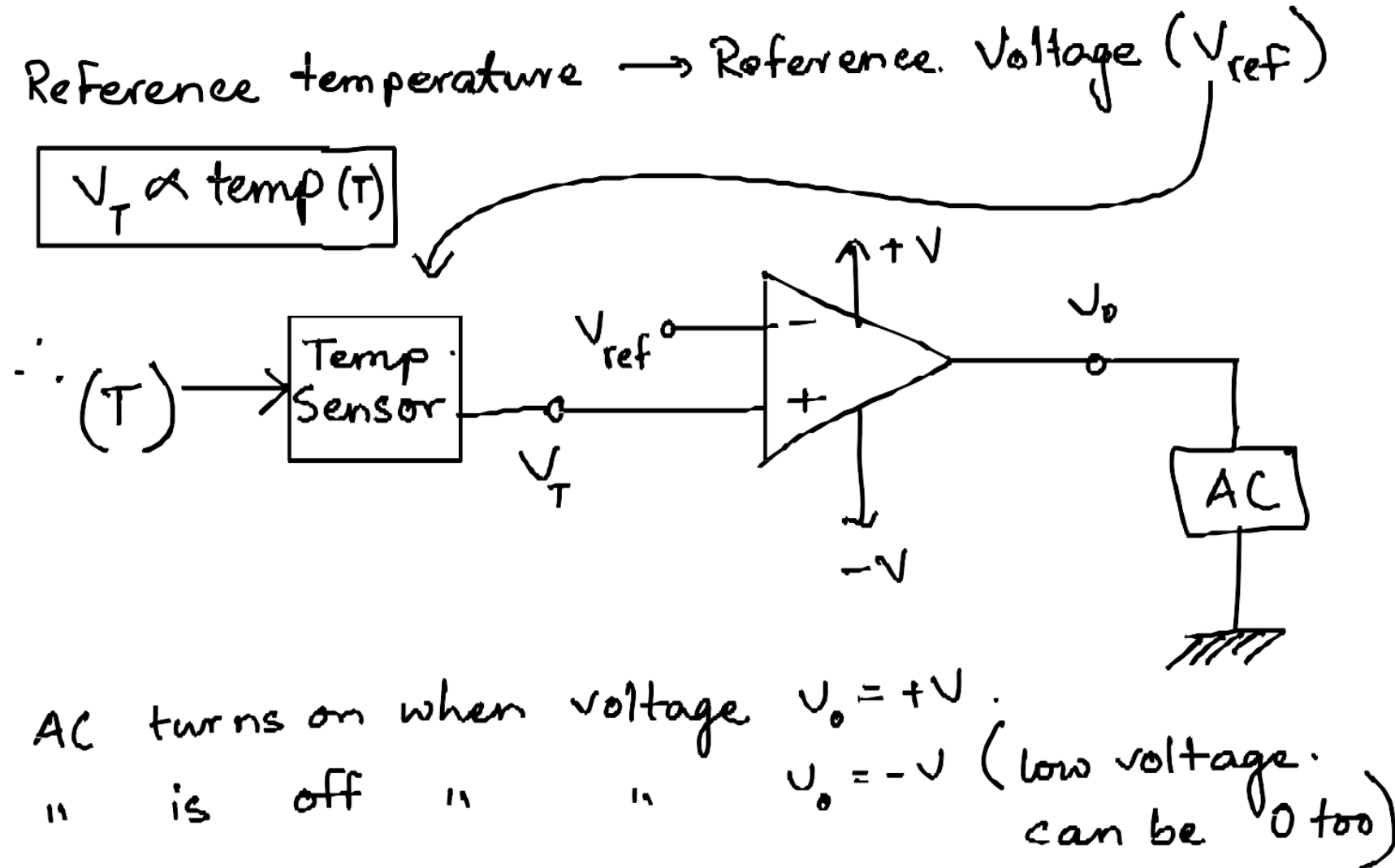

Closed Loop Configuration

Feedback

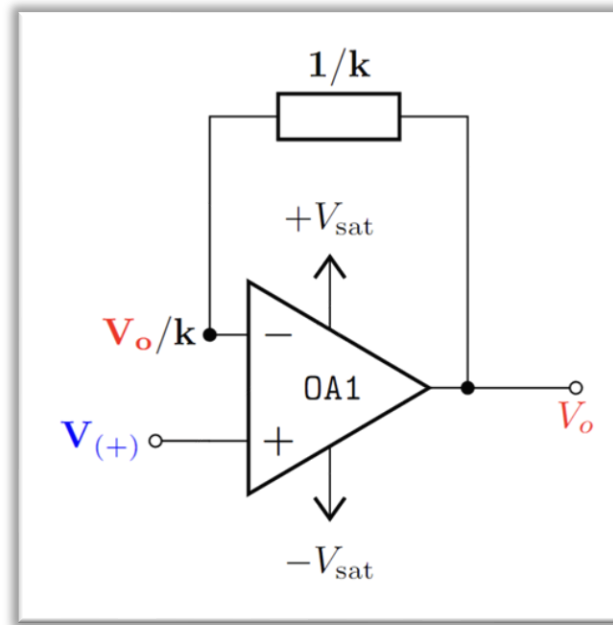

Feedback in Op-Amp circuit

Two types of feedback

1. Negative Feedback:

Output voltage is fed to the inputs **negatively**

The output voltage is connected to the **inverting** terminal



$$V_o \uparrow \Rightarrow \frac{V_o}{k} \uparrow \Rightarrow V_{(-)} \uparrow \Rightarrow V_d \downarrow = V_{(+)} - V_{(-)} \uparrow \Rightarrow V_o \propto V_d \downarrow$$

2. Positive Feedback:

Output voltage is fed to the inputs **positively**

The output voltage is connected to the **non-inverting** terminal
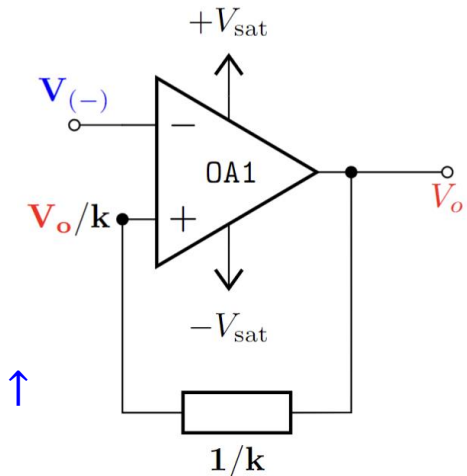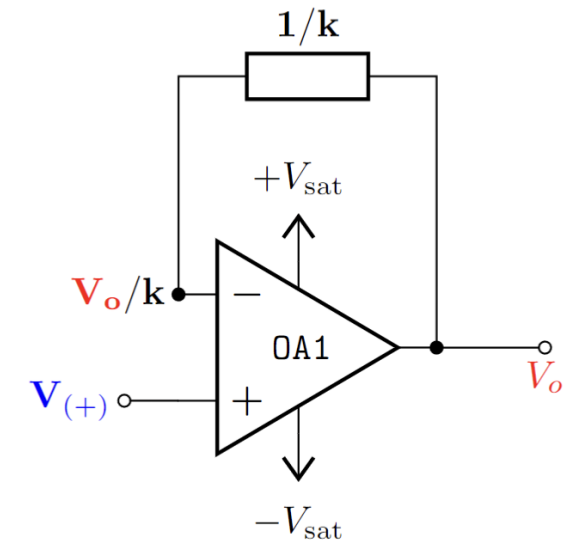
$$V_o \uparrow \Rightarrow \frac{V_o}{k} \uparrow \Rightarrow V_{(+)} \uparrow \Rightarrow V_d \uparrow = V_{(+)} \uparrow - V_{(-)} \Rightarrow V_o \propto V_d \uparrow$$



Feedback in Op-Amp circuit

Two types of feedback

1. Negative Feedback:

Output voltage is fed to the inputs **negatively**

The output voltage is connected to the **inverting** terminal



$$V_o \uparrow \Rightarrow V_o \propto V_d \downarrow$$

2. Positive Feedback:

Output voltage is fed to the inputs **positively**

The output voltage is connected to the **non-inverting** terminal
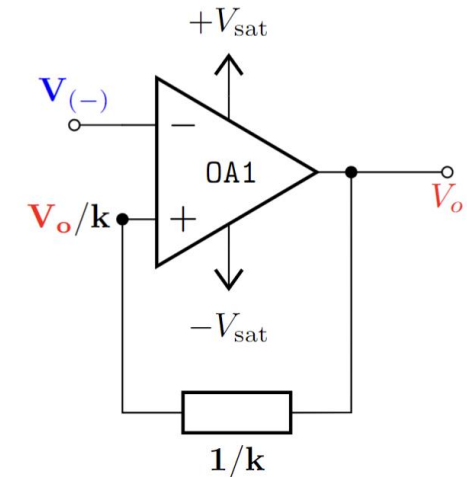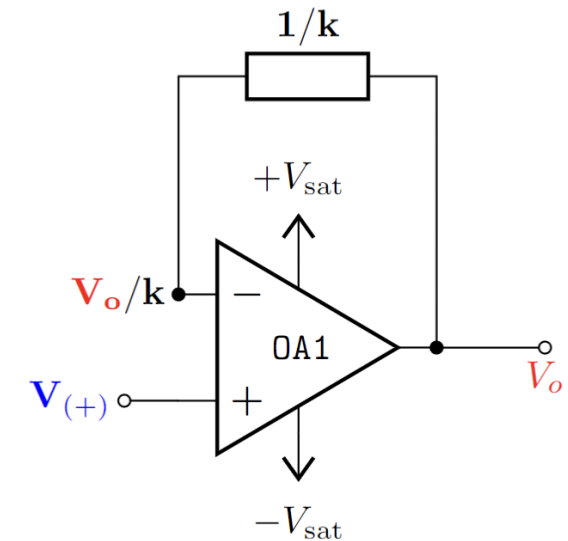
$$V_o \uparrow \Rightarrow V_o \propto V_d \uparrow$$



Feedback in Op-Amp circuit

Negative Feedback:

Output voltage is fed to the inputs **negatively**

The **output voltage** is connected to the **inverting** terminal

$$\text{Here, } V_{(-)} = \frac{V_o}{k}$$

$$\text{We know, } V_o = A V_d$$

$$V_o = A(V_{(+)} - V_{(-)})$$

$$= A\left(V_{(+)} - \frac{V_o}{k}\right)$$


$$= A V_{(+)} - \frac{A}{k} V_o$$

$$\Rightarrow V_o\left(1 + \frac{A}{k}\right) = A V_{(+)}$$

$$\frac{V_o}{V_{(+)}} = \frac{A}{1 + \frac{A}{k}} = \frac{1}{\frac{1}{A} + \frac{1}{k}}$$

$$\text{If } A \rightarrow \infty \text{ then } \frac{1}{A} \rightarrow 0.$$
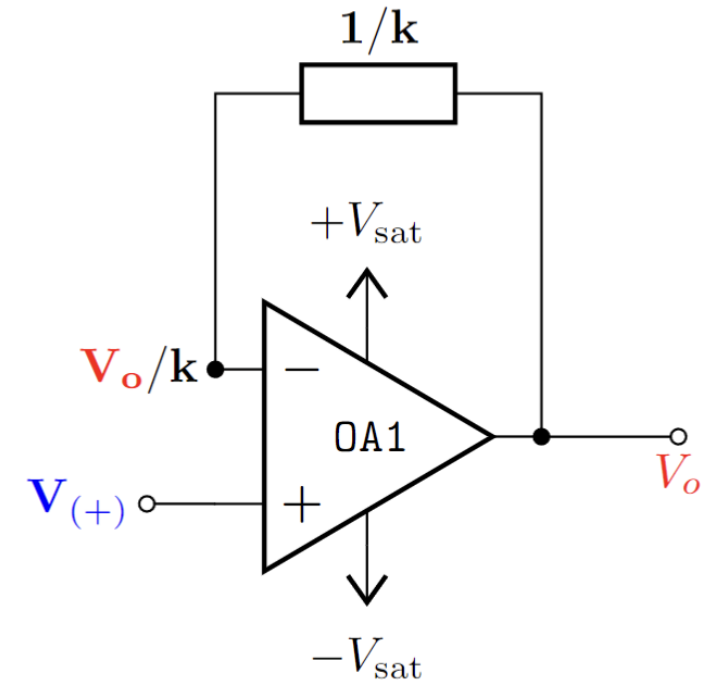
$$\therefore \frac{V_o}{V_{(+)}} = k \quad \text{This is the new amplification factor / Gain}$$





Negative Feedback in Op-Amp circuit

The **output voltage** is transformed in the following way:

$$V_{(-)} = \frac{1}{k} \cdot V_o$$

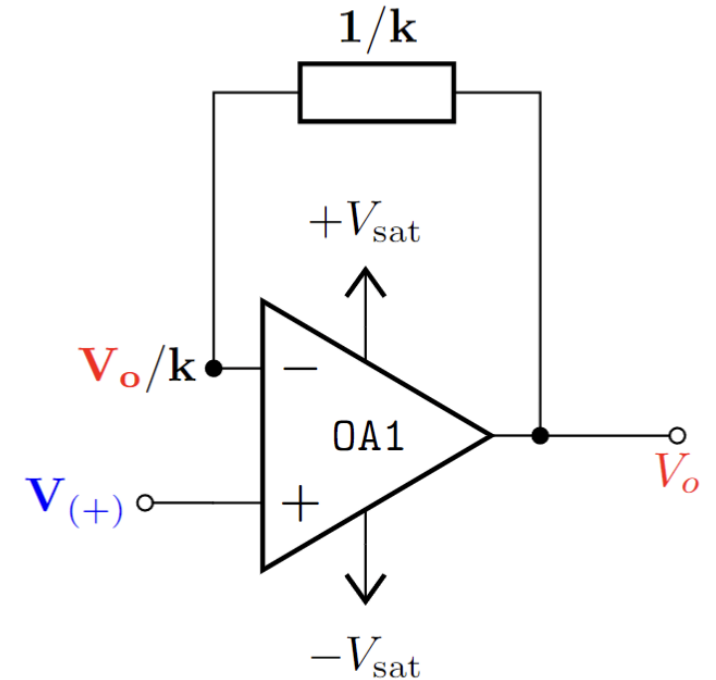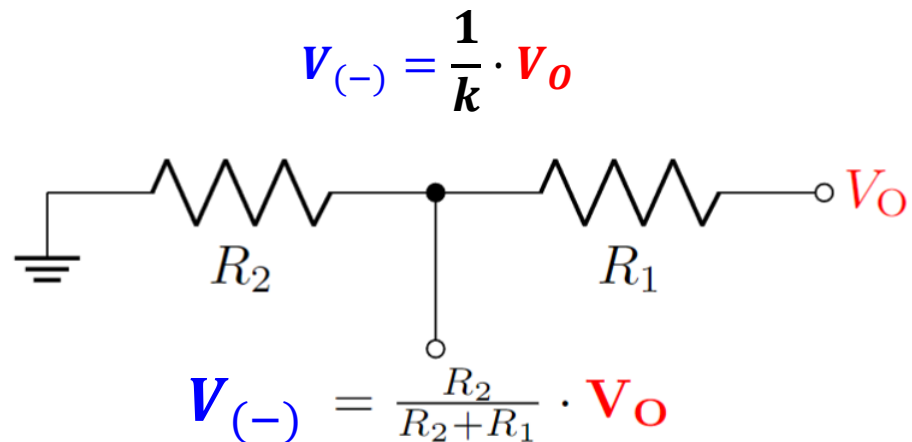
This factor of $1/k$ can be achieved with a voltage divider network.



A voltage divider can act as a multiplier/factor in the **feedback** branch


Negative Feedback in Op-Amp circuit

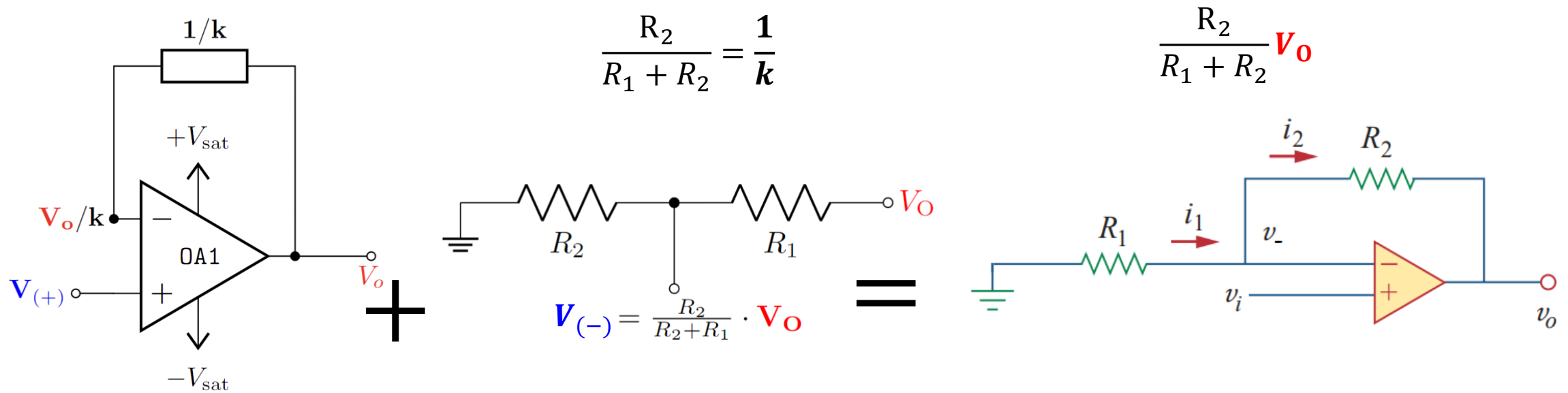A voltage divider can act as a multiplier/factor in the **feedback** branch



If $k = 10$ (meaning we feed back one tenth of the output to negative input), we will get $v_o = 10 \cdot v_i$. that is 10-fold gain.

Solving Closed Loop Op-Amp Circuit

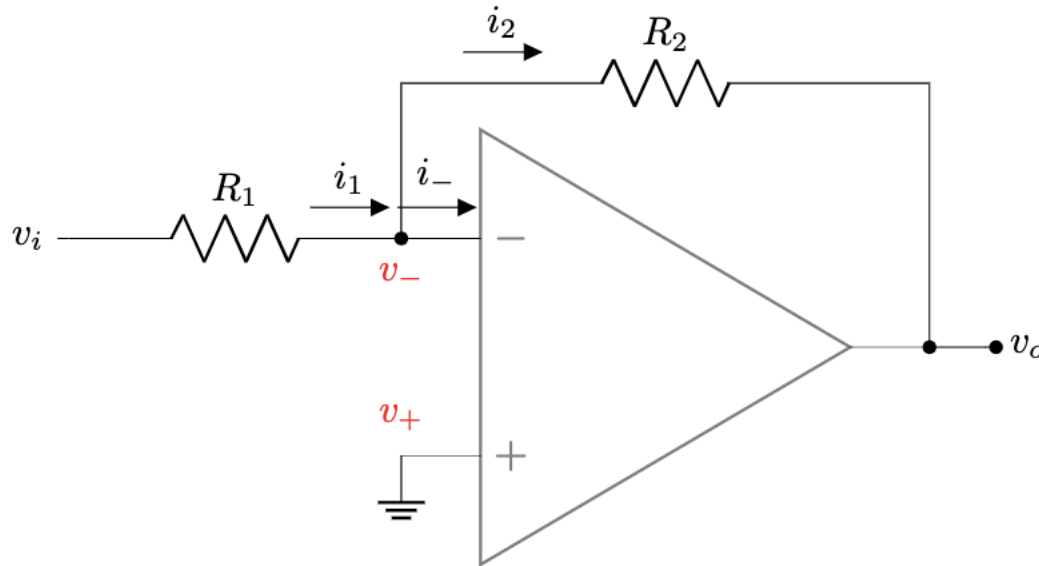

$$\text{Gain} = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

Since v_+ is connected to ground, $v_+ = 0 \text{ V}$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0 \text{ V}$

From Ohm's law for $R_1 \Rightarrow i_1 = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$


Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = v_i/R_1$


From Ohm's law for $R_2 \Rightarrow i_2 = \frac{v_- - v_o}{R_2} = \frac{v_i}{R_1} \Rightarrow v_o = -i_2 \times R_2 \Rightarrow v_o = -\frac{R_2}{R_1} v_i$ [ANS]

Solving Closed Loop Op-Amp Circuit

- For ideal op-amp
 - Infinite input resistance, $R_i = \infty = \text{open circuit}$
 - Zero output resistance, $R_o = 0 = \text{short circuit}$
 - $i_i = 0$ and $i_+ = 0$
- **When there is negative feedback**, For ideal A as is infinitely high, for a finite output voltage v_o , $\frac{v_o}{A} = v_d = 0 \Rightarrow v_+ = v_-$. This is called **virtual short circuit**
- Because of these, solving ideal op-amp circuit with negative feedback is very simple

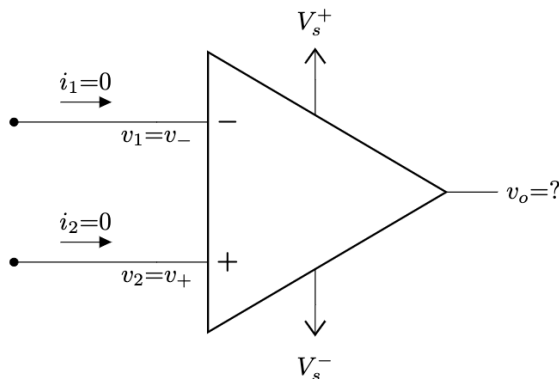

Example

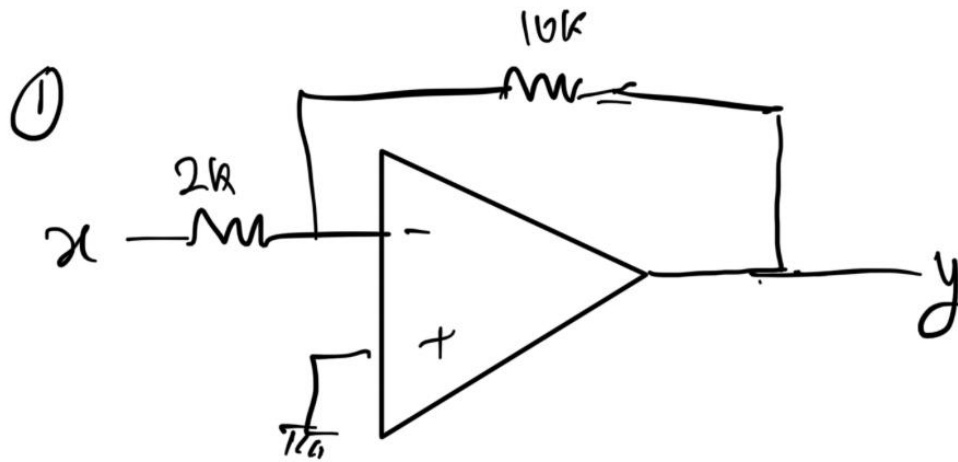

<https://forms.gle/foiEHQvKDAh2KM3i6>

