

CSE251: Electronic Devices and Circuits

Lecture: 14 - 16 – MOSFET

Prepared By:

Shadman Shahid (SHD)

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: ext.shadman.shahid@bracu.ac.bd


Outline

- Introduction to Electronic Switches
- Basic Inverter
- Introduction to Controlled Sources
- Introduction to MOSFET
- MOSFET as digital switch
- Designing Logic gates with MOSFETs


Two terminal Devices

Linear Devices


Resistor

 

Voltage Source

 


Current Source

 

IV characteristics of two terminal devices are fixed.

Non-linear Devices

Diode

 


IV characteristics of **three terminal devices** can be changed

Three terminal Devices


IV of two terminal can be controlled using a third terminal.

Example: Switch, MOSFET, BJT


Switch

 

 
IV characteristics between T_1 and T_2 can be controlled by C



Switch **ON**

 


Switch **OFF**

 


Switch – Types

 - Depending on the control, the switch can be
 - **Analog:** Controlled using physical toggle/button
 - **Digital:** Controlled using voltage or current. Example – MOSFET (voltage controlled), BJT (current controlled)




Analog switches

 

Digital switches (Transistors)


Switch Application – Logic Gates

 - We can use switches to build logic gates



A	B	Bulb
0	0	OFF
0	1	OFF
1	0	OFF
1	1	ON


AND operation

 


A	B	Bulb
0	0	OFF
0	1	ON
1	0	ON
1	1	ON

OR operation


Switch Application – Logic Gates

 

A	Bulb
0	
1	

 

A	B	Bulb
0	0	
0	1	
1	0	
1	1	

 


A	B	Bulb
0	0	
0	1	
1	0	
1	1	

These circuits are “preferred” – because they can be cascaded to build combinational logic circuits
-> if we remove the bulb and use the voltage across instead to cascade and drive the next gate


Switch Application – Logic Gates

Alternative representations:

 

Switch Application – Logic Gates


Alternative representations:

 

$$OUT = \overline{AB}$$


(NAND)

Switch Application – Logic Gates

 


$$OUT = \overline{A}$$

A	V _{OUT}
0	5V
1	0V

 

$$OUT = \overline{AB}$$

A	B	V _{OUT}
0	0	5V
0	1	5V
1	0	5V
1	1	0V

 


$$OUT = \overline{A+B}$$

A	B	V _{OUT}
0	0	5V
0	1	0V
1	0	0V
1	1	0V


Examples

①

 

$$f = \overline{A + B.C}$$


②

 

$$f = \overline{A\overline{B}}$$

Example


Implement using switches: $f = (A + B)C$

 

Practice Problem 1

In digital systems, binary data may be subjected to noise that can alter a 0 to a 1 or a 1 to a 0.

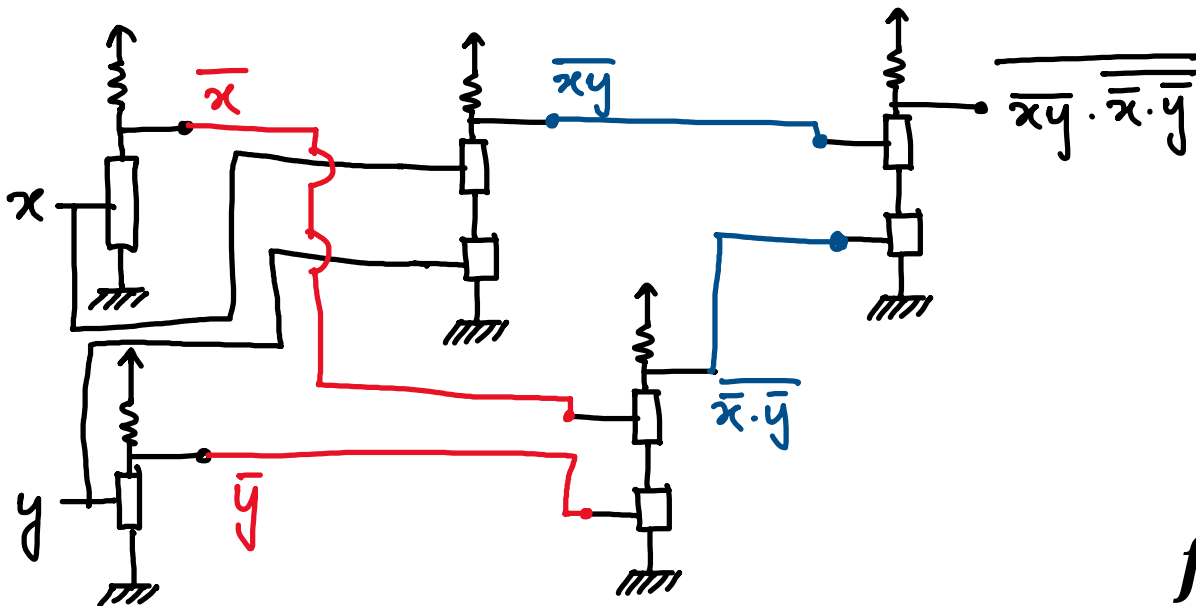A simple way to check if any error has occurred is to use an **even parity checker**. If there are two input bits x and y , the output of the even parity checker (denoted as f) will be **HIGH** if there are even number of 1s, i.e., if both x and y are 0 or if both of them are 1.



x	y	f
0	0	
0	1	
1	0	
1	1	

$$\begin{aligned} f &= x \cdot y + \bar{x} \cdot \bar{y} = \overline{\overline{x \cdot y + \bar{x} \cdot \bar{y}}} \\ &= \overline{\overline{x \cdot y} \cdot \overline{\bar{x} \cdot \bar{y}}} \end{aligned}$$

Digital Representation

- Binary → Two states (0/False, 1/True)
- Binary variables in circuit, need to use two states of device/parameters

Voltage

Current




State

|

|




Transistors as Digital Switch

- Transistors are 3 terminal non-linear devices, can be used as switch
- 2 types – **Voltage Controlled**, **Current Controlled**
- **M**etal **O**xide **S**emiconductor **F**ield **E**ffect **T**ransistor (**MOSFET**) are **voltage controlled**
- Control, $C = V_{GS}$. The IV characteristics (I_{DS} vs V_{DS}) depends on V_{GS}
- Actual dependency is complex.
- Will start with a simple (but approximate) one – **S-Model** (Switch Model)

   


MOSFET S-Model

 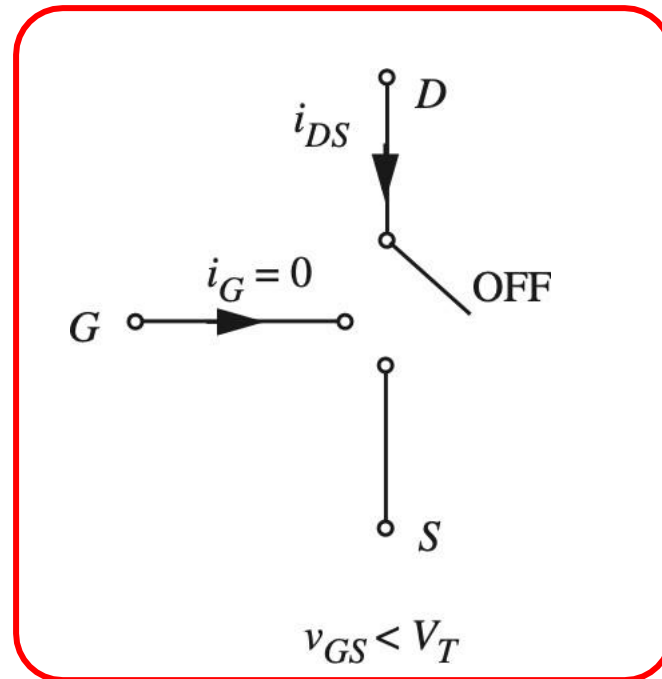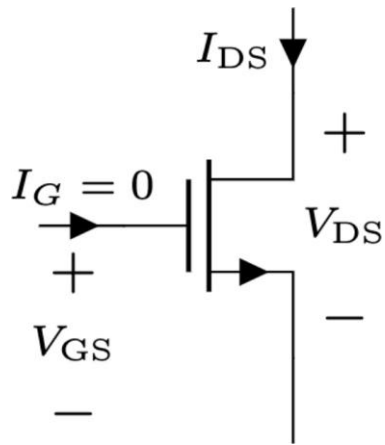- The MOSFET (approximately) behaves like a switch
- $C = V_{GS}$. Here, $C = \text{"0"} \Rightarrow V_{GS} < V_T$, and $C = \text{"1"} \Rightarrow V_{GS} \geq V_T$



MOSFET S-Model

 

We can summarize the S model for the MOSFET in algebraic form by stating its v - i characteristics as follows:


$$\text{for } v_{GS} < V_T, \quad i_{DS} = 0$$

and


$$\text{for } v_{GS} \geq V_T, \quad v_{DS} = 0 \quad (6.2)$$

Logic Gates using MOSFET


Just replace the switches with MOSFETs!

 

NOT Gate (Inverter)

 


NAND Gate (Inverter)

 


NOR Gate (Inverter)

MOSFET Logic Gates – More Examples

 

$$OUT = \overline{AB + C + D}$$

 

$$Out = \overline{\overline{(A + B)CD}} = (A + B)CD$$

Practice Problem 2


- **Design** a circuit using ideal MOSFETs (S-model) to implement the logic function

$$f = \overline{AC} + \overline{(B + C)}$$

$$= \overline{\overline{AC} + \overline{(B + C)}}$$

$$= \overline{\overline{AC}} \cdot \overline{\overline{(B + C)}} \quad [\text{De Morgan's Theorem}]$$

 
$$= \overline{AC} \cdot \overline{(B + C)}$$



Practice Problem 1

In digital systems, binary data may be subjected to noise that can alter a 0 to a 1 or a 1 to a 0.

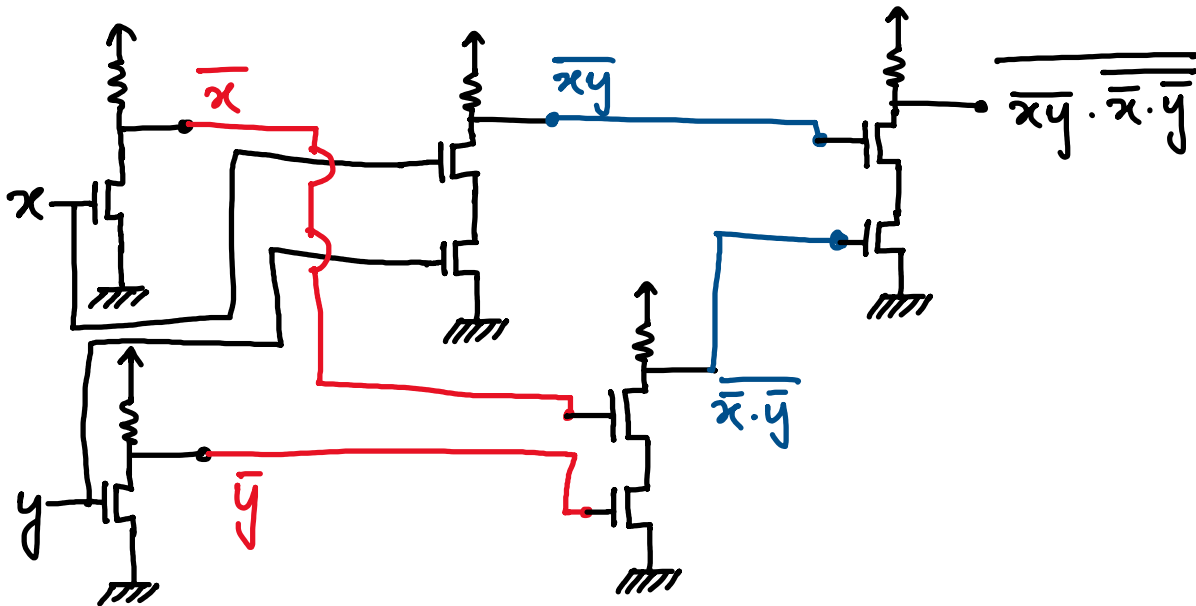A simple way to check if any error has occurred is to use an **even parity checker**. If there are two input bits x and y , the output of the even parity checker (denoted as f) will be **HIGH** if there are even number of 1s, i.e., if both x and y are 0 or if both of them are 1.




x	y	f
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned} f &= x \cdot y + \bar{x} \cdot \bar{y} = \overline{\overline{x \cdot y + \bar{x} \cdot \bar{y}}} \\ &= \overline{\bar{x} \cdot \bar{y} \cdot x \cdot y} \end{aligned}$$


Voltage Transfer Characteristics (VTC)

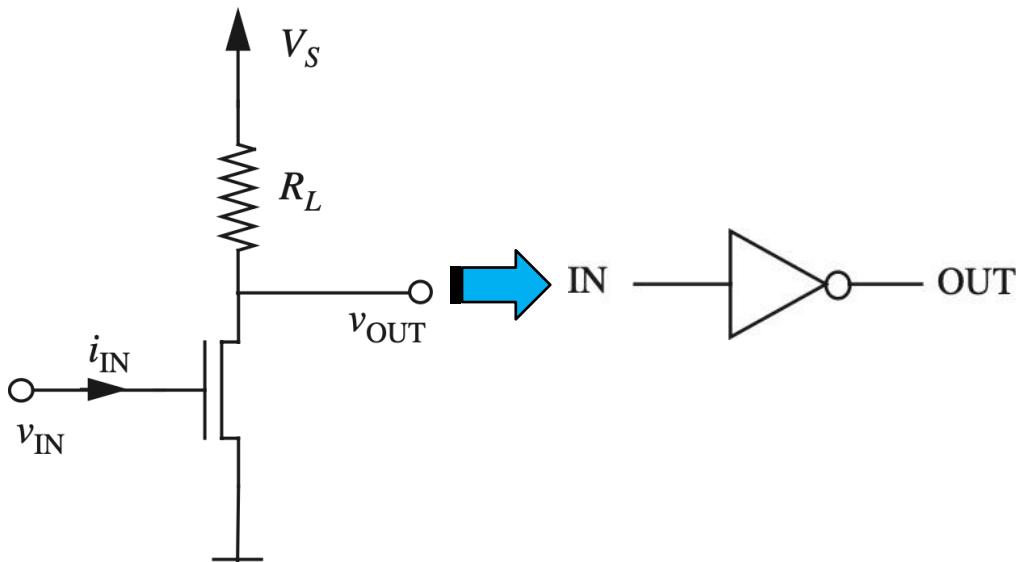- **Reminder:** VTC is a graph where x –axis = input voltage, y -axis = output voltage
- **Why?** Design logic gates to follow a given static discipline




When $v_{IN} < V_T$ (Logical 0) $v_{OUT} = V_S = 5\text{ V}$ (Logical 1)

 When $v_{IN} \geq V_T$ (Logical 1) $v_{OUT} = 0\text{ V}$ (Logical 0)




VTC of NAND gate

 
- We only have one x –axis, but two inputs
- **Solution:** Draw two VTC, one considering $V_A = 0$ one considering $V_A = 1$



When $V_A = 0$

 

When $V_A = 1$

 


Homework: Find VTC for NOR gate

Outline

- Constructing a *real* MOSFET – n/p-channel
- **Operation of an MOSFET-**
 1. Cut-Off
 2. Saturation
 3. Triode Mode
- Output Characteristics
- PWL Model and Non-ideal Analysis: **SR model**
- Real MOSFET equations
- Introduction to Static analysis



Construction of Real MOSFET

 

Top view of several n-channel MOSFETs fabricated on a chip. The square MOSFETs in the center of the photograph have a width and length of 100 μm . (Photograph Courtesy of Maxim Integrated Products.)


Real MOSFET – Enhancement Type

Device Structure (*n*-channel MOSFET)

  


n-channel MOSFET (NMOS) Physical Structure

Enhancement Type

 


NMOS in Equilibrium

 

When the transistor is left alone, some electrons from the n-type wells diffuse into the p-type material to fill holes.

This creates negative ions in the p-type material and positive ions are left behind in the n-type material.


NMOS in Cutoff

 

When a small, positive V_{GS} is applied, holes “move away” from the gate.

Electrons from complete atoms elsewhere in the p-type material move to fill holes near the gate instead.


NMOS Transistor channel

 

When V_{GS} is larger than a **threshold** voltage $V_{TH(n)}$, the attraction to the gate is so great that free electrons collect there.

The applied V_{GS} creates an **induced n-type channel** under the gate (an area with free electrons).



NMOS Transistor Drain Current

 


When a positive V_{DS} is applied, the free electrons flow from the source to the drain. (Positive current flows from drain to source).

The amount of current depends on V_{DS} , as well as the number of electrons in the channel, channel dimensions, and material.

NMOS Transistor Circuit symbol

  


NMOS I-V Characteristic

 

- Since the transistor is a 3-terminal device, there is no single I-V characteristic.
- Note that because of the insulator, $I_G = 0$ A.
- We typically define the MOS I-V characteristic as I_D vs. V_{DS} for a fixed V_{GS} .
- The I-V characteristic changes as V_{GS} changes.

NMOS I-V Characteristic

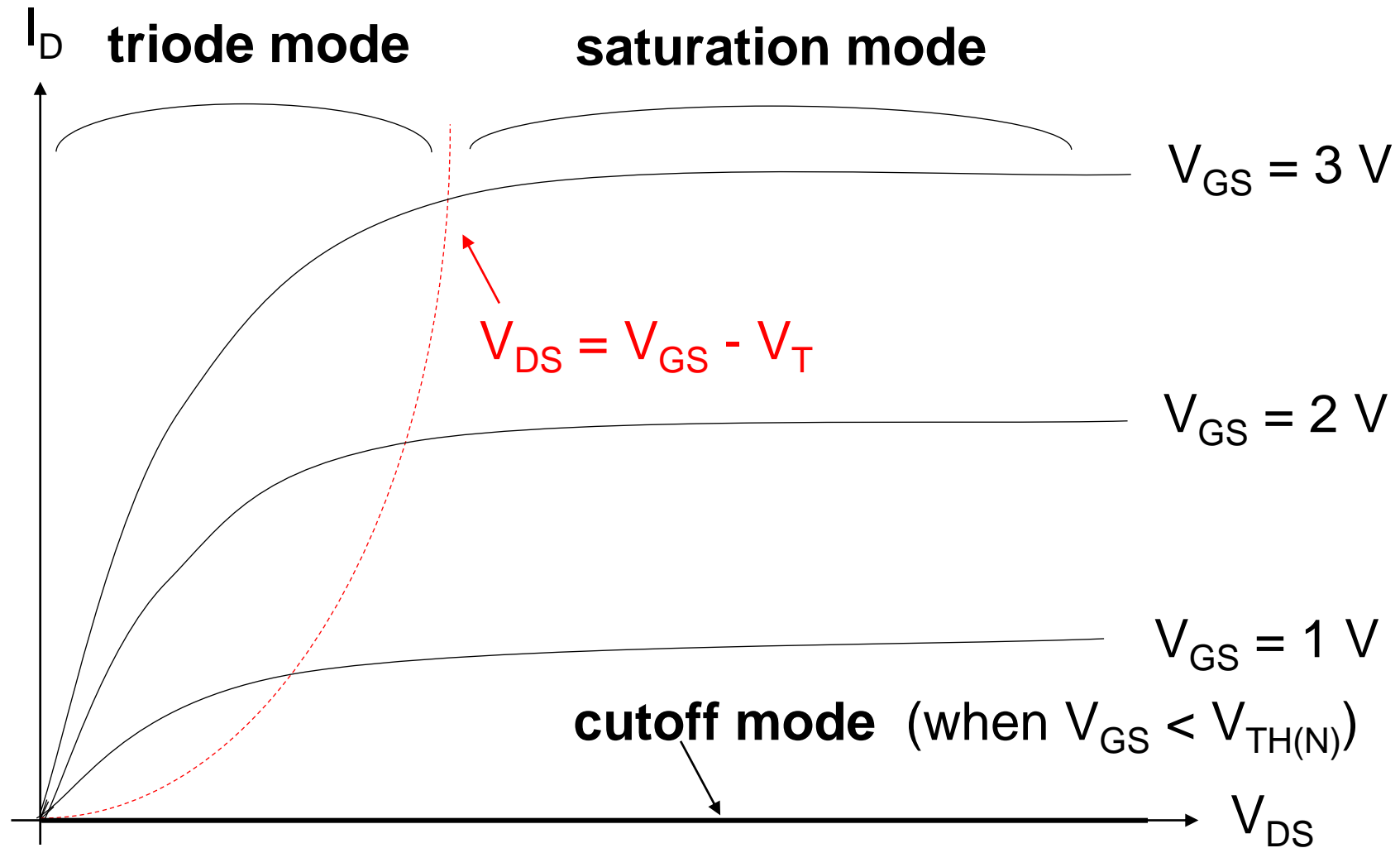

Modes of Operation

- For small values of V_{GS} , $V_{GS} \leq V_{TH(n)}$, the n-type channel is not formed. No current flows. This is **cutoff mode**.
- When $V_{GS} > V_{TH(n)}$, current I_D may flow from drain to source, and the following modes of current flow are possible.
 - The mode of current flow depends on the propelling voltage, V_{DS} , and the channel-inducing voltage, $V_{GS} - V_{TH(n)}$.
 - When $V_{DS} < V_{GS} - V_{TH(n)}$, current is starting to flow. I_D increases rapidly with increased V_{DS} . This is **triode mode**.
 - When $V_{DS} \geq V_{GS} - V_{TH(n)}$, current is reaching its maximum value. I_D does not increase much with increased V_{DS} . This is called **saturation mode**.

Water Tap Analogy

Imagine the water tap on your kitchen sink.

- To make water flow, the water supply has to be connected to the water tap. This establishes a path for water to flow.
- Setting V_{GS} above the threshold voltage is like connecting the water supply.
- **Cutoff = water supply disconnected (no path for current flow)**
- Setting V_{GS} to a larger value is like connecting a high-pressure water supply—more flow can potentially occur.

Water Tap Analogy

- The water tap itself is used to adjust water flow. You can turn the flow up and down.
- V_{DS} is like the water tap. It controls the amount of flow.
- There is, of course, a saturation point. If you keep turning the water tap control, eventually you won't get any more flow.
- **Triode = water tap in “normal range”, controls flow**
- **Saturation = water tap turned up to (or past) point for maximum flow**

NMOS Equations

Cutoff Mode

Occurs when $v_{GS} < V_T$

$$I_D = 0$$

$v_{GS} - V_T = V_{OV}$: Overdrive Voltage

Triode Mode

Occurs when $v_{GS} \geq V_T$ and $v_{DS} < v_{GS} - V_T$

$$I_{DS} = k'_n \frac{W}{L} \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$

V_{OV}
Indicates the available excess voltage at **gate** after forming the n-channel.


Saturation Mode

Occurs when $v_{GS} > V_T$ and $v_{DS} \geq v_{GS} - V_T$

$$I_{DS} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_T)^2$$

V_T
The minimum voltage necessary at the **gate** terminal to form a channel.

Real MOSFET

 

$$k_n = k'_n \frac{W}{L}$$

MOSFET transconductance



v_{GS} : Gate Voltage
 v_{DS} : Drain to Source Voltage
 V_T : Threshold Voltage
 $V_{OV} = v_{GS} - V_T$: Overdrive voltage

NMOS Triode Mode

Occurs when $v_{GS} \geq V_T$ and $v_{DS} < v_{GS} - V_T$

$$I_{DS} = k_n \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$
  
$$\begin{aligned} I_{DS} &\propto k'_n \\ I_{DS} &\propto \frac{W}{L} \\ I_{DS} &\propto (V_{OV} - \frac{1}{2} v_{DS}) \end{aligned}$$



Overdrive Voltage is defined as:

$$V_{OV} = v_{GS} - V_T$$

In triode mode, average voltage across channel is actually:


$$(V_{OV} - \frac{1}{2} v_{DS})$$

NMOS Triode Mode

$$I_{DS} = k'_n \frac{W}{L} \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$

$$I_{DS} = \frac{1}{R_{ON}} v_{DS}$$
 
$$\begin{aligned} R_{ON} &= \frac{1}{k'_n \frac{W}{L} (v_{GS} - V_T - \frac{1}{2} v_{DS})} \\ &= \frac{1}{k_n (V_{OV} - \frac{1}{2} v_{DS})} \end{aligned}$$





NMOS Saturation mode

Occurs when $v_{GS} > V_T$ and $v_{DS} \geq v_{GS} - V_T$

$$I_{DS} = \frac{1}{2} k_n (v_{GS} - V_T)^2 = \frac{1}{2} k_n V_{OV}^2$$
  
$$\begin{aligned} I_{DS} &\propto k'_n \\ I_{DS} &\propto \frac{W}{L} \end{aligned}$$




Overdrive Voltage is defined as:

$$V_{OV} = v_{GS} - V_T$$


In **Saturation** mode, average voltage across channel fixed at:

$$\frac{1}{2} V_{OV}$$

n-channel MOSFET - Summary

 


No channel, open ckt

 

Cut off mode


G – Gate:
S – Source:
D – Drain:

 

The created **channel**
will have some R
-> SR model

Trigger terminal
Charge carrier reservoir
Charge carrier sink

 
Small v_{DS} : Triode Mode
Large v_{DS} : Saturation Mode



Solving Circuits with MOSFET


- Use **Method of Assumed State!**
- Three steps:
 - **Assume:** One of the modes (Cutoff, Triode, Saturation)
 - **Solve:** Use corresponding equation and KCL+KVL
 - **Verify:** Check if the conditions of V_{DS} and V_{GS} are satisfied. If not, repeat.
- Might need to solve quadratic equation ($ax^2 + bx + c = 0$).
- If we get two roots, choose the one that's *favorable* to your assumption

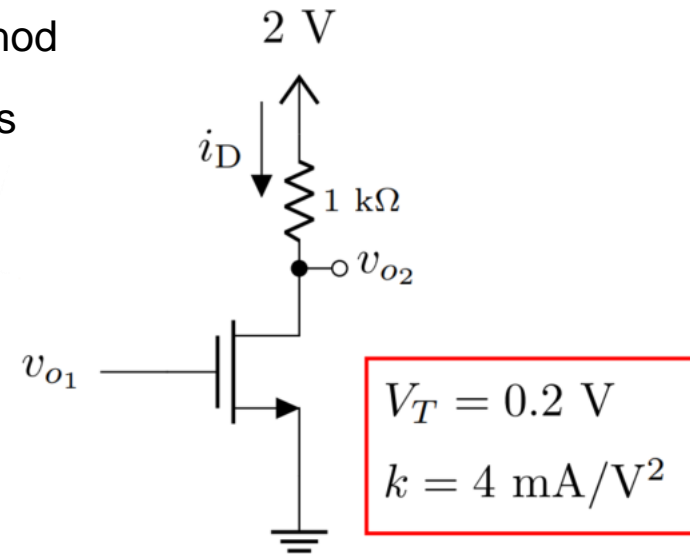Analyze the circuit to find i_D and v_{o2} using the Method of Assumed State. Here, the input of the MOSFET is $v_{o1} = 1\text{ V}$. You must validate your assumptions.




- Design the circuit, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_T = 0.7 \text{ V}$, $k = 3.2 \text{ mA/V}^2$.

What is the mode of this transistor?

 


- For the circuit, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_T = 0.5$ V, $k'_n = \mu_n C_{OX} = 0.4$ mA/V², $\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}$
 
$$k_n = k'_n \frac{W}{L} = 1.6 \text{ mA/V}^2$$







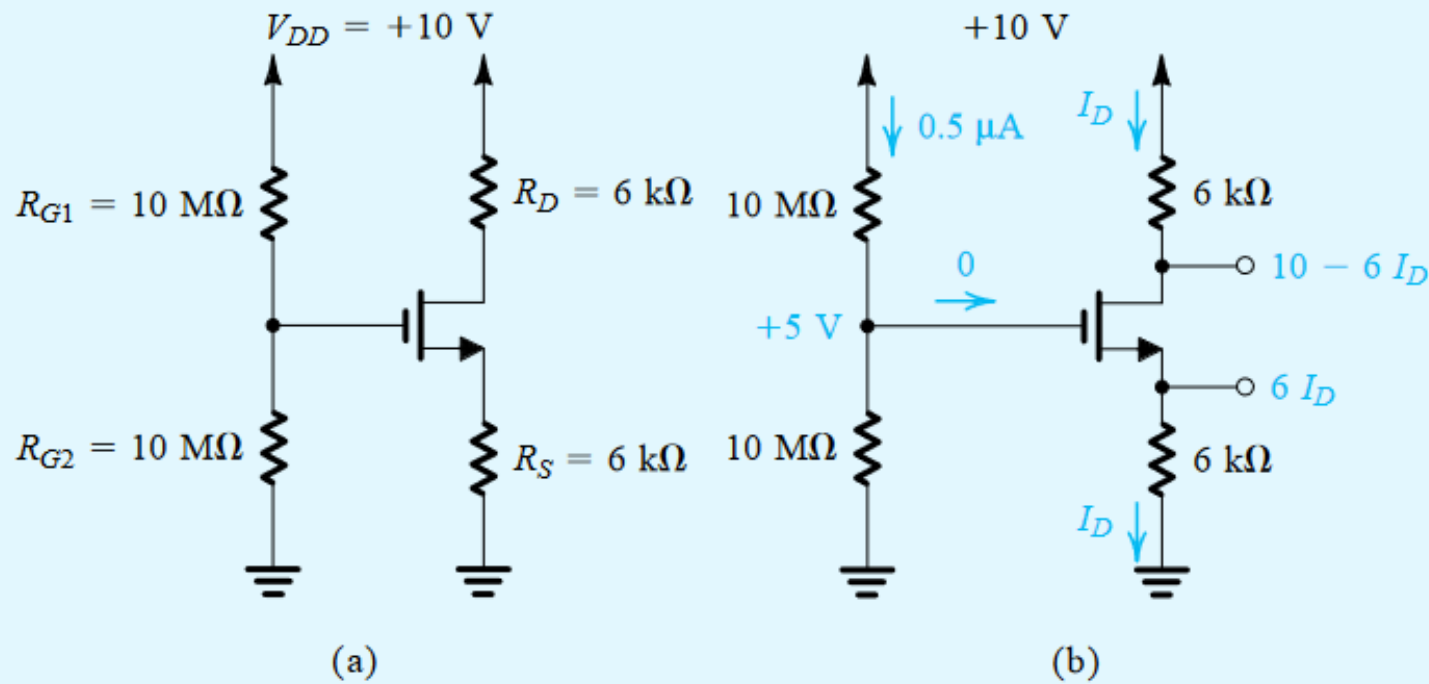Analyze the circuit shown in Fig. 5.24(a) to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1 \text{ V}$ and $k'_n(W/L) = 1 \text{ mA/V}^2$. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$).



n-channel MOSFET - Summary

SR Model:

    


$$R_{ON} = \frac{1}{k_n(V_{OV} - \frac{1}{2}v_{DS})}$$

V_{OV}
Indicates the available
excess voltage at **gate** after
forming the n-channel.

- SR model is a better approximation than S model.
- **Triode Mode exists until:** $v_{DS} \leq (v_{GS} - V_T)$

SR Model - Inverter

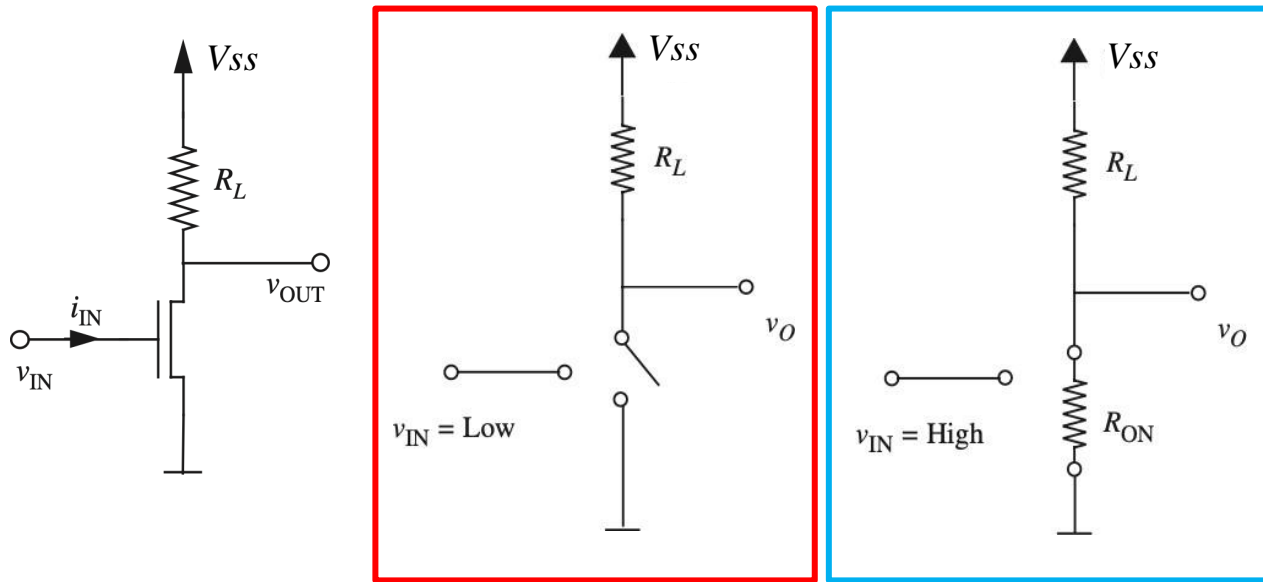

$$v_{o,HI} = V_{SS}$$

$$v_{o,LO} = \frac{R_{ON}}{R_{ON} + R_L} V_{SS}$$

For example, If


$$V_{SS} = 5 \text{ V},$$

$$R_{ON} = 1 \text{ k}\Omega,$$



$$R_L = 14 \text{ k}\Omega$$

$$\frac{R_{ON}}{R_{ON} + R_L} V_{SS} = 0.33 \text{ V}$$
 
$$\frac{V_{SS} R_{ON}}{R_{ON} + R_L} = 0.33 \text{ V}$$



Design of logic gates

  

Expected

IN	B	OUT
Low ($V_{IN} < V_T$)	High (5V)	Low ($V_{OUT} = V_{OUT,Low}$)
High ($V_{IN} > V_T$)	Low ($V_{OUT,Low}$)	High (5V)

Actual

IN	B	OUT
Low ($V_{IN} < V_T$)	High (5V)	Low ($V_{OUT} = V_{OUT,Low}$)
High ($V_{IN} > V_T$)	Low ($V_{OUT,Low} = 0.5 \text{ V} \neq V_T$)	Low ($V_{OUT,Low} = 0.5 \text{ V}$)

$$V_T = 0.4 \text{ V}$$

$$V_{SS} = 5 \text{ V}, \quad R_{ON} = 1 \text{ k}\Omega, \quad R_L = 9 \text{ k}\Omega$$

$$V_{OUT,HI} = V_{SS}$$

$$V_{OUT,LOW} = \frac{R_{ON}}{R_{ON} + R_L} V_S = 5 \cdot \frac{1}{1 + 9} = 0.5 \text{ V} \neq V_T$$

Therefore, need to design logic gates properly such that

$$\frac{R_{ON}}{R_{ON} + R_L} V_{SS} < V_T$$

Design of logic gates - Example

Assume the following values for the inverter circuit parameters: $V_{SS} = 5\text{ V}$, $V_T = 1\text{ V}$, and $R_L = 10\text{ k}\Omega$.

Assume, further, that $\frac{1}{k'_n V_{OV}} = 5$ for the MOSFET. Determine a $(\frac{W}{L})$ sizing for the MOSFET so that the inverter gate output for a logical 0 is able to switch OFF the MOSFET of another inverter.

Solution:

[Assume $R_{ON} = \frac{1}{k'_n V_{OV}}$ if v_{DS} is not given or low]

$$V_{SS} \cdot \frac{R_{ON}}{R_{ON} + R_L} < V_T$$

$$\Rightarrow 5 \frac{R_{ON}}{R_{ON} + R_L} < 1$$

$$\Rightarrow 5R_{ON} < R_{ON} + 10$$



$$\Rightarrow R_{ON} < \frac{10}{4}\text{ k}\Omega = 2.5\text{ k}\Omega$$

$$\text{Now, } R_{ON} = \frac{1}{k'_n V_{OV}} = \frac{1}{k'_n \frac{W}{L} V_{OV}} = \frac{1}{5} \times \frac{1}{W/L}$$

$$\text{Hence } \frac{5}{W/L} < 2.5$$

$$\Rightarrow \frac{W}{L} > \frac{5}{2.5} = 2$$

Review – MOSFET

  

Control = $V_{GS} = V_G - V_S$ controls the IV between drain-source (I_{DS} vs V_{DS})




Threshold voltage = V_T , minimum voltage required to create the channel

Models




1. **S Mode:** Assumes an ideal channel with zero resistance
2. **SR Model:** Assumes finite channel resistance, R_{ON} , depends on $V_{GS} - V_T = V_{OV}$

MOSFET Linear Models

S Model

   




SR Model

   

$$R_{ON} = \frac{1}{k'_n \frac{W}{L} (v_{GS} - V_T - \frac{1}{2} v_{DS})}$$


Construction of Real MOSFET

Simplified cross section
and 3D view

   

No channel, open ckt

$$V_{12} = 0V$$



 


$$V_{12} > V_{th}$$


Channel created
Will have some R
-> SR model

Real MOSFET

   - For small V_{DS} , uniform channel, hence fixed R_{ON} therefore SR model valid.
- As V_{DS} is increased, channel becomes tapered cause $V_{GD} \downarrow$. Resistance \uparrow , slope \downarrow .
- This mode is called the **triode mode**. Condition: $V_{DS} < V_{OV}$




Real MOSFET

 

- When $V_{DS} = V_{OV}$, channel pinches off.
- Increasing V_{DS} further have no effect on channel shape. Hence, current saturates
- This mode is called the **saturation mode**. Condition: $V_{DS} \geq V_{OV}$
- Behaves like a current source (constant current) that depends on V_{OV} ,

IV Characteristics of Real MOSFET

 


Mode	Condition	Equation
Cutoff	$V_{GS} < V_T$	$I_D = 0$
Triode	$V_{GS} \geq V_T$ $V_{DS} < V_{OV}$	$I_D = k[V_{OV}V_{DS} - \frac{1}{2}V_{DS}^2]$
Saturation	$V_{GS} \geq V_T$ $V_{DS} \geq V_{OV}$	$I_D = \frac{k}{2}V_{OV}^2$

$$V_{GS} - V_T = V_{OV}$$

$$k_n = \frac{k'_n W}{L}$$


Digital Representation

Suppose you want to send 010110

 

- Single value based representation fails in the presence of noise
- Better approach – threshold-based system
- Simplest: **Logical 0** = $V < V_T$ **Logical 1** = $V > V_T$


Static Discipline

 

- Specification for “all” digital devices
- Requires devices to adhere to common representation to ensure that **valid input produces valid output**
- This means, if
 - Sender sends “0” $\xrightarrow[\text{Channel}]{\text{noise}}$ Receiver interprets as “0”
 - Sender sends “1” $\xrightarrow[\text{Channel}]{\text{noise}}$ Receiver interprets as “1”


Static Discipline

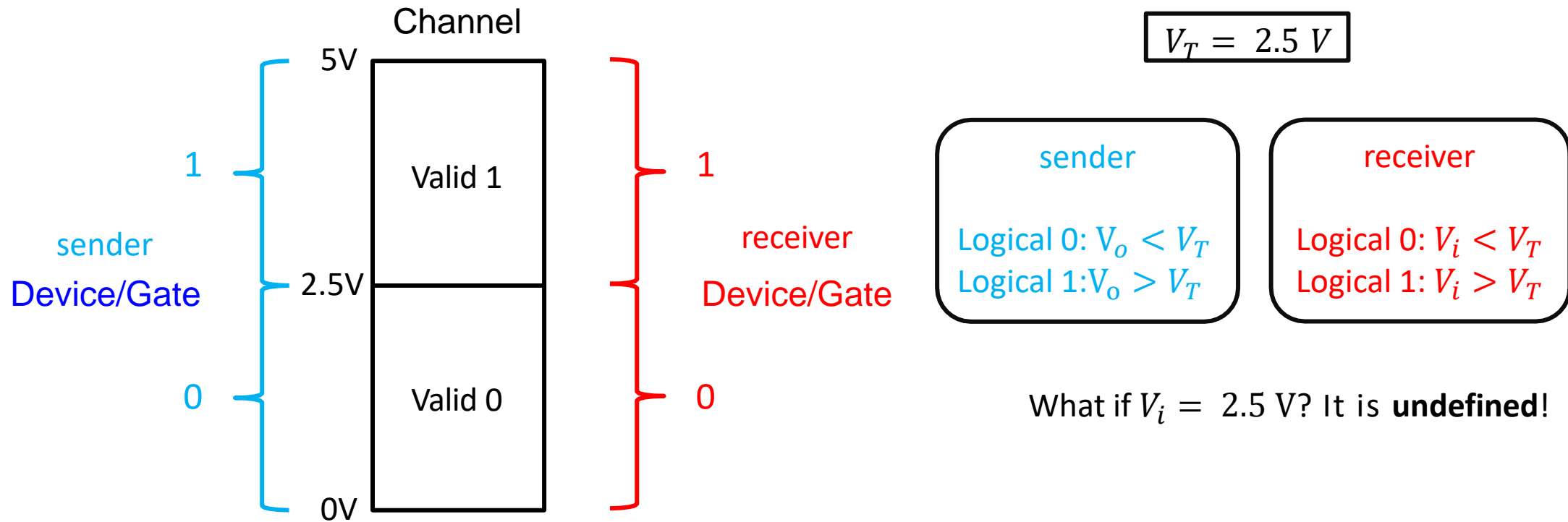Naïve approach: Single threshold-based system



Static Discipline

Double threshold based system

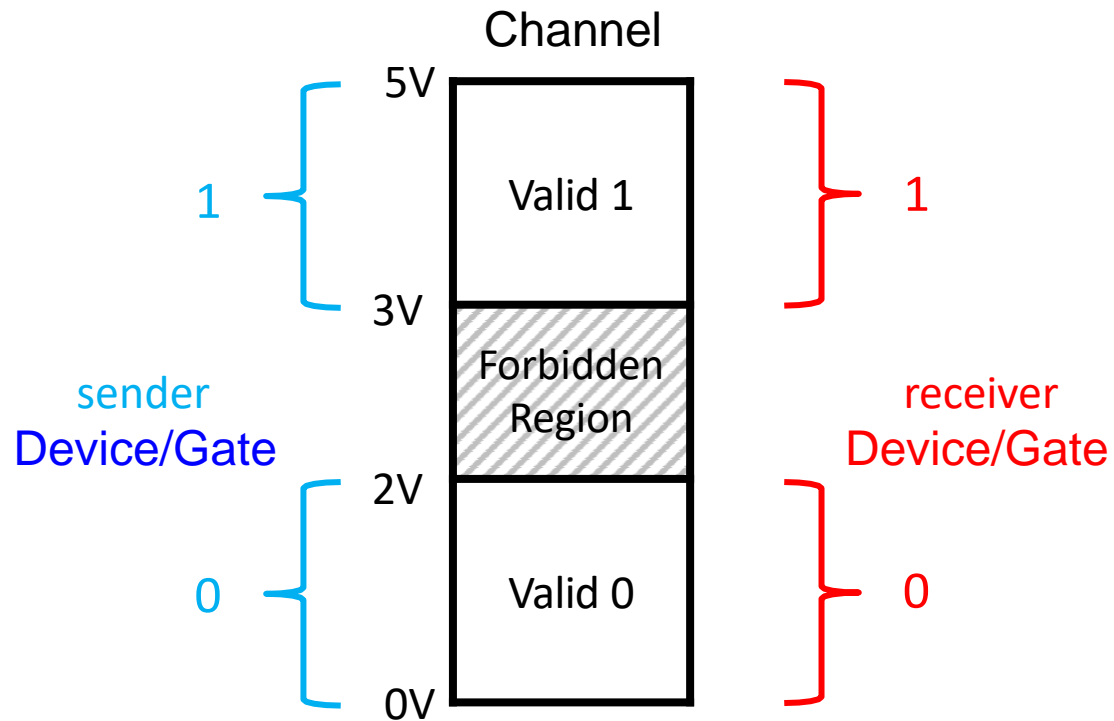

V_H = High voltage threshold = 3V

V_L = High voltage threshold = 2V

sender

Logical 0: $V_o < V_L$
Logical 1: $V_o > V_H$

receiver

Logical 0: $V_i < V_L$
Logical 1: $V_i > V_H$


What if $V_o = 1.9V$ and channel noise is $0.5V$?

$V_i = 1.9V + 0.5V = 2.4V = \text{invalid}$

→ valid output producing invalid input,
i.e., no margin for noise

Static Discipline

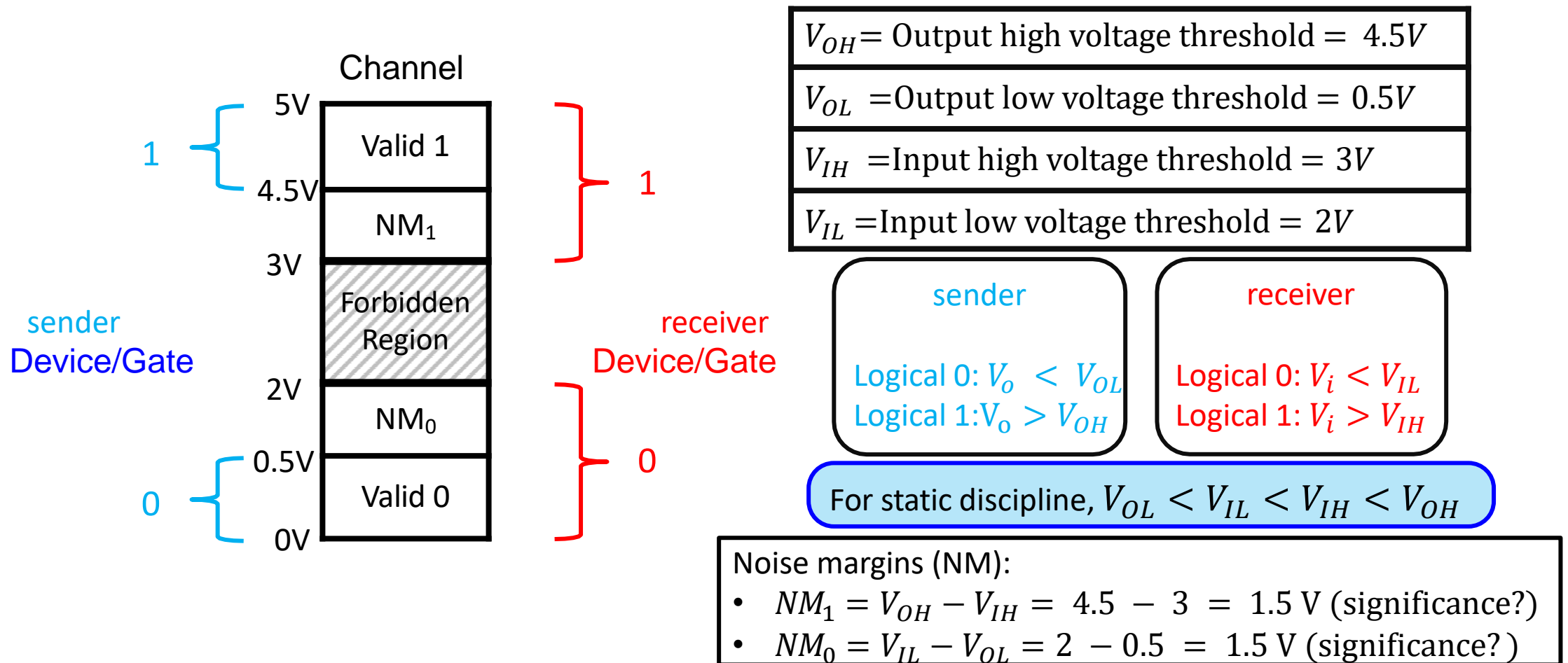Four threshold-based system → Tighter restriction on sender (**output**)





Static Discipline

Four threshold-based system → Tighter restriction on sender (**output**)

V_{OH} : The lowest output voltage value that a digital device **can produce** when it outputs a logical 1.

  V_{OL} : The highest output voltage value that a digital device **can produce** when it outputs a logical 0.




V_{IH} : The *lowest input voltage* value that a digital device **must recognize** as a logical 1.

V_{IL} : The *highest input voltage* value that a digital device **must recognize** as a logical 0.


Static Discipline and VTC graph

 Four threshold-based system → Tighter restriction on sender (**output**)



During high to low or low to high **transition**:

Higher Slope in VTC graph

 

While **not** in **transition**; at logical **HIGH** or **LOW** voltage level:

Smaller Slope in VTC graph

Static Discipline and VTC graph

