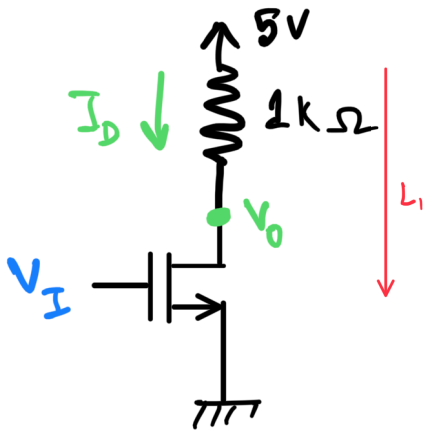


Example 1



The MOSFET is specified as $V_T = 1V$ and $k = 0.5 \text{ mA/V}^2$. Find I_D and V_O for $V_I = 2V$.

Solution:

Step 1: Assume the MOSFET in **saturation**

Step 2: $I_D = \frac{k}{2} V_{OV}^2$ Here, $V_{GS} = V_G - V_S = V_G - 0 = V_G = V_I = 2V$
Therefore, $V_{OV} = V_{GS} - V_T = 2 - 1 = 1V$

$$\therefore I_D = \frac{0.5}{2} (1)^2 = 0.25 \text{ mA}$$

Again, $V_{DS} = V_D - V_S = V_D - 0 = V_D = V_O$

KVL along L_1 : $I_D \times 1k\Omega + V_O = 5 - 0 \Rightarrow V_O = 5 - I_D \times 1k\Omega$


$$\Rightarrow V_O = 5 - 0.25 \times 1 = 4.75 \text{ V} = V_{DS}$$

Step 3: $V_{GS} = 2V > V_T$ ✓ Therefore, **assumption correct!**

$V_{DS} = 1V > V_{OV}$ ✓

Correct ans: $I_D = 0.25 \text{ mA}$, $V_O = 4.75 \text{ V}$

Example 2

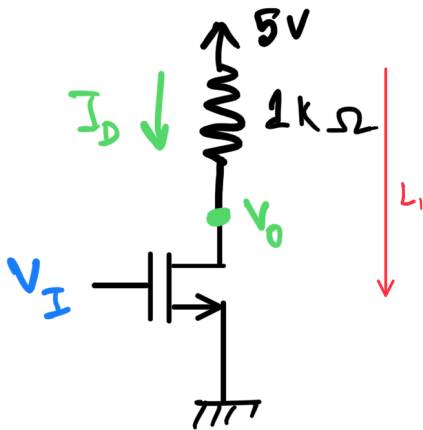

The MOSFET is specified as $V_T = 1V$ and $k = 0.5 \text{ mA/V}^2$. Find I_D and V_O for $V_I = 5V$.

Solution:

Step 1: Assume the MOSFET in **saturation**

Step 2: $I_D = \frac{k}{2} V_{OV}^2$ Here, $V_{GS} = V_G - V_S = V_G - 0 = V_G = V_I = 5V$
Therefore, $V_{OV} = V_{GS} - V_T = 5 - 1 = 4V$

$$\therefore I_D = \frac{0.5}{2} (4)^2 = 4 \text{ mA}$$

Again, $V_{DS} = V_D - V_S = V_D - 0 = V_D = V_O$


KVL along L_1 : $I_D \times 1k\Omega + V_O = 5 - 0 \Rightarrow V_O = 5 - I_D \times 1k\Omega$

$$\Rightarrow V_O = 5 - 4 \times 1 = 1 \text{ V} = V_{DS}$$

Step 3: $V_{GS} = 5V > V_T$ ✓ Therefore, **assumption wrong!**

$$V_{DS} = 1V \not> V_{OV} \times$$

Example 2

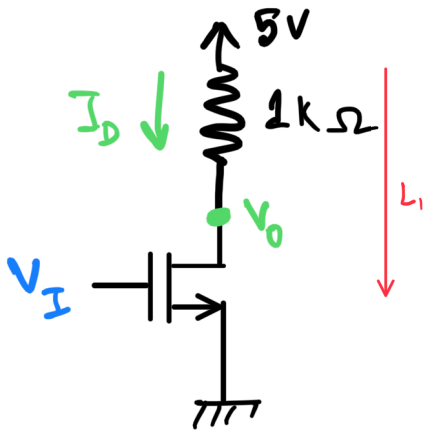

The MOSFET is specified as $V_T = 1V$ and $k = 0.5 \text{ mA/V}^2$. Find I_D and V_O for $V_I = 5V$.

Repeat:

Step 1: Assume the MOSFET in **triode**

Step 2: $I_D = k[V_{OV}V_{DS} - \frac{1}{2}V_{DS}^2]$

Here, $V_{GS} = V_G - V_S = V_G - 0 = V_G = V_I = 5V$

Therefore, $V_{OV} = V_{GS} - V_T = 5 - 1 = 4V$

Again, $V_{DS} = V_D - V_S = V_D - 0 = V_D = V_O$. Assuming $V_{DS} = x$

KVL along L_1 : $I_D \times 1k\Omega + V_O = 5 - 0 \Rightarrow I_D = \frac{5 - V_{DS}}{1} = 5 - x$

$\therefore I_D = 0.5 \left[4 \times V_{DS} - \frac{1}{2} V_{DS}^2 \right] \Rightarrow (5 - x) = 0.5 \left[4x - \frac{1}{2} x^2 \right]$

$\Rightarrow 5 - x = 2x - 0.25x^2 \Rightarrow 0.25x^2 - 3x + 5 = 0$

Solving, $x = 2V, x = 10V$

Since $V_{DS} = x$ is small in triode, smaller value of x is favorable


Therefore, $V_O = V_{DS} = x = 2V$, and $I_D = 5 - x = 3 \text{ mA}$

Step 3: $V_{GS} = 5V > V_T$ ✓ Therefore, **assumption correct!**

$V_{DS} = 2V < V_{OV}$ ✓

Correct ans: $I_D = 3 \text{ mA}, V_O = 2 \text{ V}$

Example 3

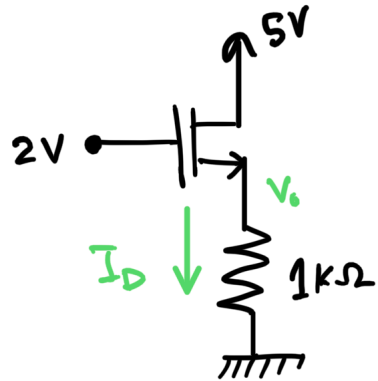

The MOSFET is specified as $V_T = 1V$ and $k = 4 \text{ mA/V}^2$.

Find I_D and V_O

Solution:

Step 1: Assume the MOSFET in **saturation**

Step 2: $I_D = \frac{k}{2} V_{ov}^2$

Let's assume $V_O = V_S = x$

Here, $V_{GS} = V_G - V_S = V_G - V_O = 2 - x$

Therefore, $V_{OV} = V_{GS} - V_T = (2 - x) - 1 = 1 - x$

Again, $V_{DS} = V_D - V_S = V_D - V_O = 5 - x$

Ohm's law for the resistor: $I_D = \frac{V_O - 0}{1k\Omega} = x$

$$\therefore x = \frac{4}{2} (1 - x)^2 \Rightarrow x = 2(1 - 2x + x^2) \Rightarrow x = 2 - 4x + 2x^2$$

$$\Rightarrow 2x^2 - 5x + 2 = 0$$

Solving, $x = 0.5, \cancel{x = 2V}$

Since $V_{DS} = 5 - x$ is large in saturation smaller value of x is favorable

$$\therefore V_O = V_S = x = 0.5V, I_D = x = 0.5 \text{ mA},$$

$$V_{DS} = 5 - x = 4.5V, V_{GS} = 2 - x = 1.5V, \text{ and } V_{OV} = 1 - x = 0.5V$$

Step 3: $V_{GS} = 1.5V > V_T$ ✓ Therefore, **assumption correct!**

$V_{DS} = 4.5V > V_{OV}$ ✓ **Correct ans: $I_D = 0.5 \text{ mA}, V_O = 0.5 V$**

Practice


Question 4 [CO1, CO4]

10

Analyze the following circuit to find the values of I_D and V_{DS} **using** the Method of Assumed State. You must **validate** your assumptions.

[7 + 3]

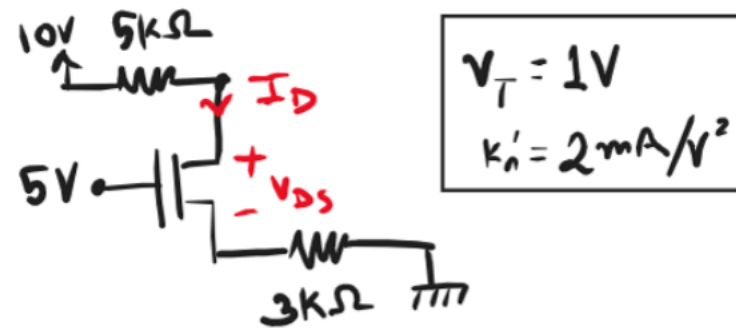Hint: Use I_D as unknown x . Use Ohm's law to represent V_D and V_S in terms of x .



Hint Explanation

Assume $I_D = x$. For $5k\Omega$: $I_D = \frac{10 - V_D}{5} \Rightarrow V_D = 10 - 5 \times I_D = 10 - 5x$.

For $3k\Omega$: $I_D = \frac{V_S - 0}{3} \Rightarrow V_S = 3 \times I_D = 3x$.

Therefore, $V_{GS} = V_G - V_S = 5 - 3x$, and $V_{OV} = V_{GS} - V_T = (5 - 3x) - 1$

Also, $V_{DS} = V_D - V_S = (10 - 5x) - 3x = 10 - 8x$

Now if you assume saturation:

$$I_D = \frac{k}{2} V_{OV}^2 \Rightarrow x = \frac{2}{2} (4 - 3x)^2$$

And if you assume triode:

$$I_D = k[V_{OV}V_{DS} - \frac{1}{2}V_{DS}^2]$$

$$\Rightarrow x = 2[(4 - 3x)(10 - 8x) - 0.5 \times (10 - 8x)^2]$$

Solve for x , take the _____ root