

CSE251: Electronic Devices and Circuits

Lecture: MOSFET 2

Prepared By:

Shadman Shahid (SHD)


Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: ext.shadman.shahid@bracu.ac.bd

Outline

- Constructing a *real* MOSFET – n/p-channel
- **Operation of an MOSFET-**
 1. Cut-Off
 2. Saturation
 3. Triode Mode
- Output Characteristics
- PWL Model and Non-ideal Analysis: **SR model**
- Real MOSFET equations
- Introduction to Static analysis



Construction of Real MOSFET

 

Top view of several n-channel MOSFETs fabricated on a chip. The square MOSFETs in the center of the photograph have a width and length of 100 μm . (Photograph Courtesy of Maxim Integrated Products.)


Real MOSFET – Enhancement Type

Device Structure (*n*-channel MOSFET)

  


n-channel MOSFET (NMOS) Physical Structure

Enhancement Type

 


NMOS in Equilibrium

 

When the transistor is left alone, some electrons from the n-type wells diffuse into the p-type material to fill holes.

This creates negative ions in the p-type material and positive ions are left behind in the n-type material.


NMOS in Cutoff

 

When a small, positive V_{GS} is applied, holes “move away” from the gate.

Electrons from complete atoms elsewhere in the p-type material move to fill holes near the gate instead.


NMOS Transistor channel

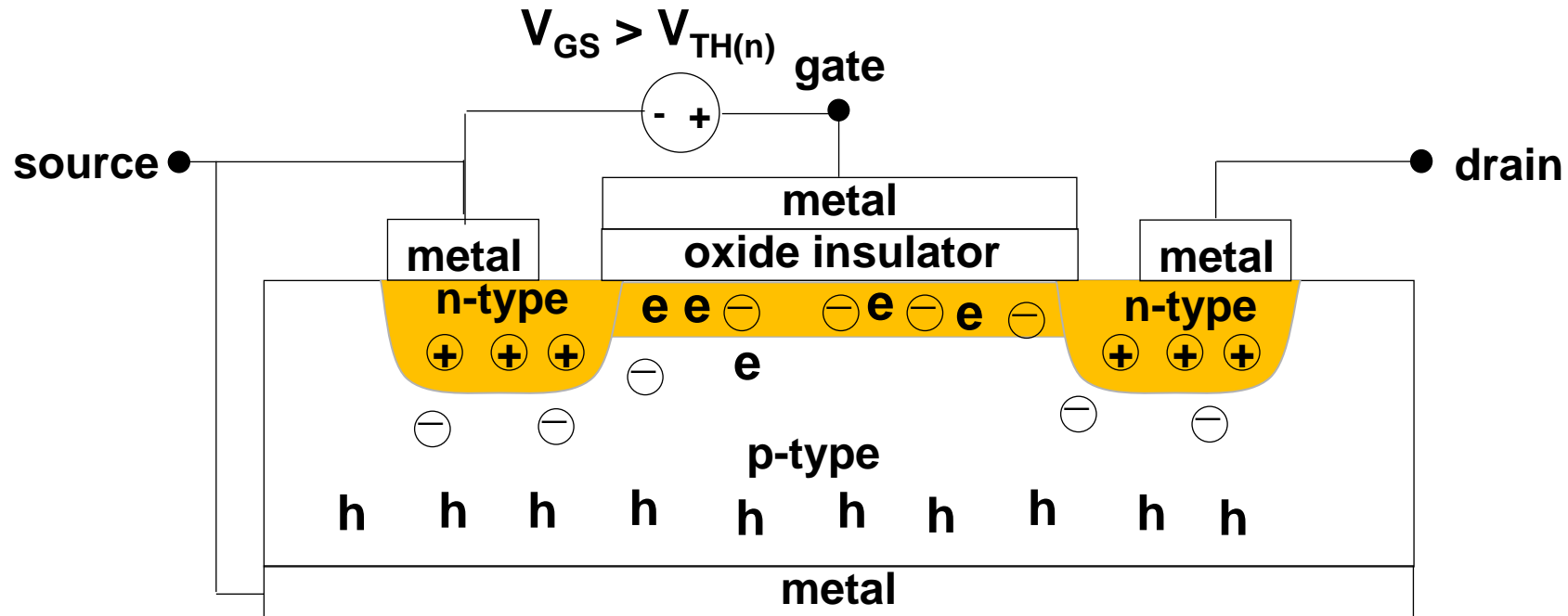

When V_{GS} is larger than a **threshold** voltage $V_{TH(n)}$, the attraction to the gate is so great that free electrons collect there.

The applied V_{GS} creates an **induced n-type channel** under the gate (an area with free electrons).



NMOS Transistor Drain Current

 


When a positive V_{DS} is applied, the free electrons flow from the source to the drain. (Positive current flows from drain to source).

The amount of current depends on V_{DS} , as well as the number of electrons in the channel, channel dimensions, and material.

NMOS Transistor Circuit symbol

  


NMOS I-V Characteristic

 

- Since the transistor is a 3-terminal device, there is no single I-V characteristic.
- Note that because of the insulator, $I_G = 0$ A.
- We typically define the MOS I-V characteristic as I_D vs. V_{DS} for a fixed V_{GS} .
- The I-V characteristic changes as V_{GS} changes.

NMOS I-V Characteristic

 

Modes of Operation

- For small values of V_{GS} , $V_{GS} \leq V_{TH(n)}$, the n-type channel is not formed. No current flows. This is **cutoff mode**.
- When $V_{GS} > V_{TH(n)}$, current I_D may flow from drain to source, and the following modes of current flow are possible.
 - The mode of current flow depends on the propelling voltage, V_{DS} , and the channel-inducing voltage, $V_{GS} - V_{TH(n)}$.
 - When $V_{DS} < V_{GS} - V_{TH(n)}$, current is starting to flow. I_D increases rapidly with increased V_{DS} . This is **triode mode**.
 - When $V_{DS} \geq V_{GS} - V_{TH(n)}$, current is reaching its maximum value. I_D does not increase much with increased V_{DS} . This is called **saturation mode**.

Water Tap Analogy

Imagine the water tap on your kitchen sink.

- To make water flow, the water supply has to be connected to the water tap. This establishes a path for water to flow.
- Setting V_{GS} above the threshold voltage is like connecting the water supply.
- **Cutoff = water supply disconnected (no path for current flow)**
- Setting V_{GS} to a larger value is like connecting a high-pressure water supply—more flow can potentially occur.

Water Tap Analogy

- The water tap itself is used to adjust water flow. You can turn the flow up and down.
- V_{DS} is like the water tap. It controls the amount of flow.
- There is, of course, a saturation point. If you keep turning the water tap control, eventually you won't get any more flow.
- **Triode = water tap in “normal range”, controls flow**
- **Saturation = water tap turned up to (or past) point for maximum flow**

NMOS Equations

Cutoff Mode

Occurs when $v_{GS} < V_T$

$$I_D = 0$$

$v_{GS} - V_T = V_{OV}$: Overdrive Voltage

Triode Mode

Occurs when $v_{GS} \geq V_T$ and $v_{DS} < v_{GS} - V_T$

$$I_{DS} = k'_n \frac{W}{L} \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$

V_{OV}
Indicates the available excess voltage at **gate** after forming the n-channel.


Saturation Mode

Occurs when $v_{GS} > V_T$ and $v_{DS} \geq v_{GS} - V_T$

$$I_{DS} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_T)^2$$

V_T
The minimum voltage necessary at the **gate** terminal to form a channel.

Real MOSFET

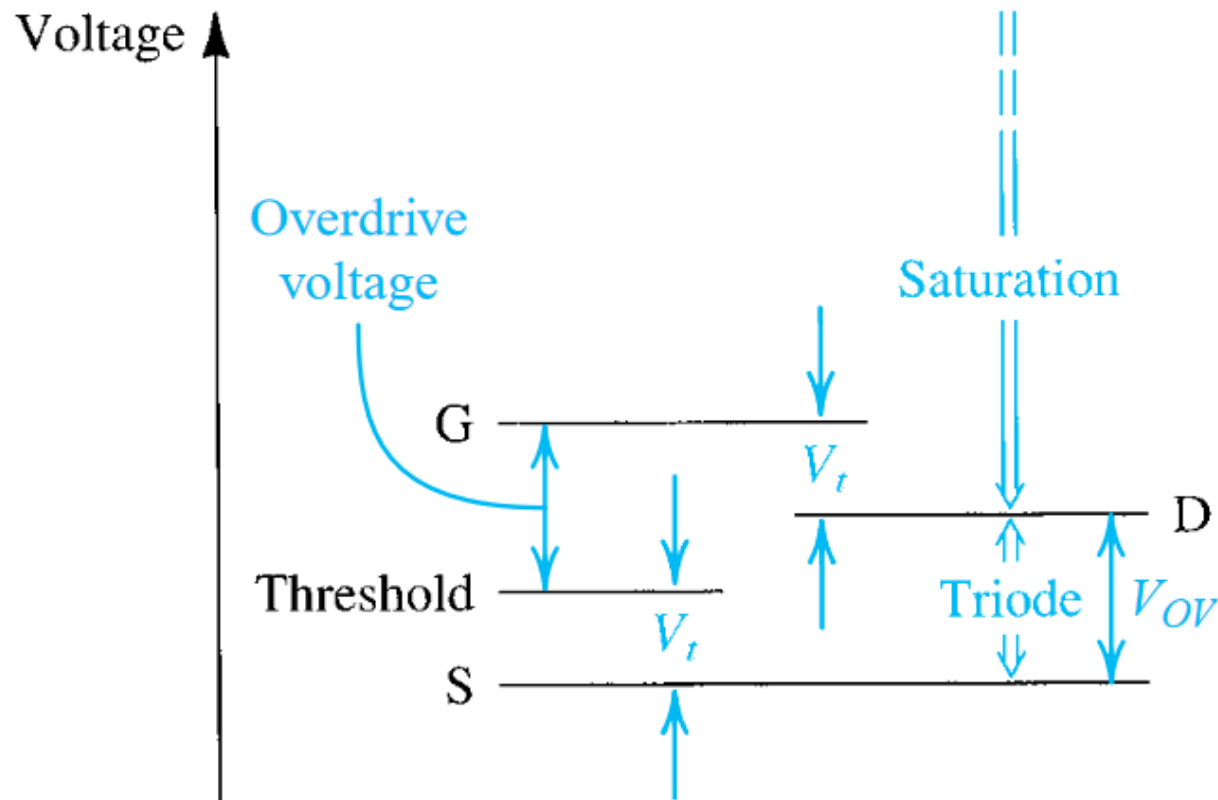

$$k_n = k'_n \frac{W}{L}$$

MOSFET transconductance



v_{GS} : Gate Voltage
 v_{DS} : Drain to Source Voltage
 V_T : Threshold Voltage
 $V_{OV} = v_{GS} - V_T$: Overdrive voltage

NMOS Triode Mode

Occurs when $v_{GS} \geq V_T$ and $v_{DS} < v_{GS} - V_T$

$$I_{DS} = k_n \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$
  
$$\begin{aligned} I_{DS} &\propto k'_n \\ I_{DS} &\propto \frac{W}{L} \\ I_{DS} &\propto (V_{OV} - \frac{1}{2} v_{DS}) \end{aligned}$$



Overdrive Voltage is defined as:

$$V_{OV} = v_{GS} - V_T$$

In triode mode, average voltage across channel is actually:


$$(V_{OV} - \frac{1}{2} v_{DS})$$

NMOS Triode Mode

$$I_{DS} = k'_n \frac{W}{L} \left(v_{GS} - V_T - \frac{1}{2} v_{DS} \right) v_{DS}$$

$$I_{DS} = \frac{1}{R_{ON}} v_{DS}$$
 
$$\begin{aligned} R_{ON} &= \frac{1}{k'_n \frac{W}{L} (v_{GS} - V_T - \frac{1}{2} v_{DS})} \\ &= \frac{1}{k_n (V_{OV} - \frac{1}{2} v_{DS})} \end{aligned}$$





NMOS Saturation mode

Occurs when $v_{GS} > V_T$ and $v_{DS} \geq v_{GS} - V_T$

$$I_{DS} = \frac{1}{2} k_n (v_{GS} - V_T)^2 = \frac{1}{2} k_n V_{OV}^2$$
  
$$\begin{aligned} I_{DS} &\propto k'_n \\ I_{DS} &\propto \frac{W}{L} \end{aligned}$$




Overdrive Voltage is defined as:

$$V_{OV} = v_{GS} - V_T$$


In **Saturation** mode, average voltage across channel fixed at:

$$\frac{1}{2} V_{OV}$$

n-channel MOSFET - Summary

 


No channel, open ckt

 

Cut off mode


G – Gate:
S – Source:
D – Drain:

 

The created **channel**
 will have some R
 -> SR model

Trigger terminal
 Charge carrier reservoir
 Charge carrier sink

 
Small v_{DS} : Triode Mode
Large v_{DS} : Saturation Mode



Solving Circuits with MOSFET


- Use **Method of Assumed State!**
- Three steps:
 - **Assume:** One of the modes (Cutoff, Triode, Saturation)
 - **Solve:** Use corresponding equation and KCL+KVL
 - **Verify:** Check if the conditions of V_{GS} and V_{DS} are satisfied. If not, repeat.
- Might need to solve quadratic equation ($ax^2 + bx + c = 0$).
- If we get two roots, choose the one that's *favorable* to your assumption

 Analyze the circuit to find i_D and v_{o2} using the Method of Assumed State. Here, the input of the MOSFET is $v_{o1} = 1\text{ V}$. You must validate your assumptions.




- Design the circuit, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_T = 0.7 \text{ V}$, $k = 3.2 \text{ mA/V}^2$.

What is the mode of this transistor?

 


- For the circuit, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_T = 0.5$ V, $k'_n = \mu_n C_{OX} = 0.4$ mA/V², $\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}$
 
$$k_n = k'_n \frac{W}{L} = 1.6 \text{ mA/V}^2$$







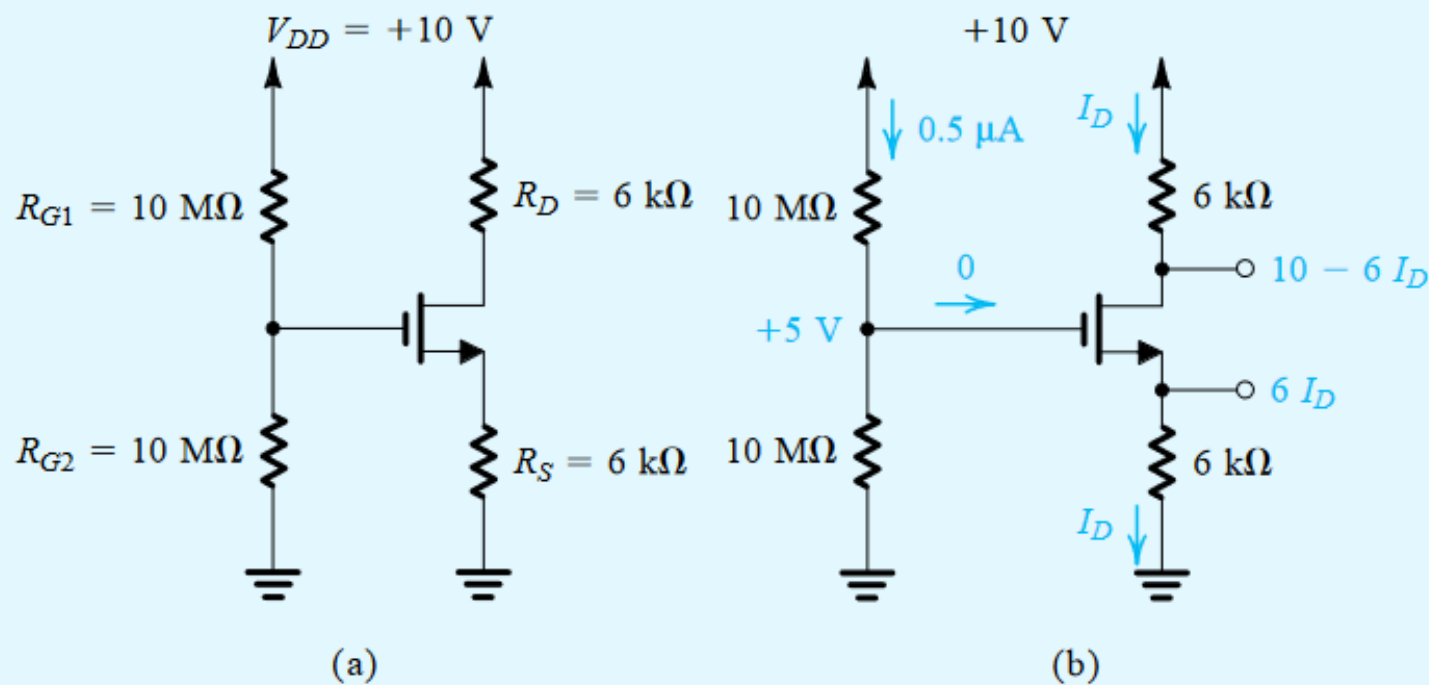Analyze the circuit shown in Fig. 5.24(a) to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1$ V and $k'_n(W/L) = 1$ mA/V². Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$).



n-channel MOSFET - Summary

SR Model:

    


$$R_{ON} = \frac{1}{k_n(V_{OV} - \frac{1}{2}v_{DS})}$$

V_{OV}
Indicates the available
excess voltage at **gate** after
forming the n-channel.

- SR model is a better approximation than S model.
- **Triode Mode exists until:** $v_{DS} \leq (v_{GS} - V_T)$

SR Model - Inverter

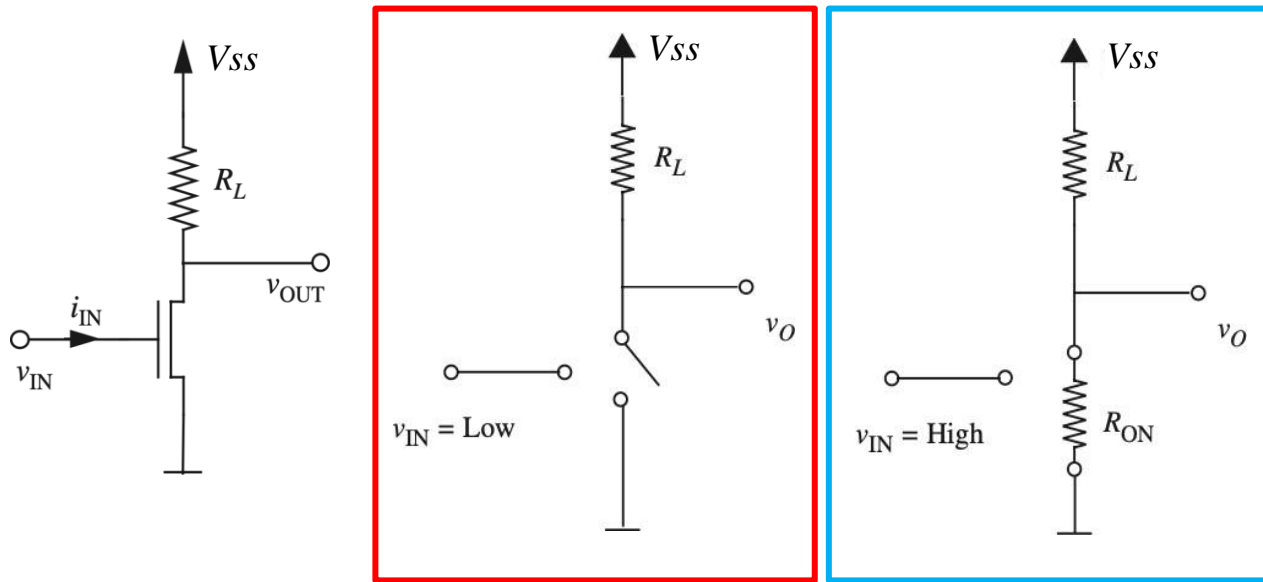

$$v_{o,HI} = V_{SS}$$

$$v_{o,LO} = \frac{R_{ON}}{R_{ON} + R_L} V_{SS}$$


For example, If

$$V_{SS} = 5 \text{ V},$$



$$R_{ON} = 1 \text{ k}\Omega,$$

$$R_L = 14 \text{ k}\Omega$$
 
$$\frac{R_{ON}}{R_{ON} + R_L} V_{SS} = 0.33 \text{ V}$$



Design of logic gates

  

Expected

$$V_T = 0.4 \text{ V}$$

IN	B	OUT
Low ($V_{IN} < V_T$)	High (5V)	Low ($V_{OUT} = V_{OUT,Low}$)
High ($V_{IN} > V_T$)	Low ($V_{OUT,Low}$)	High (5V)

Actual

IN	B	OUT
Low ($V_{IN} < V_T$)	High (5V)	Low ()
High ($V_{IN} > V_T$)	Low ()	Low ()

$$V_T = 0.4 \text{ V}, \quad V_S = 5 \text{ V}, \quad R_{ON} = 1 \text{ k}\Omega, \quad R_L = 9 \text{ k}\Omega$$

$$V_{OUT,HI} = V_{SS}$$

$$V_{OUT,LOW} = \frac{R_{ON}}{R_{ON} + R_L} V_{SS} = 5 \cdot \frac{1}{1 + 9} = 0.5 \text{ V}$$

$$\frac{R_{ON}}{R_{ON} + R_L} V_{SS} < V_T$$

Therefore, need to design logic gates properly such that

Design of logic gates - Example

Assume the following values for the inverter circuit parameters: $V_S = 5\text{ V}$, $V_T = 1\text{ V}$, and $R_L = 10\text{ k}\Omega$. Assume, further, that $\frac{1}{k_n V_{OV}} = 5$ for the MOSFET. Determine a $(\frac{W}{L})$ sizing for the MOSFET so that the inverter gate output for a logical 0 is able to switch OFF the MOSFET of another inverter.

Solution:

$$V_S \cdot \frac{R_{ON}}{R_{ON} + R_L} < V_T$$

$$\Rightarrow 5 \frac{R_{ON}}{R_{ON} + R_L} < 1$$

$$\Rightarrow 5R_{ON} < R_{ON} + 10$$



$$\Rightarrow R_{ON} < \frac{10}{4}\text{ k}\Omega = 2.5\text{ k}\Omega$$

$$\text{Now, } R_{ON} = \frac{1}{k_n V_{OV}} = \frac{1}{k'_n \frac{W}{L} V_{OV}} = \frac{1}{5} \times \frac{1}{W/L}$$

$$\text{Hence } \frac{5}{W/L} < 2.5$$

$$\Rightarrow \frac{W}{L} > \frac{5}{2.5} = 2$$

Review – MOSFET

  

Control = $V_{GS} = V_G - V_S$ controls the IV between drain-source (I_{DS} vs V_{DS})




Threshold voltage = V_T , minimum voltage required to create the channel

Models




1. **S Mode:** Assumes an ideal channel with zero resistance
2. **SR Model:** Assumes finite channel resistance, R_{ON} , depends on $V_{GS} - V_T = V_{OV}$

MOSFET Linear Models

S Model

   




SR Model

   

$$R_{ON} = \frac{1}{k'_n \frac{W}{L} (v_{GS} - V_T - \frac{1}{2} v_{DS})}$$


Construction of Real MOSFET

Simplified cross section
and 3D view

   

No channel, open ckt

$$V_{12} = 0V$$



 


$$V_{12} > V_{\phi}$$




Channel created
Will have some R
→ SR model

Real MOSFET

   - For small V_{DS} , uniform channel, hence fixed R_{ON} therefore SR model valid.
- As V_{DS} is increased, channel becomes tapered cause $V_{GD} \downarrow$. Resistance \uparrow , slope \downarrow .
- This mode is called the **triode mode**. Condition: $V_{DS} < V_{OV}$




Real MOSFET

   

- When $V_{DS} = V_{OV}$, channel pinches off.
- Increasing V_{DS} further have no effect on channel shape. Hence, current saturates
- This mode is called the **saturation mode**. Condition: $V_{DS} \geq V_{OV}$
- Behaves like a current source (constant current) that depends on V_{OV} ,

IV Characteristics of Real MOSFET

 

Mode	Condition	Equation
Cutoff	$V_{GS} < V_T$	$I_D = 0$
Triode	$V_{GS} \geq V_T$ $V_{DS} < V_{OV}$	$I_D = k[V_{OV}V_{DS} - \frac{1}{2}V_{DS}^2]$
Saturation	$V_{GS} \geq V_T$ $V_{DS} \geq V_{OV}$	$I_D = \frac{k}{2}V_{OV}^2$

$$V_{GS} - V_T = V_{OV}$$

$$k_n = \frac{k'_n W}{L}$$