

# CSE251: Electronic Devices and Circuits

Lecture: 14 - 16 – MOSFET

**Prepared By:**

**Shadman Shahid (SHD)**

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: [ext.shadman.shahid@bracu.ac.bd](mailto:ext.shadman.shahid@bracu.ac.bd)


# Outline

- Introduction to Electronic Switches
- Logic Functions using Switches
- Introduction to a voltage-controlled switch - MOSFET
- Designing Logic gates with MOSFETs
- VTC – Voltage Transfer Characteristics


# Two terminal Devices

## Linear Devices


Resistor

 

Voltage Source

 


Current Source

 

IV characteristics of two terminal devices are fixed.

## Non-linear Devices

Diode

 


IV characteristics of **three terminal devices** can be changed

# Three terminal Devices


IV of two terminal can be controlled using a third terminal.

**Example:** Switch, MOSFET, BJT


Switch

 

 
IV characteristics between  $T_1$  and  $T_2$  can be controlled by  $C$



Switch **ON**

 


Switch **OFF**

 

 
# Switch – Types

- Depending on the control, the switch can be
  - **Analog:** Controlled using physical toggle/button
  - **Digital:** Controlled using voltage or current. Example – MOSFET (voltage controlled), BJT (current controlled)




Analog switches

 

Digital switches (Transistors)

 
# Switch Application – Logic Gates

- We can use switches to build logic gates



A	B	Bulb
0	0	OFF
0	1	OFF
1	0	OFF
1	1	ON


**AND operation**

 

A	B	Bulb
0	0	OFF
0	1	ON
1	0	ON
1	1	ON


**OR operation**

# Switch Application – Logic Gates

 


A	Bulb
0	ON
1	OFF

**NOT operation**

 

A	B	Bulb
0	0	ON
0	1	ON
1	0	ON
1	1	OFF

**NAND operation**

 


A	B	Bulb
0	0	ON
0	1	OFF
1	0	OFF
1	1	OFF

**NOR operation**

These circuits are “preferred” – because they can be cascaded to build combinational logic circuits  
-> if we remove the bulb and use the voltage across instead to cascade and drive the next gate


# Switch Application – Logic Gates

Alternative representations:

 


$$\text{OUT} = \overline{A}$$

(NOT)

 

$$\text{OUT} = \overline{AB}$$

(NAND)

 


$$\text{OUT} = \overline{A+B}$$

(NOR)




# Switch Application – Logic Gates

Alternative representations:

 


$$OUT = \overline{AB}$$

(NAND)

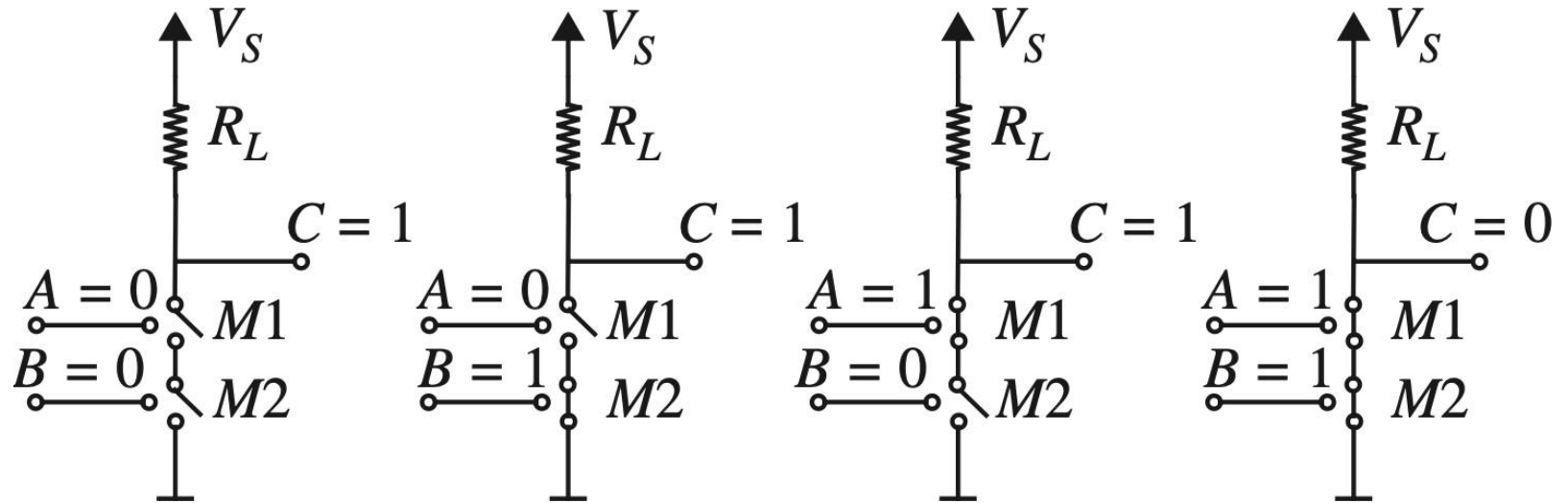


# Switch Application – Logic Gates

 


$$OUT = \overline{A}$$

A	V <sub>OUT</sub>
0	5V
1	0V

 

$$OUT = \overline{AB}$$

A	B	V <sub>OUT</sub>
0	0	5V
0	1	5V
1	0	5V
1	1	0V

 


$$OUT = \overline{A+B}$$

A	B	V <sub>OUT</sub>
0	0	5V
0	1	0V
1	0	0V
1	1	0V


# Examples

①

 

$$f = \overline{A + B.C}$$


②

 

$$f = \overline{A\overline{B}}$$
 
# Example


Implement using switches:  $f = (A + B)C$


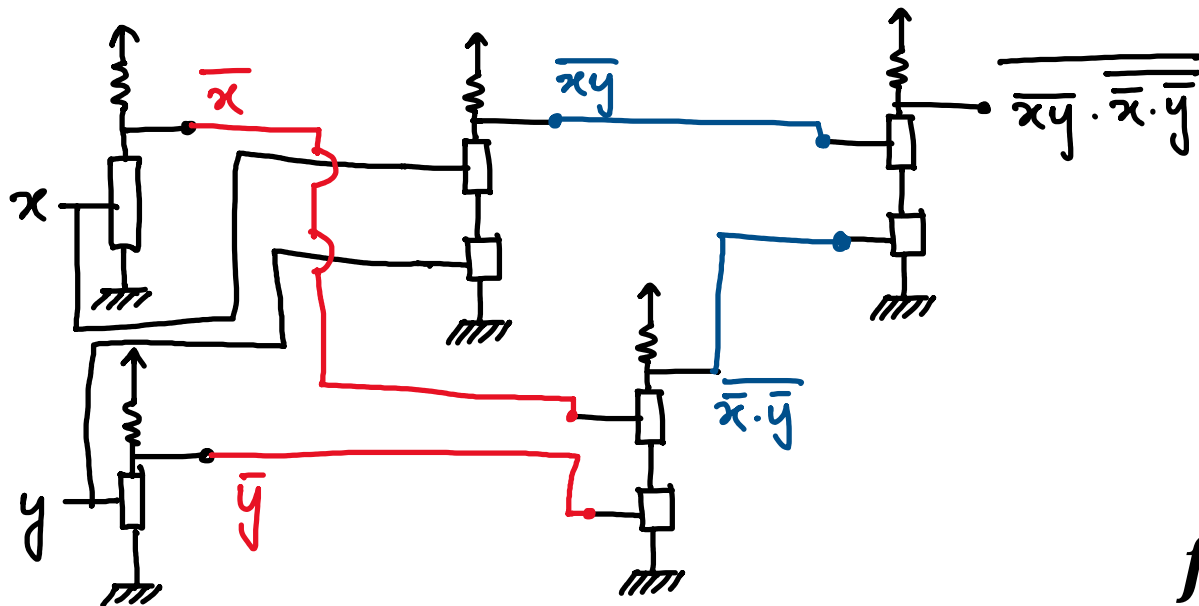
# Practice Problem 1

In digital systems, binary data may be subjected to noise that can alter a 0 to a 1 or a 1 to a 0.

A simple way to check if any error has occurred is to use an **even parity checker**. If there are two input bits  $x$  and  $y$ , the output of the even parity checker (denoted as  $f$ ) will be **HIGH** if there are even number of 1s, i.e., if both  $x$  and  $y$  are 0 or if both of them are 1.



$x$	$y$	$f$
0	0	
0	1	
1	0	
1	1	

$$\begin{aligned} f &= x \cdot y + \bar{x} \cdot \bar{y} = \overline{\overline{x \cdot y + \bar{x} \cdot \bar{y}}} \\ &= \overline{\overline{x \cdot y} \cdot \overline{\bar{x} \cdot \bar{y}}} \end{aligned}$$

# Digital Representation

- Binary  $\rightarrow$  Two states (0/False, 1/True)
- Binary variables in circuit, need to use two states of device/parameters

## Voltage

5V  $\rightarrow$  1

0V  $\rightarrow$  0

0V  $\rightarrow$  1

3.3V  $\rightarrow$  0

## Current

2mA  $\rightarrow$  1

3mA  $\rightarrow$  0

## State

Diode

ON  $\rightarrow$  1

OFF  $\rightarrow$  0




Memristor

Low resistance

High resistance

 
 
 
# Transistors as Digital Switch

- Transistors are 3 terminal non-linear devices, can be used as switch
- 2 types – **Voltage Controlled**, **Current Controlled**
- **M**etal **O**xide **S**emiconductor **F**ield **E**ffect **T**ransistor (**MOSFET**) are **voltage controlled**
- Control,  $C = V_{GS}$ . The IV characteristics ( $I_{DS}$  vs  $V_{DS}$ ) depends on  $V_{GS}$
- Actual dependency is complex.
- Will start with a simple (but approximate) one – **S-Model** (Switch Model)



  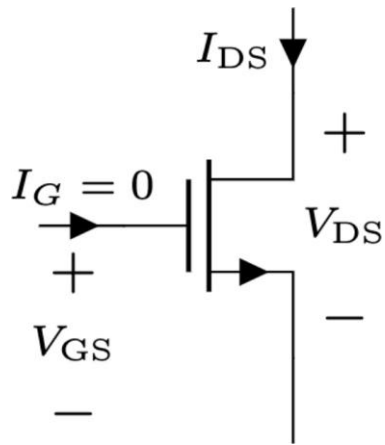
# MOSFET S-Model

- The MOSFET (approximately) behaves like a switch
- $C = V_{GS}$ . Here,  $C = \text{"0"} \Rightarrow V_{GS} < V_T$ , and  $C = \text{"1"} \Rightarrow V_{GS} \geq V_T$





# MOSFET S-Model

 

We can summarize the S model for the MOSFET in algebraic form by stating its  $v$ - $i$  characteristics as follows:


$$\text{for } v_{GS} < V_T, \quad i_{DS} = 0$$

and


$$\text{for } v_{GS} \geq V_T, \quad v_{DS} = 0 \quad (6.2)$$

# Logic Gates using MOSFET


Just replace the switches with MOSFETs!

 

NOT Gate (Inverter)

 


NAND Gate (Inverter)

 


NOR Gate (Inverter)

# MOSFET Logic Gates – More Examples

 

$$OUT = \overline{AB + C + D}$$

 

$$Out = \overline{\overline{(A + B)CD}} = (A + B)CD$$

# Practice Problem 2


- **Design** a circuit using ideal MOSFETs (S-model) to implement the logic function

$$f = \overline{AC} + \overline{(B + C)}$$

$$= \overline{\overline{AC} + \overline{(B + C)}}$$

$$= \overline{\overline{AC}} \cdot \overline{\overline{(B + C)}} \quad [\text{De Morgan's Theorem}]$$

 
$$= \overline{AC} \cdot \overline{(B + C)}$$


 
# Practice Problem 1

In digital systems, binary data may be subjected to noise that can alter a 0 to a 1 or a 1 to a 0.

A simple way to check if any error has occurred is to use an **even parity checker**. If there are two input bits  $x$  and  $y$ , the output of the even parity checker (denoted as  $f$ ) will be **HIGH** if there are even number of 1s, i.e., if both  $x$  and  $y$  are 0 or if both of them are 1.




$x$	$y$	$f$
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned} f &= x \cdot y + \bar{x} \cdot \bar{y} = \overline{\overline{x \cdot y + \bar{x} \cdot \bar{y}}} \\ &= \overline{\overline{x} \cdot \overline{y} \cdot \overline{\bar{x}} \cdot \overline{\bar{y}}} \end{aligned}$$

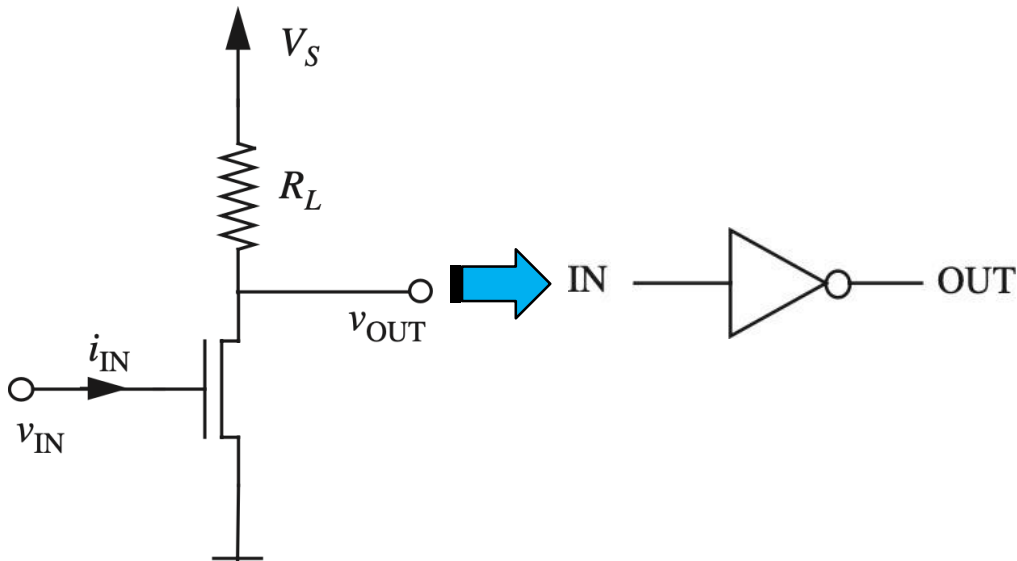
# Voltage Transfer Characteristics (VTC)

- **Reminder:** VTC is a graph where  $x$  –axis = input voltage,  $y$ -axis = output voltage
- **Why?** Design logic gates to follow a given static discipline




When  $v_{IN} < V_T$  (Logical 0)  $v_{OUT} = V_S = 5\text{ V}$  (Logical 1)

 When  $v_{IN} \geq V_T$  (Logical 1)  $v_{OUT} = 0\text{ V}$  (Logical 0)



 
# Voltage Transfer Characteristics (VTC)

- **Reminder:** VTC is a graph where  $x$  –axis = input voltage,  $y$ -axis = output voltage
- **Why?** Design logic gates to follow a given static discipline




When  $v_{IN} < V_T$  (Logical 0)  $v_{OUT} = V_S = 5\text{ V}$  (Logical 1)

 When  $v_{IN} \geq V_T$  (Logical 1)  $v_{OUT} = 0\text{ V}$  (Logical 0)



 
# VTC of NAND gate


- We only have one  $x$  –axis, but two inputs
- **Solution:** Draw two VTC, one considering  $V_A = 0$  one considering  $V_A = 1$



When  $V_A = 0$

 


When  $V_A = 1$

 



 
# VTC of NAND gate


- We only have one  $x$  –axis, but two inputs
- **Solution:** Draw two VTC, one considering  $V_A = 0$  one considering  $V_A = 1$



When  $V_A = 0$

 


When  $V_A = 1$

 

**Homework:** Find VTC for NOR gate


# Digital Representation

Suppose you want to send 010110

 

- Single value based representation fails in the presence of noise
- Better approach – threshold-based system
- Simplest: **Logical 0** =  $V < V_T$       **Logical 1** =  $V > V_T$


# Static Discipline

 

- Specification for “all” digital devices
- Requires devices to adhere to common representation to ensure that **valid input produces valid output**
- This means, if
  - Sender sends “0”  $\xrightarrow[\text{Channel}]{\text{noise}}$  Receiver interprets as “0”
  - Sender sends “1”  $\xrightarrow[\text{Channel}]{\text{noise}}$  Receiver interprets as “1”

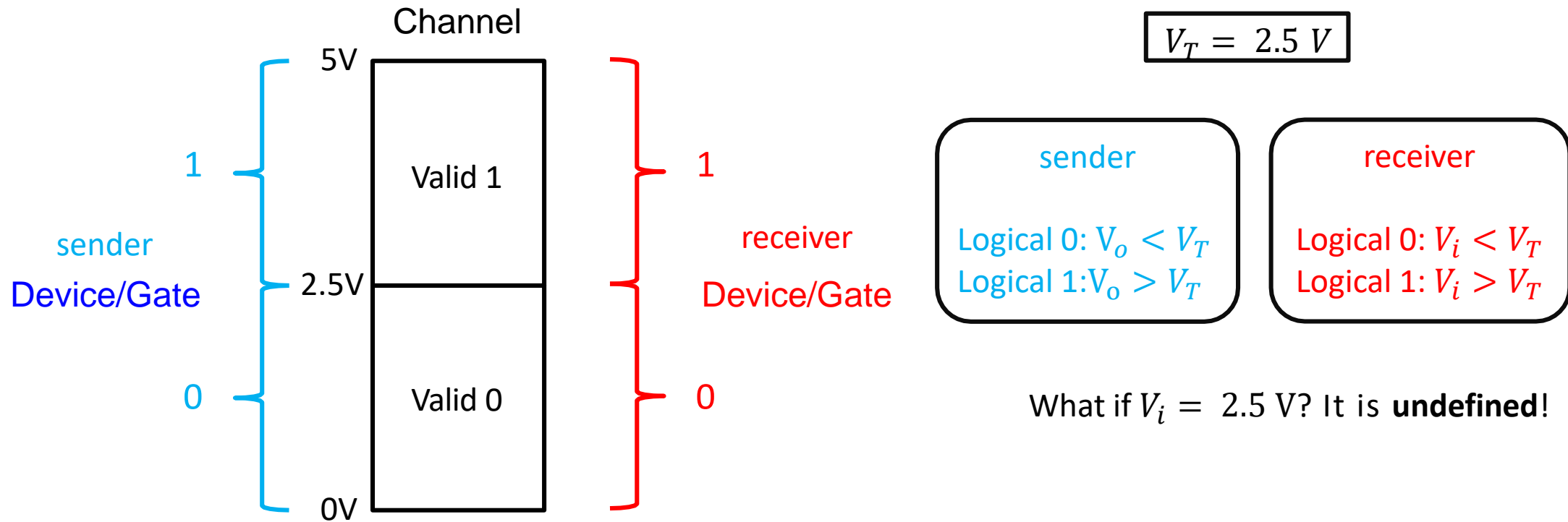
# Static Discipline

Naïve approach: Single threshold-based system



# Static Discipline

## Double threshold based system

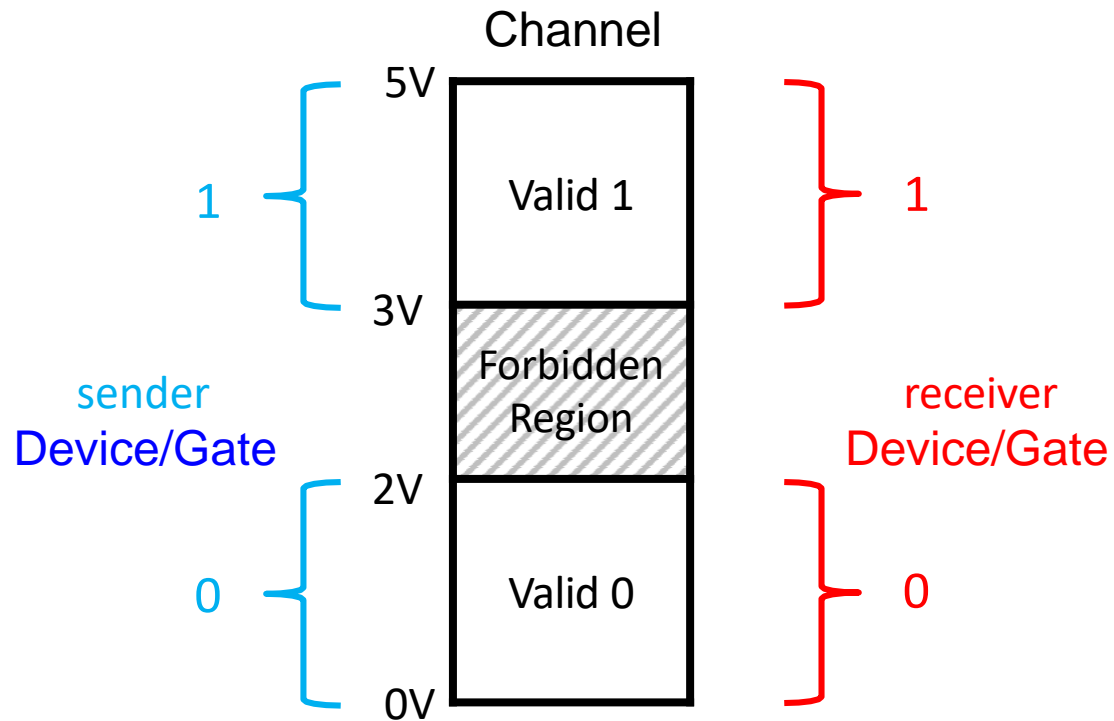

$V_H$  = High voltage threshold = 3V

$V_L$  = High voltage threshold = 2V

sender

Logical 0:  $V_o < V_L$   
Logical 1:  $V_o > V_H$

receiver

Logical 0:  $V_i < V_L$   
Logical 1:  $V_i > V_H$


What if  $V_o = 1.9V$  and channel noise is  $0.5V$ ?

$V_i = 1.9V + 0.5V = 2.4V = \text{invalid}$

→ valid output producing invalid input,  
i.e., no margin for noise
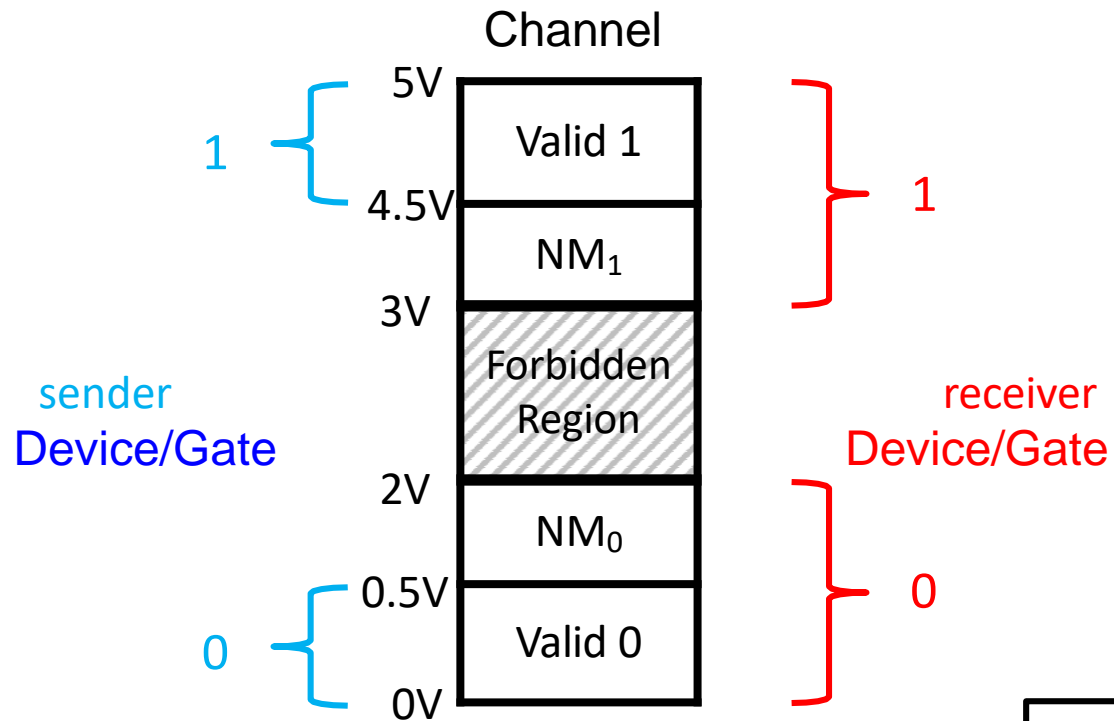
# Static Discipline

Four threshold-based system → Tighter restriction on sender (**output**)



$V_{OH}$  = Output high voltage threshold = 4.5V

$V_{OL}$  = Output low voltage threshold = 0.5V

$V_{IH}$  = Input high voltage threshold = 3V

$V_{IL}$  = Input low voltage threshold = 2V

sender

Logical 0:  $V_o < V_{OL}$   
Logical 1:  $V_o > V_{OH}$

receiver

Logical 0:  $V_i < V_{IL}$   
Logical 1:  $V_i > V_{IH}$

For static discipline,  $V_{OL} < V_{IL} < V_{IH} < V_{OH}$

Noise margins (NM):



- $NM_1 = V_{OH} - V_{IH} = 4.5 - 3 = 1.5 \text{ V}$  (significance?)
- $NM_0 = V_{IL} - V_{OL} = 2 - 0.5 = 1.5 \text{ V}$  (significance?)

# Static Discipline

Four threshold-based system → Tighter restriction on sender (**output**)

$V_{OH}$ : The lowest output voltage value that a digital device **can produce** when it outputs a logical 1.

  $V_{OL}$ : The highest output voltage value that a digital device **can produce** when it outputs a logical 0.




$V_{IH}$ : The *lowest input voltage* value that a digital device **must recognize** as a logical 1.

$V_{IL}$ : The *highest input voltage* value that a digital device **must recognize** as a logical 0.

 
# Static Discipline and VTC graph

Four threshold-based system → Tighter restriction on sender (**output**)



During high to low or low to high **transition**:

Higher Slope in VTC graph

 


While **not** in **transition**; at logical **HIGH** or **LOW** voltage level:

Smaller Slope in VTC graph



# Static Discipline and VTC graph

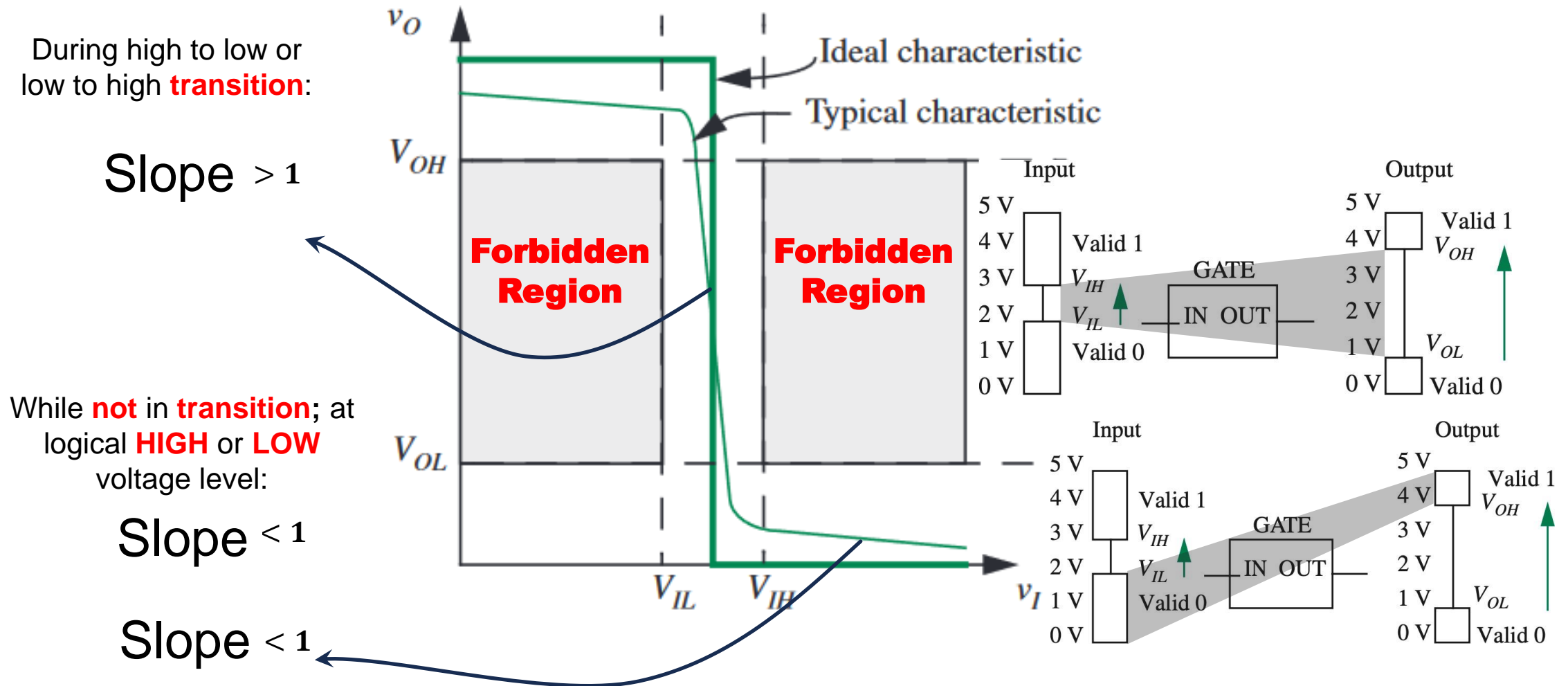

# Next Class

- Constructing a \*real\* MOSFET – n/p-channel
- Operation of an Ideal FET- Cut-Off, Saturation and Triode Mode
- Output Characteristics
- PWL Model and Non-ideal Analysis: SR model
- Real MOSFET equations
- Introduction to Static analysis