
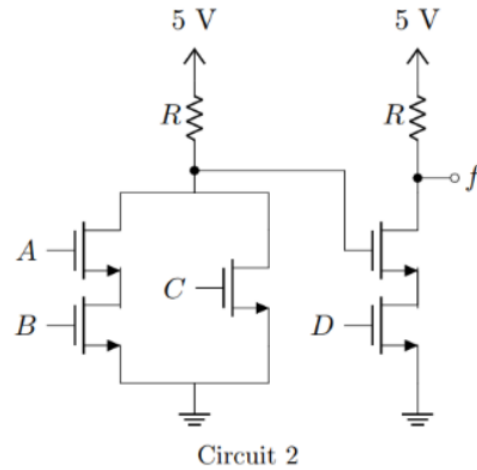


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, the **exam script** must be returned to the invigilator.
- ✓ Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room for an answer, please continue on the back of the page".
- ✓ Symbols have their usual meanings.

Question 1:

10 Marks

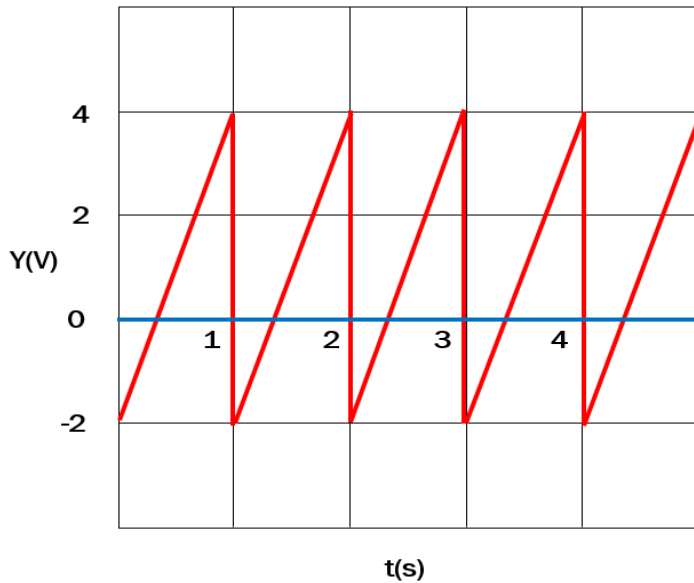

The input of a **Half-wave rectifier** is exhibited in the Figure above and output load resistance is $R = 5 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7 \text{ V}$.

- i. Show the input and output waveforms. [2.5]
- ii. Draw the VTC curve [2.5]
- iii. Calculate input and output frequency [2.5]
- iv. Write down the logic function f of **Circuit 2**. [2.5]

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, the **exam script** must be returned to the invigilator.
- ✓ Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room for an answer, please continue on the back of the page".
- ✓ Symbols have their usual meanings.

Question 1: [CO2]

10 Marks

The BJT in the adjacent figure has a $V_0 = -4.7$ V and $I_B = 0.042$ mA. and $B = 100$

- i. Determine the operating mode of the BJT. [4]
- ii. Find V_E , I_C and I_E [6]

