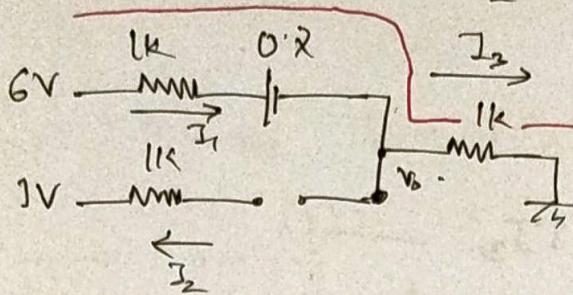


Find I_1 , I_2 , I_3 , V_0 . Use CVD model with $V_f = 0.2V$

Solⁿ: Assume $D_1 = ON$, $D_2 = OFF$



$$I_2 = 0. \quad [OFF]$$

$$I_1 = I_2 + I_3 \quad [KCL]$$

$$\therefore I_1 = I_3$$

Writing KVL along 6V to GND [Red line]

$$6 = 1I_1 + 0.2 + I_3 + 0$$

$$\Rightarrow 2I_1 = 6 - 0.2 \quad [since I_1 = I_3]$$

$$\Rightarrow I_1 = I_3 = 2.65 \text{ mA}$$


$$\therefore V_0 = 1I_3 = 2.65V$$

Now $I_1 = +ve$, so D_1 assumption correct

$\begin{aligned} & \text{Ans for } D_2, \\ & V_A = V_0 = 2.65V \\ & V_C = 1V \\ & \therefore V_D = 1.65V \end{aligned}$

So assumption wrong

Assume $D_1 = ON, D_2 = ON$

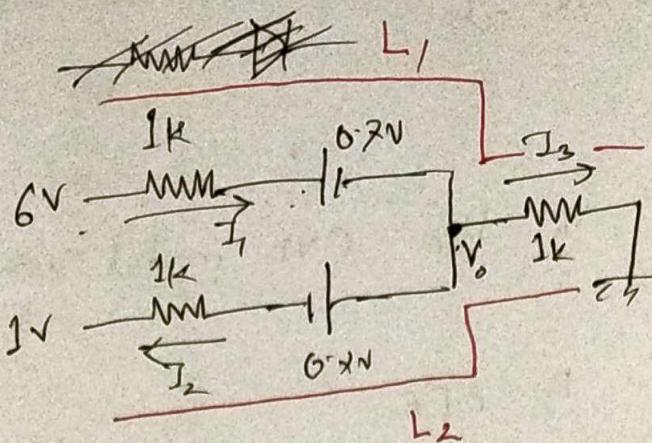

KVL along L_1

$$6 = 1I_1 + 0.2 + 1I_3 \quad \text{--- (1)}$$

$$\text{KVL along } L_2 \\ 1 = -1I_2 - 0.2 + 1I_3 \quad \text{--- (1')}$$

KCL \Rightarrow

$$I_1 = I_2 + I_3 \quad \text{--- (1'')}$$

Solving (1), (1') and (1'')


$$I_1 = 2.96 \text{ mA}$$

$$I_2 = 0.63 \text{ mA}$$

$$I_3 = 2.33 \text{ mA}$$


$$\therefore V_0 = 1I_3 = 2.33 \text{ V}$$

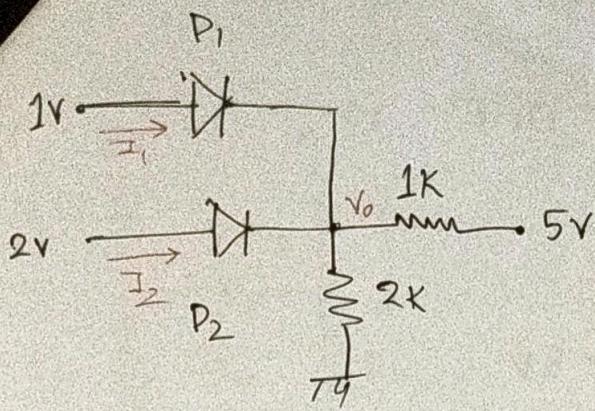$I_1 = +ve \Rightarrow D_1 \text{ assumption correct} \checkmark$
 $I_2 = +ve \Rightarrow D_2 \text{ assumption correct} \checkmark$



Find I_1 , I_2 and V_o . Assume the diodes are ideal.

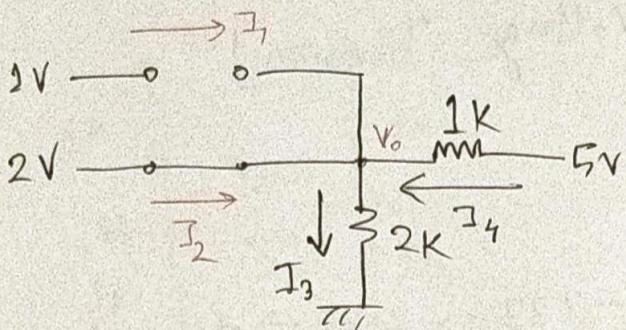Sol'n.: Assume $D_1 = \text{OFF}$, $D_2 = \text{ON}$



$$\therefore I_1 = 0 \quad (\text{OFF})$$

$$\therefore V_o = 2V$$

$$\therefore I_3 = \frac{V_o}{2} = 1mA, \quad I_4 = \frac{5 - V_o}{1} = \frac{5 - 2}{1} = 3mA$$


$$\text{KCL} \Rightarrow I_2 + I_4 = I_3 \Rightarrow I_2 = I_3 - I_4$$

$$\therefore [I_2 = -2mA]$$

D_2 assumption wrong

For D_1 , $V_D = V_A - V_C = 1 - 2 = -1 \Rightarrow$ Assumption correct

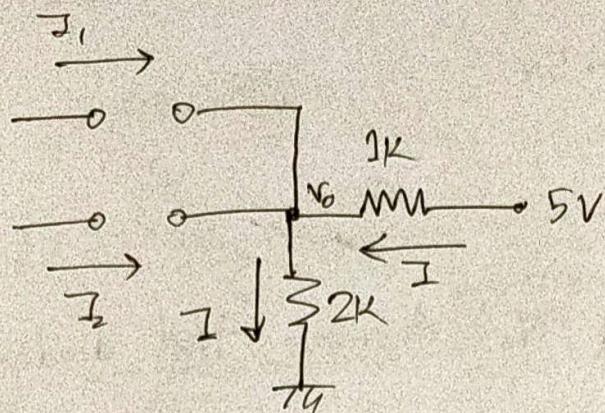Assume $D_1 = \text{OFF}$, $D_2 = \text{OFF}$



$$I_1 = 0$$

$$I_2 = 0$$

$$V_o = \frac{2}{2+1} \times 5 \quad [\text{Voltage Division}]$$


$$\Rightarrow V_o = 3.33V$$

For $D_1 \Rightarrow V_D = V_A - V_C = 1 - 3.33 = -2.33 \Rightarrow \text{Assumption correct}$

For $D_2 \Rightarrow V_D = V_A - V_C = 2 - 3.33 = -1.33 \Rightarrow$


✓ ↴

(3)

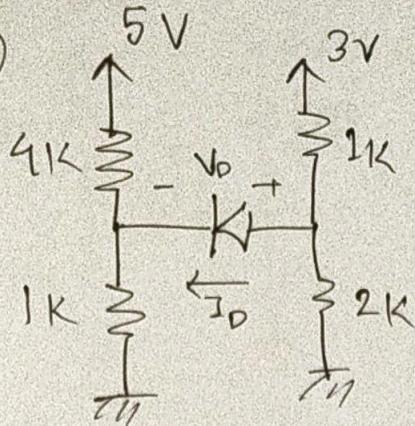

Find V_D and I_D . Use CVD with $V_g = 0.8V$.

Solⁿ: Assume diode OFF

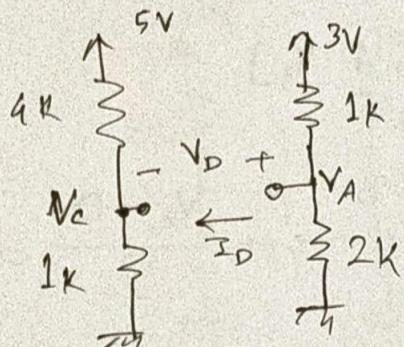

$$\therefore I_D = 0$$


$$V_A = \frac{2}{2+1} \times 3 = 2V \quad [\text{Voltage division}]$$

$$V_C = \frac{1}{9+1} \times 5 = 1V \quad [\quad \quad \quad]$$

$$\therefore V_D = V_A - V_C = 2 - 1 = 1V$$

∴ Assumption wrong!

So, the diode would be on!

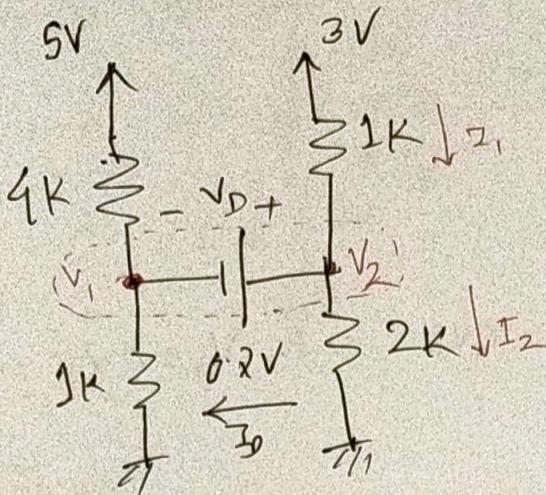

$$\therefore V_D = 0.2V$$

Super node equation (V_1 and V_2)

$$\frac{V_1 - 5}{1} + \frac{V_1 - 0}{1} + \frac{V_2 - 3}{1} + \frac{V_2 - 0}{2} = 0 \quad (1)$$

$$V_2 - V_1 = 0.2 \quad (II)$$


Solving (I) and (II)

$$V_1 = \cancel{1.636V} \approx 1.63V$$

$$V_2 = 1.863V$$

$$I_1 = \frac{3 - V_2}{1} = 1.137 \text{ mA}, \quad I_2 = \frac{V_2 - 0}{2} = 0.932 \text{ mA}$$

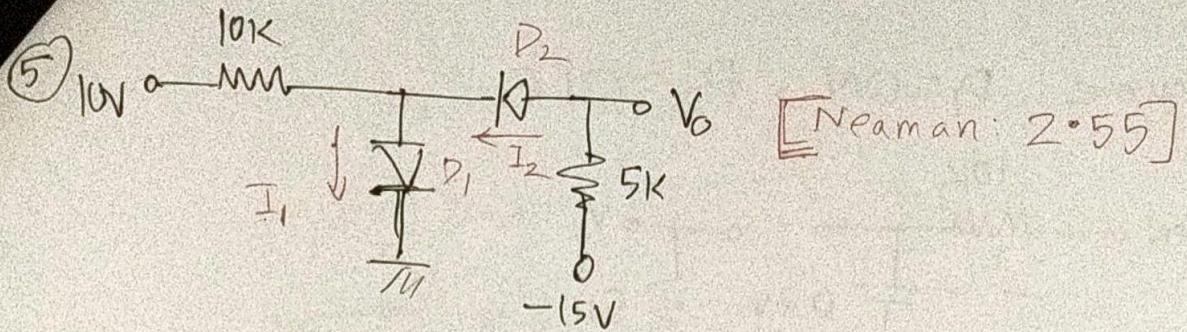
$$\therefore I_D = I_1 - I_2 \quad [\text{KCL}] = 0.205 \text{ mA} \quad [\text{Correct assumption}]$$



[Neaman: 2.55]

Find V_0, I_1, I_2 . Use CVD model with $V_2 = 0.2V$.

Soln: Assume $D_1 = ON, D_2 = ON$.

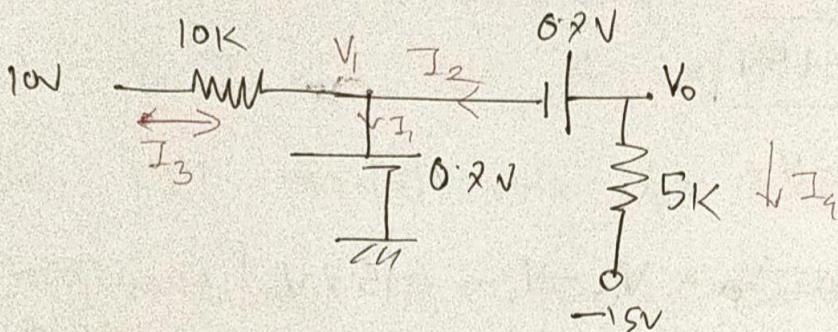

$$V_1 = 0.2V$$

$$V_0 = V_1 + 0.2V = 1.4V$$


$$I_3 = \frac{10 - 0.2}{10} = 0.93mA$$

$$I_4 = \frac{1.4 - (-15)}{5} = 3.28mA$$

From KCL, $I_2 = -I_4 = -3.28mA$ [Assumption wrong for D_2]

$$I_1 = I_3 + I_2 = -2.35mA$$
 [Assumption wrong for D_1]

Assume $D_1 = ON \Rightarrow D_2 = OFF$

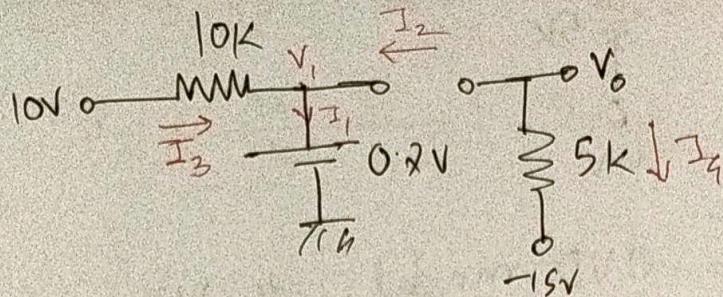

$$\text{open } CKT \Rightarrow I_2 = 0$$

$$I_4 = 0$$

$$\therefore \boxed{V_0 = -15V}$$

$$V_1 = 0.2V$$

$$\therefore V_{D_2} = \cancel{V_0} - \cancel{V_D} = V_0 - V_1 = -15.2V$$

[Assumption correct for D_2]

$$I_3 = \frac{10 - V_1}{10} = \frac{10 - 0.2}{10} = 0.93mA$$


$$I_1 = I_3 = 0.93mA$$

[Assumption correct for D_1]

$$\therefore \boxed{V_0 = -15V}$$

Ans


(6)

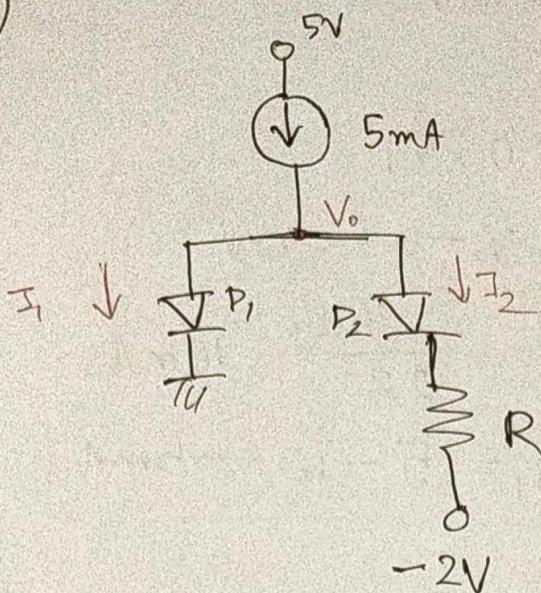

Find V_o , I_1 and I_2 for (a) $R = 100\text{ k}\Omega$, (b) ~~$R = 1\text{ k}\Omega$~~ .

Use CVD model with $V_T = 0.2\text{ V}$.

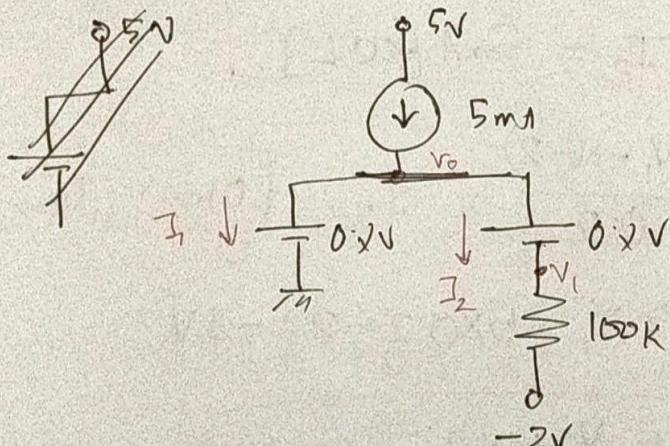Solⁿ: (a) assume $D_1 = \text{ON}$, $D_2 = \text{ON}$




$$V_o = 0.2\text{ V}$$

$$V_i = V_o - 0.2 = 0\text{ V}$$

$$\therefore \begin{cases} I_2 = \frac{0 - (-2)}{100} = 0.02\text{ mA} \\ I_1 = 5 - I_2 [KCL] = 4.98\text{ mA} \end{cases}$$

Since I_1 and I_2 both are positive, Assumption correct.

b) Assume $D_1 = ON, D_2 = ON$

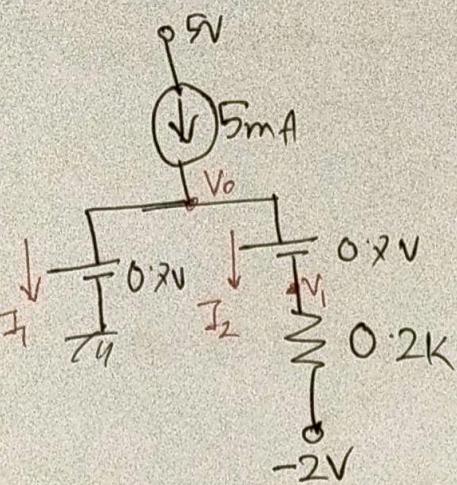

$$V_o = 0.2V$$


$$V_i = V_o - 0.2 = 0V$$

$$I_2 = \frac{0 - (-2)}{0.2} = 10mA$$

$$\therefore I_1 = 5 - I_2 = -5mA$$

Since current through D_1 is negative, assumption wrong.

Assume $D_1 = OFF, D_2 = ON$

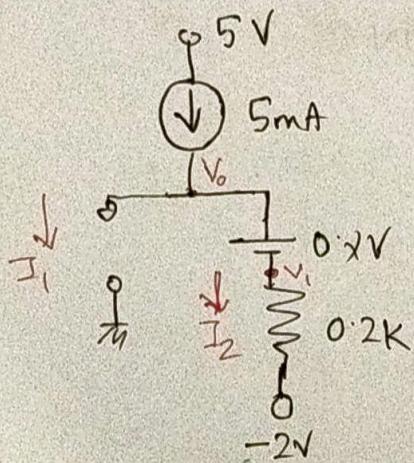

$$I_1 = 0mA$$

$$I_2 = 5mA [FCL]$$

$$\frac{V_i - (-2)}{0.2} = I_2 \quad [Ohm's Law]$$

$$\Rightarrow V_i = 5 \times 0.2 - 2 = -1V$$

$$V_o = V_i + 0.2 = -0.3V$$

Since $V_D = -0.3V$ for D_1 and $V_D < 0.2V$

assumption for D_1 correct.

$I_1 = +ve \Rightarrow$ Assumption for D_2 correct.