



# CSE251: Electronic Devices and Circuits

## Lecture 1

**Alt. Representation, CSE250 Review, IV Characteristics**

Prepared By:

**Shadman Shahid (SHD)**

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

*Email: shadman9085@gmail.com*


# Alternative Circuit Representation: Line diagrams

Steps to decompose circuits to line diagram



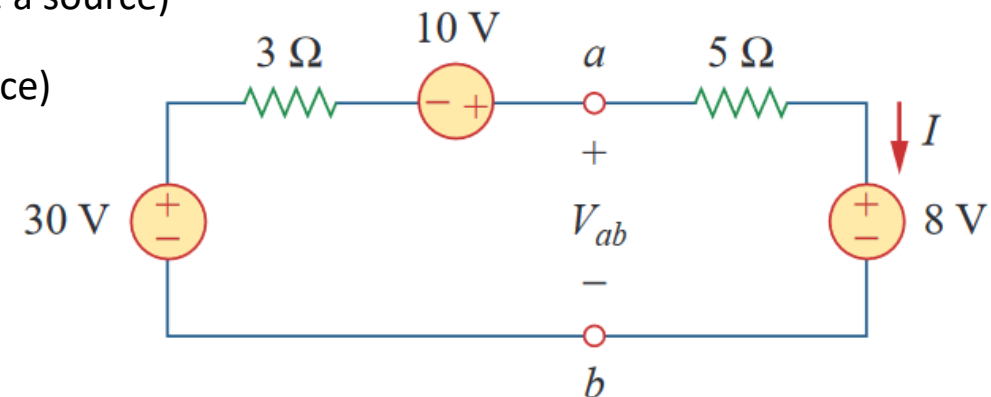
1. Set a ground so that number of **floating voltage** sources are minimized.
2. Detach the ground
3. Convert the non-floating voltage sources (~~current sources~~) into:
  - Arrow : ( $\rightarrow$ ) **Fixed/Constant voltage source**
  - Open circle dot: ( $-o$ ) Input/Output node voltage (may or may not be a source)
  - Filled circle dot: ( $-●$ ) Known node voltage (may or may not be a source)
4. Keep passive elements as they are.

**Floating voltage** sources:




Voltage sources which are **not connected the ground** terminal. In the diagram, the **10 V** voltage source is floating



# Line diagrams: Example 1

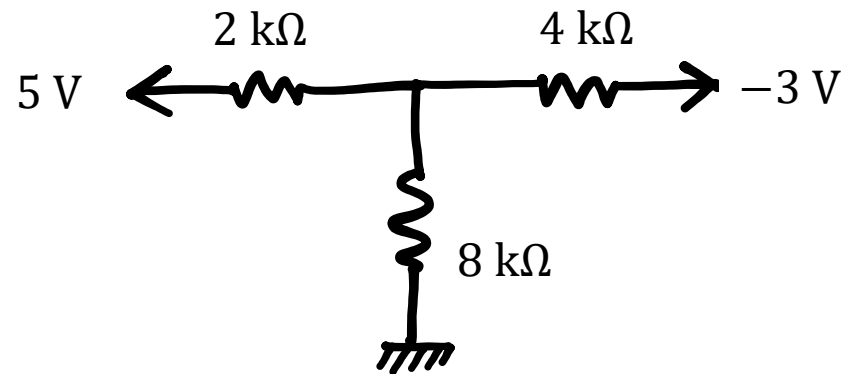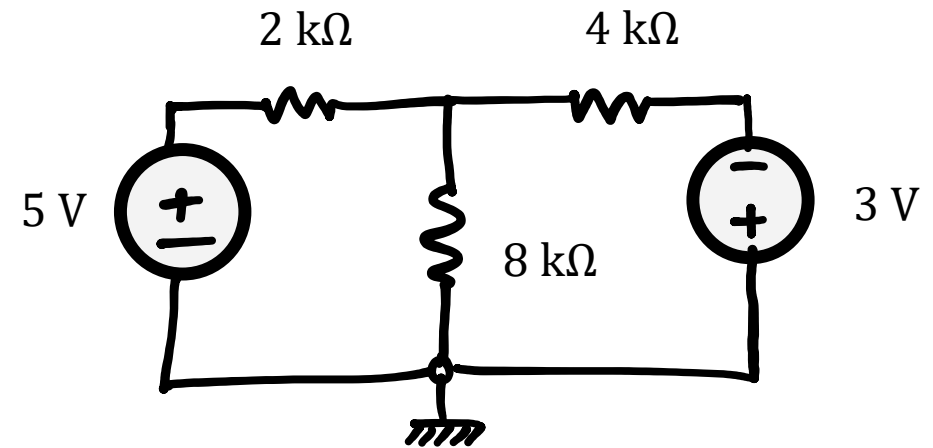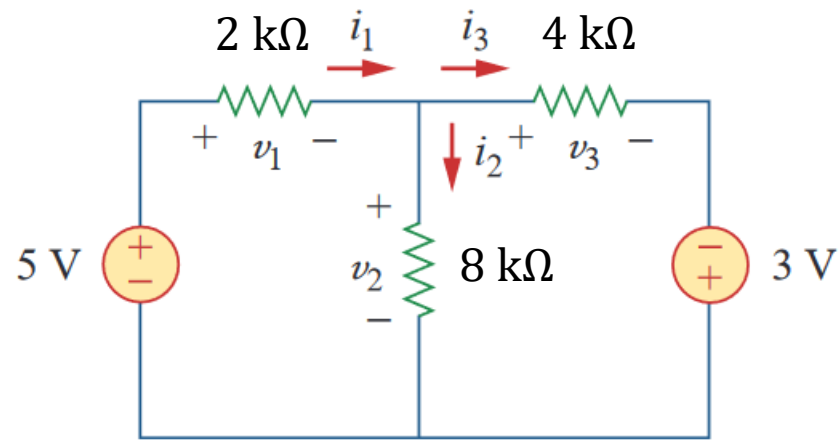


# Line diagrams: Example 2

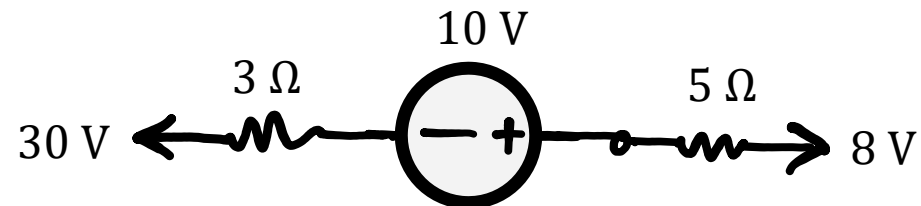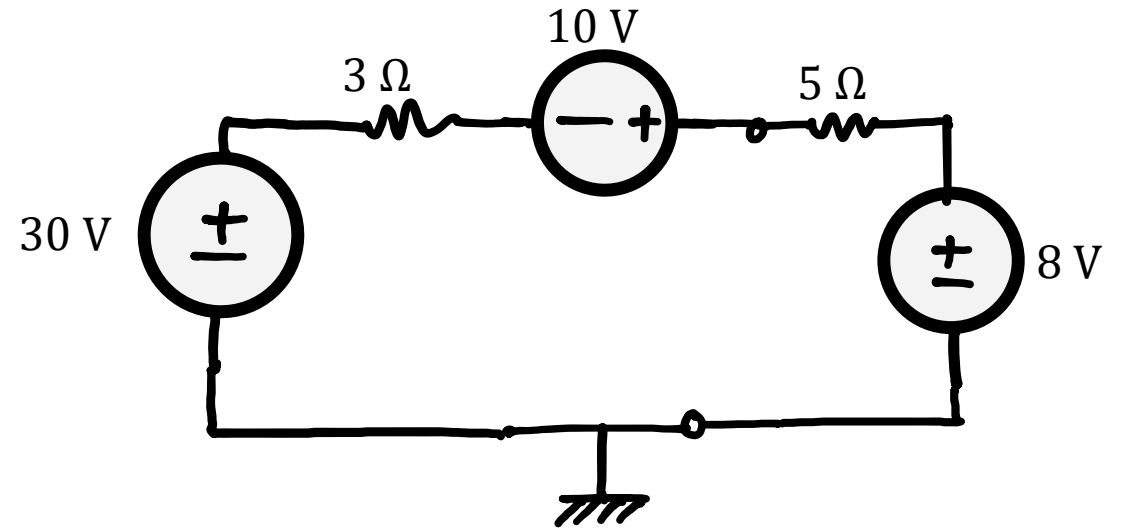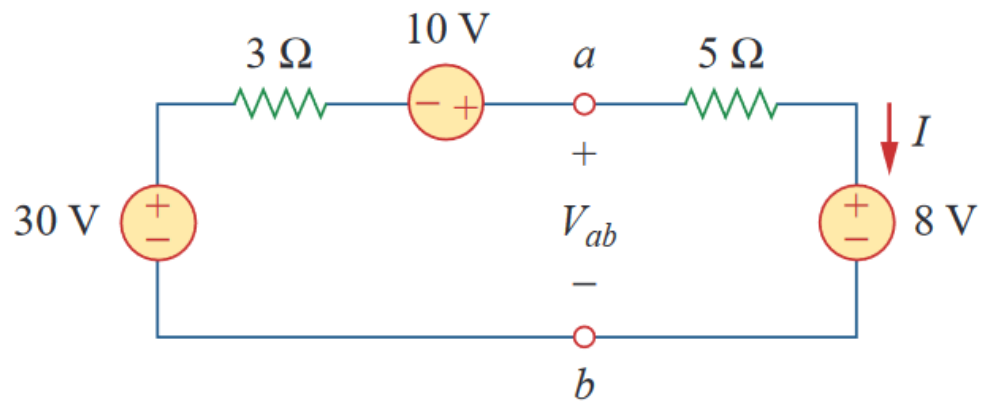


# More Examples

Difficulty : 2/5

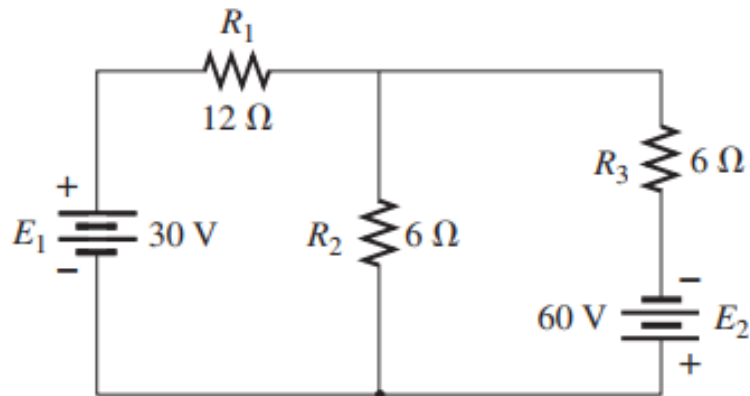

Example: 2


Difficulty : 3/5

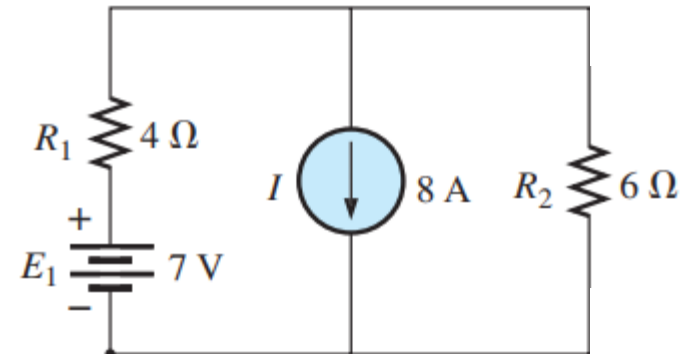

Example: 3

# More Examples

Difficulty : 4/5

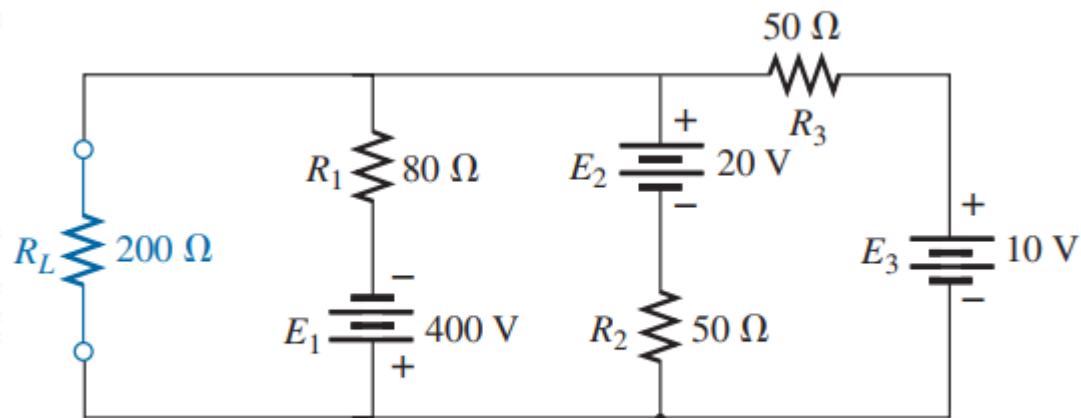

Example: 4

Step – (4) Make all the active elements (dc/ac type, voltage/~~current~~ sources) into single terminals (arrows/circles) using the voltages you wrote as much as you can **[THERE MIGHT BE CASES WHERE YOU CAN'T DO THAT]**


# The fundamentals ...

## Ohm's Law –

- the voltage  $v$  across a resistor is **directly proportional** to the current  $i$  flowing through the resistor ( $R$ )

$$v \propto i$$

$$v = iR$$

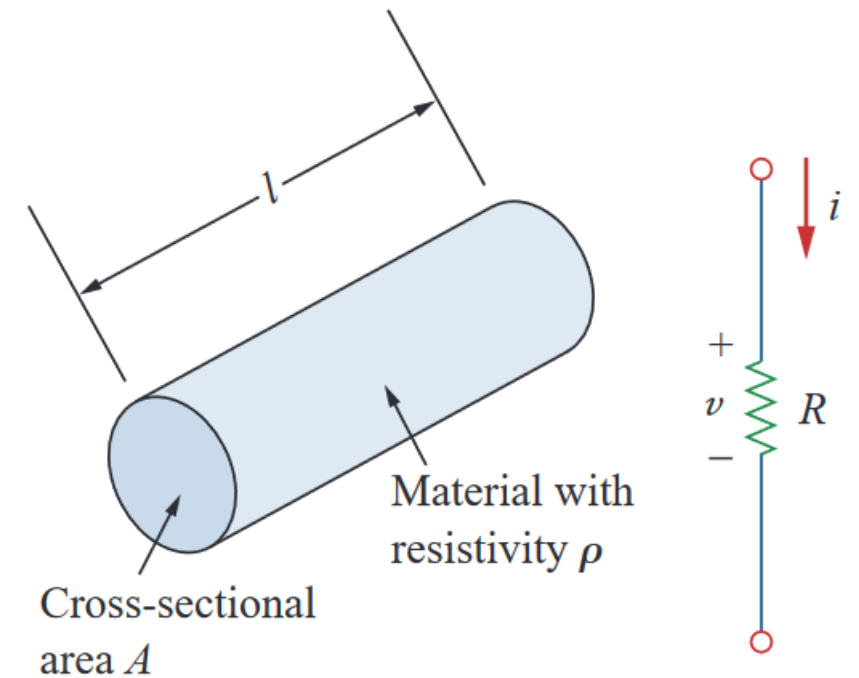


# KVL: Kirchhoff's voltage law

The algebraic sum of all **voltages** around **a closed path (or loop)** is zero.

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_2 + v_3 + v_5 = v_1 + v_4$$

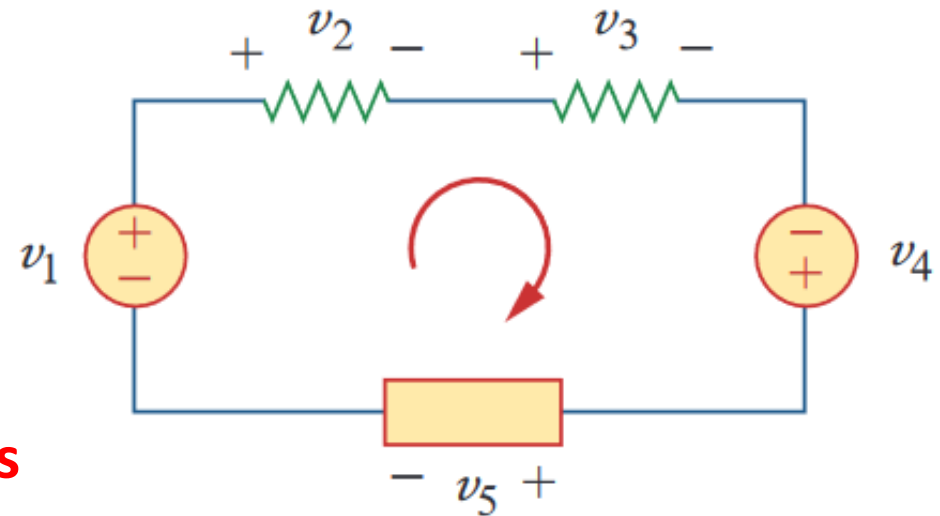Sum of voltage drops = **Sum of voltage rises**






# KVL: Kirchhoff's voltage law

$$-V_{ab} + V_1 + V_2 + V_3 = 0$$

$$V_{ab} = V_1 + V_2 + V_3$$

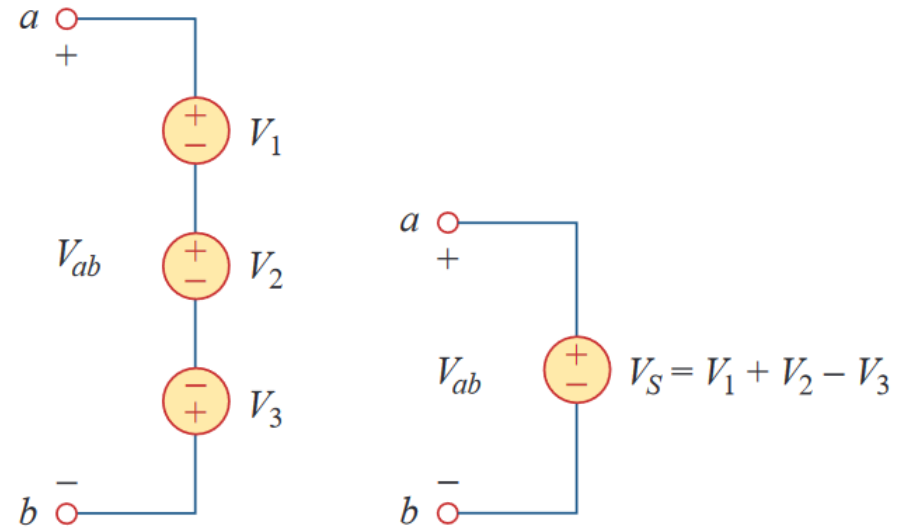

Equivalent Circuits

# KVL – Example 1

Find  $I$  and  $V_{ab}$  in the circuit

**Solution:**

KVL


$$-30 + 3I - 10 + 5I + 8 = 0$$

$$I = \frac{32}{8} \text{ A} = 4 \text{ A}$$

KVL

$$-V_{ab} + 5I + 8 = 0$$

$$V_{ab} = 28 \text{ V}$$

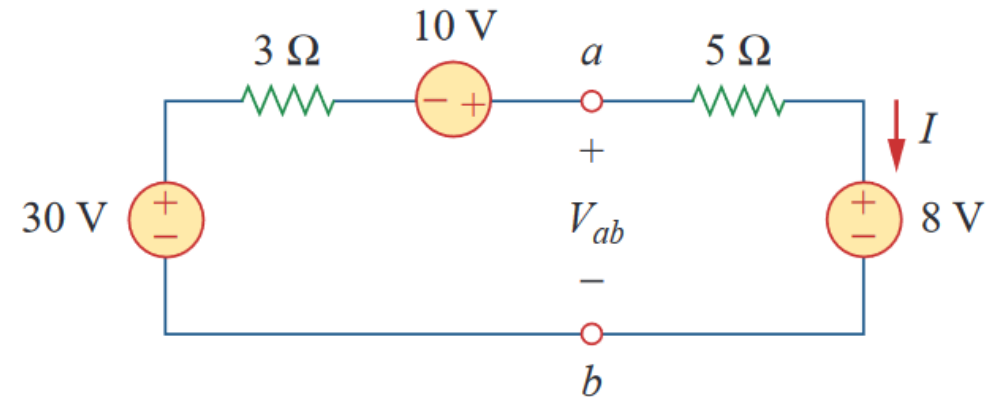

**Tip:** If you find resistance values in **kΩ** instead of **Ω**, don't convert the **kΩ** values to **Ω**. Just find currents in **mA** instead of **A**.

# KVL – Example 2

Find  $v_1, v_2, v_3, i_1, i_2$  and  $i_3$  in the circuit

## Solution:

KVL in first loop

$$-5 + 2i_1 + 8(i_1 - i_3) = 0$$

$$10i_1 - 8i_3 = 5$$

KVL in second loop

$$-8(i_1 - i_3) + 4i_3 - 3 = 0$$

$$-8i_1 + 12i_3 = 3$$

Solving:

$$i_1 = 1.5 \text{ mA}$$


$$i_3 = 1.25 \text{ mA}$$

$$i_2 = i_1 - i_3 = 0.25 \text{ mA}$$

$$v_1 = 3 \text{ V}$$

$$v_2 = 2 \text{ V}$$

$$v_3 = 5 \text{ V}$$

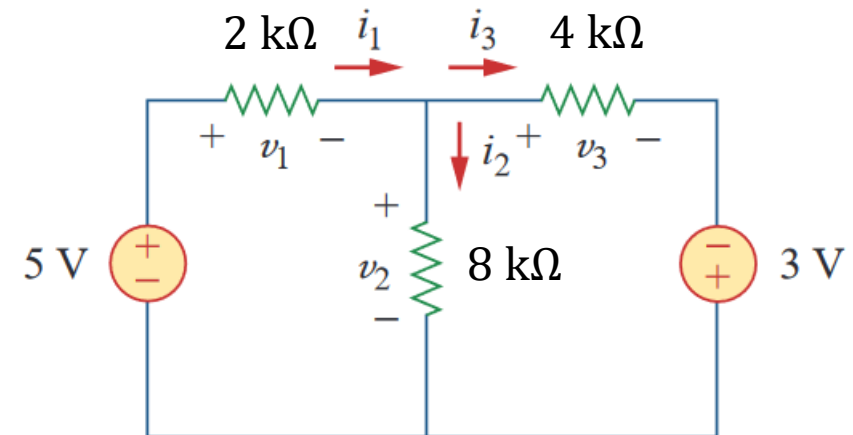

**Tip:** If you find resistance values in **kΩ** instead of **Ω**, don't convert the **kΩ** values to **Ω**. Just find currents in **mA** instead of **A**.


# KCL: Kirchhoff's Current Law

The algebraic sum of the **currents** entering a **node (closed boundary)** is equal to the sum of the currents leaving the node.

$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$

Current Entering node: **Positive**  
Current Exiting node: **Negative**

Or vice versa...

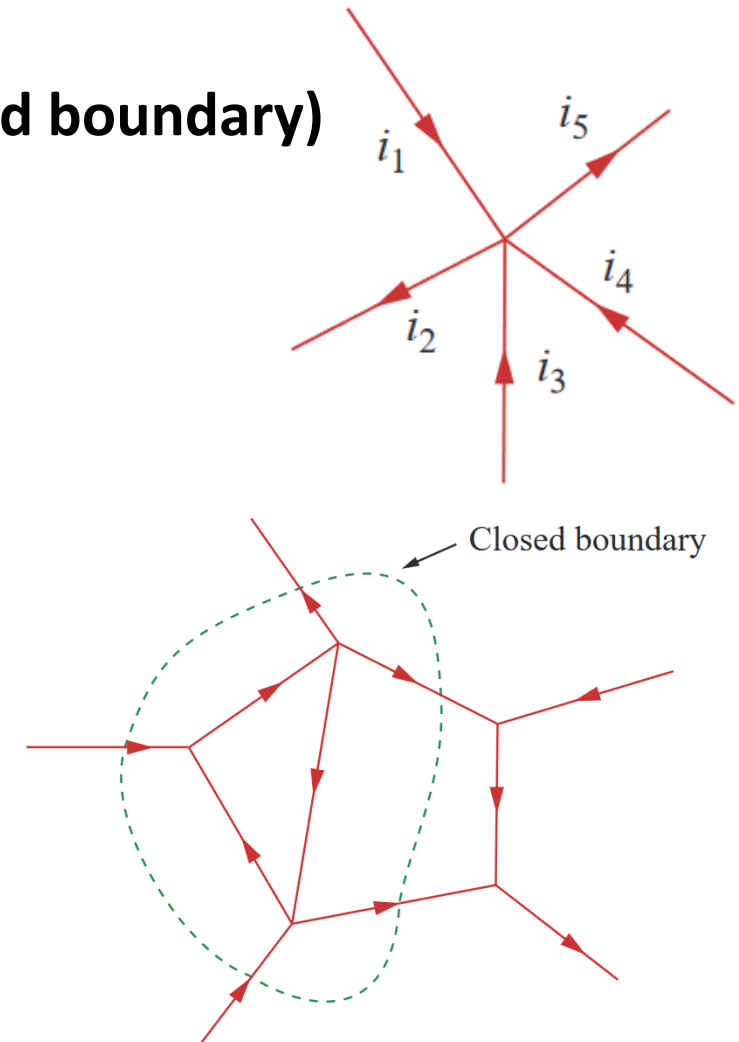

# KCL- Example 1

Find  $v_1, v_2, v_3, i_1, i_2$  and  $i_3$  in the circuit

**Solution:**

KCL in node  $v_a$ . (PS:  $v_a = v_2$ )


$$\frac{5 - v_2}{2} - \frac{v_2 - (-3)}{4} - \frac{v_2 - 0}{8} = 0$$

$$v_2 \left( -\frac{1}{2} - \frac{1}{4} - \frac{1}{8} \right) = -\left( \frac{5}{2} - \frac{3}{4} \right)$$

$$v_2 = \frac{7}{4} \cdot \frac{8}{7} \text{ V} = 2 \text{ V}$$

$$v_1 = 5 - v_2 = 3 \text{ V}$$

$$v_3 = v_2 - (-3) = 5 \text{ V}$$

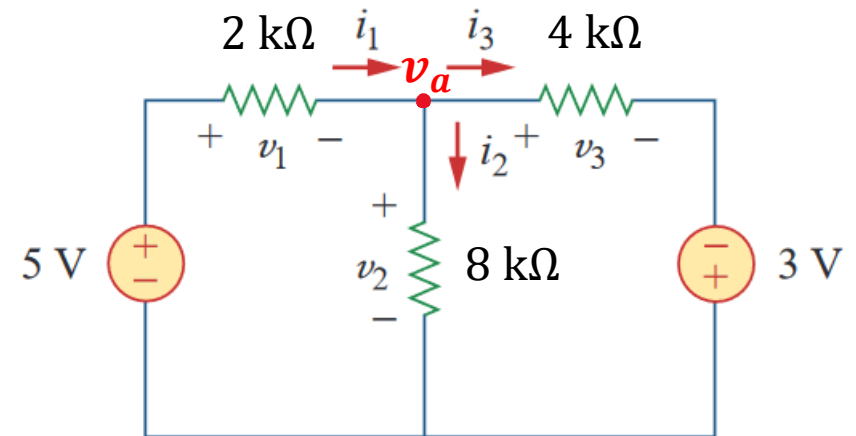


# Series Resistors and Voltage Division

The **equivalent resistance** of any number of resistors connected in **series** is the sum of the individual resistances.

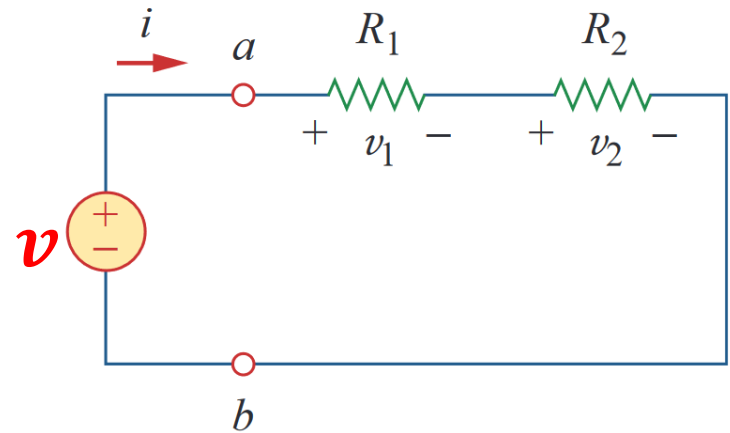
## Principle of voltage division

**Source voltage**  $v$  - is divided among the resistors in direct proportion to their resistances; the larger the resistance, the larger the voltage drop.



$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$



# Line diagram: Example 3

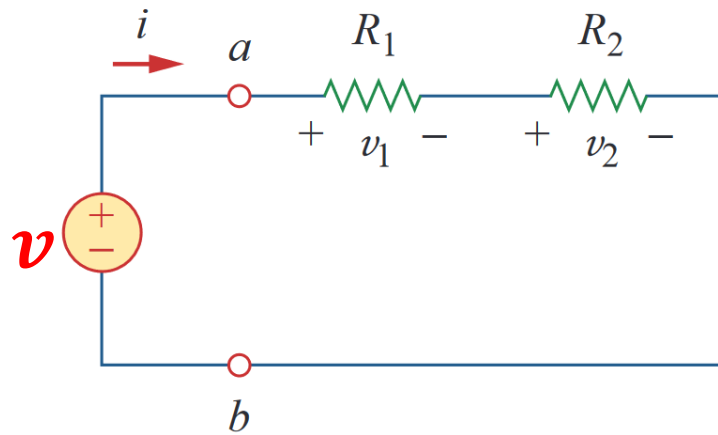

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

A diagram illustrating the voltage divider principle. It shows two resistors,  $R_1$  and  $R_2$ , connected in series. The total voltage  $v$  is applied across the series combination. The voltage  $v_2$  is the voltage across  $R_2$ . The diagram shows  $R_1$  on top and  $R_2$  on bottom, with a ground symbol at the bottom. A bracket on the right indicates the voltage across  $R_1$  is  $\frac{R_1}{R_1 + R_2} v$ .

# Line diagram: Example 3

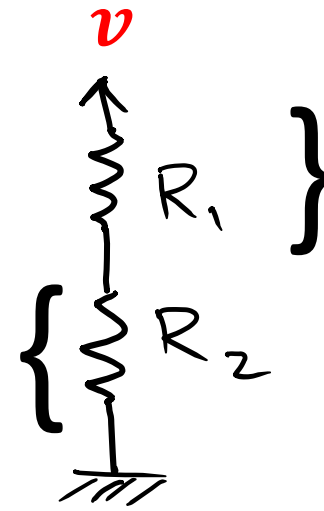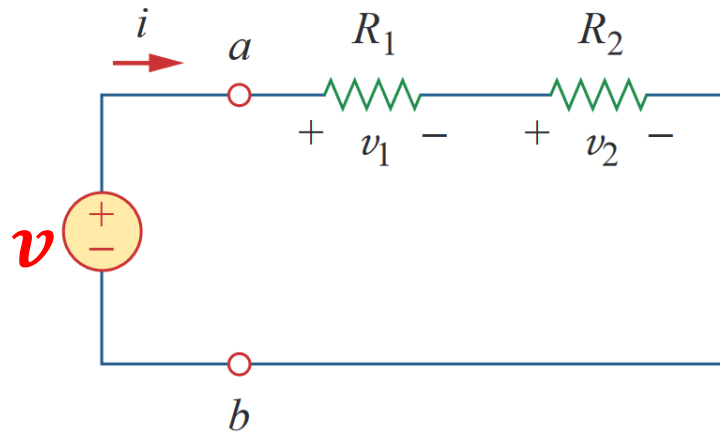

KVL (acts along a line instead of a loop)


$$v - iR_1 - iR_2 = 0$$


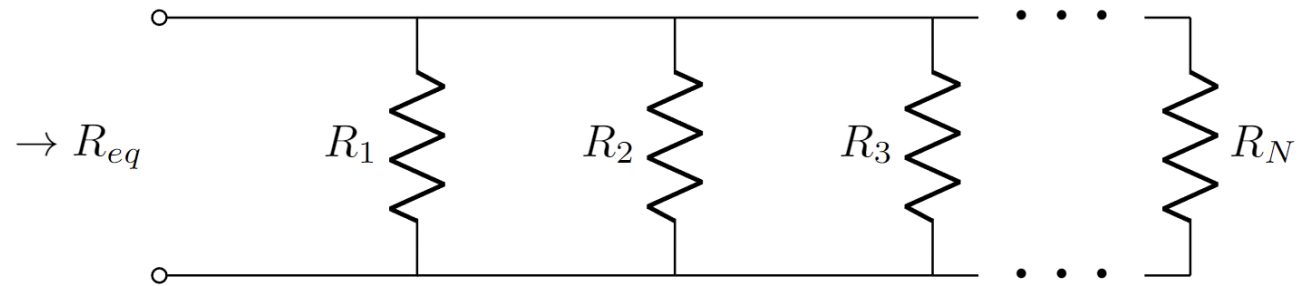
# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots \frac{1}{R_N}$$



Simplification for the case when  $R_1 = R_2 = R_3 \cdots = R_N$

$$R_{eq} = \frac{R_1}{N}$$


# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad R_{eq} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Simplification for the case when  $R_1 = R_2$

$$R_{eq} = \frac{R_1}{2}$$

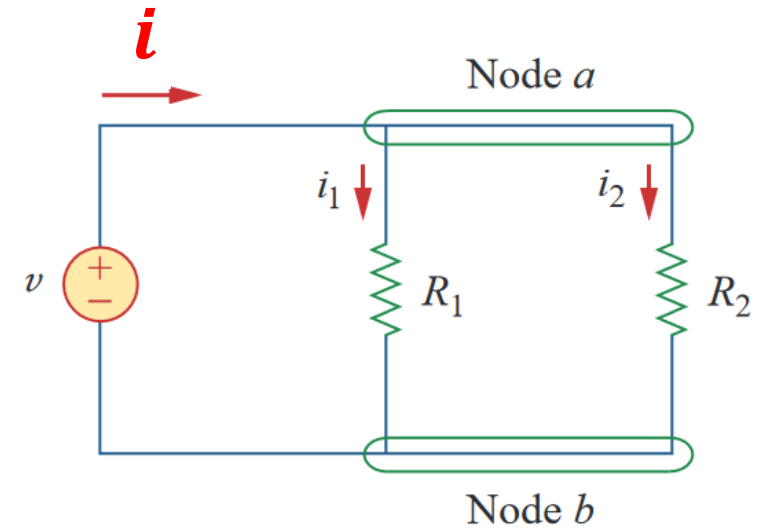


# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.


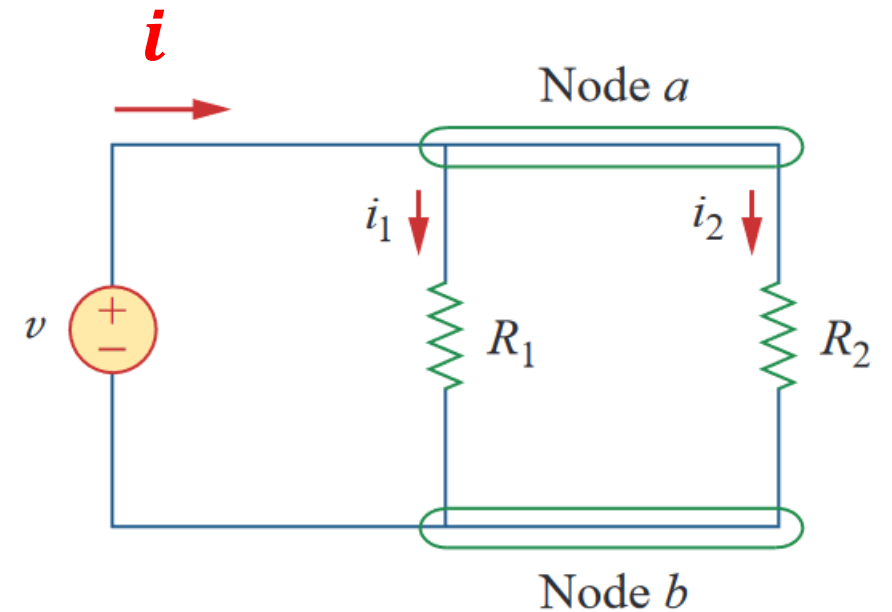
## Principle of current division

**Source current  $i$**  - is divided among the resistors in direct **inverse** proportion to their resistances; the larger the resistance, the larger the voltage drop.

$$i_1 = \frac{1/R_1}{1/R_1 + 1/R_2} i \quad i_2 = \frac{1/R_2}{1/R_1 + 1/R_2} i$$



# Line diagrams: Example 4

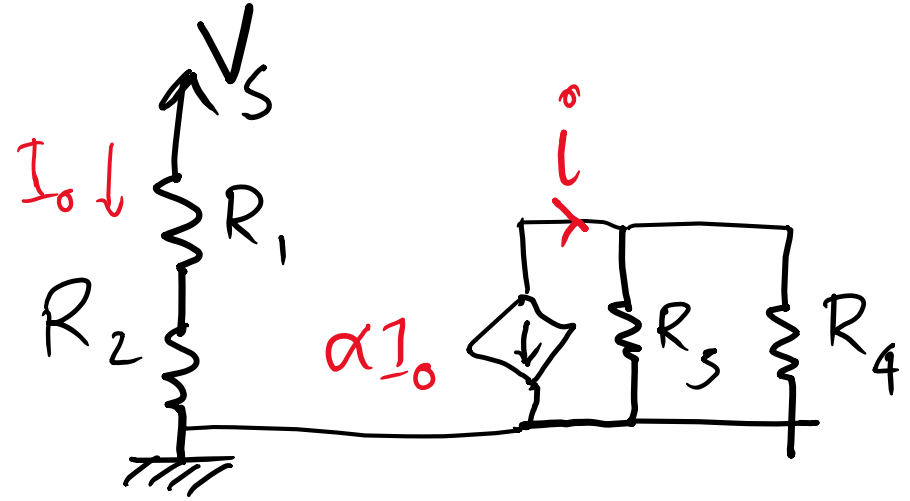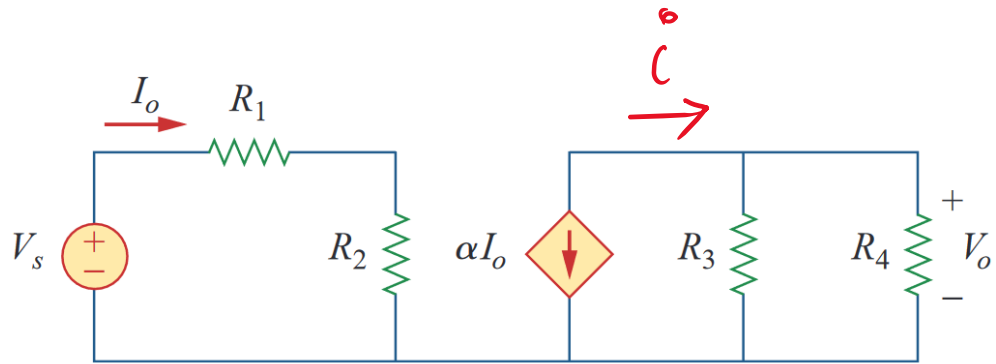

# Practice Problem 1

For the circuit, find  $\left| \frac{V_o}{V_s} \right|$  in terms of  $\alpha$ ,  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .

If  $R_1 = R_2 = R_3 = R_4$  what value of  $\alpha$  will produce  $\left| \frac{V_o}{V_s} \right| = 10$ ?

**Solution:**


Ohm's Law across  $R_1 + R_2$ .

$$I_o = \frac{V_s}{R_1 + R_2}$$

$$i = -\alpha I_o$$



Voltage across **Parallel Resistors**  $R_3, R_4$

$$V_o = i(R_3 || R_4) = -\frac{\alpha V_s}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

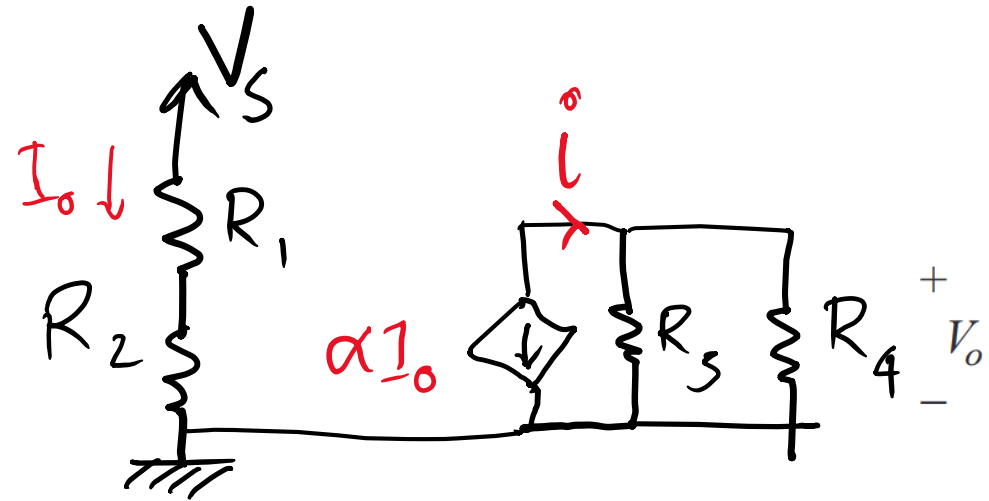


$$\left| \frac{V_o}{V_s} \right| = \frac{\alpha}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

# Example 1- Nodal Analysis

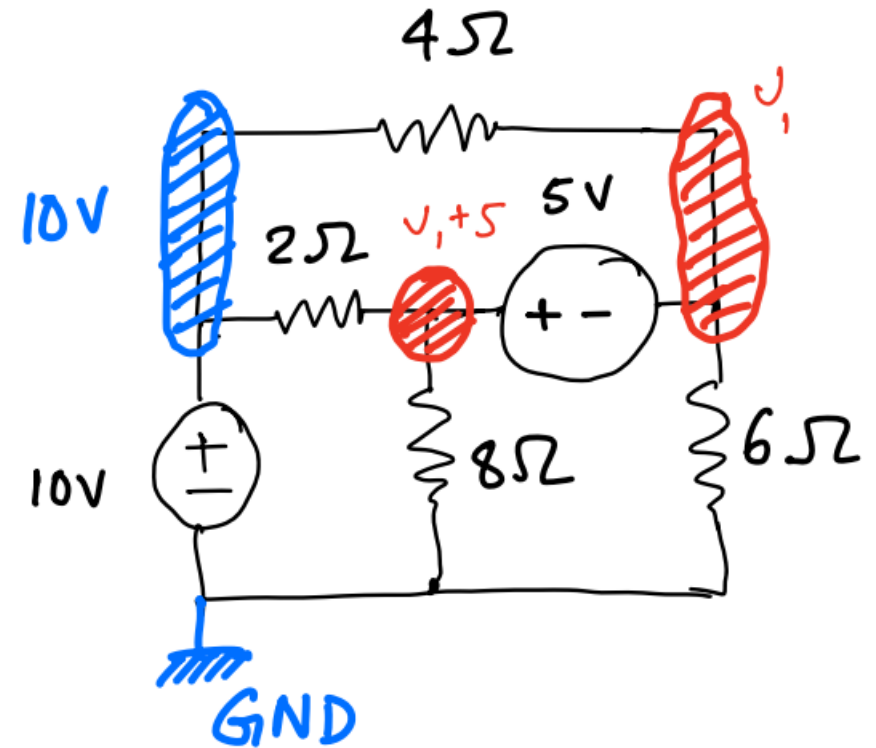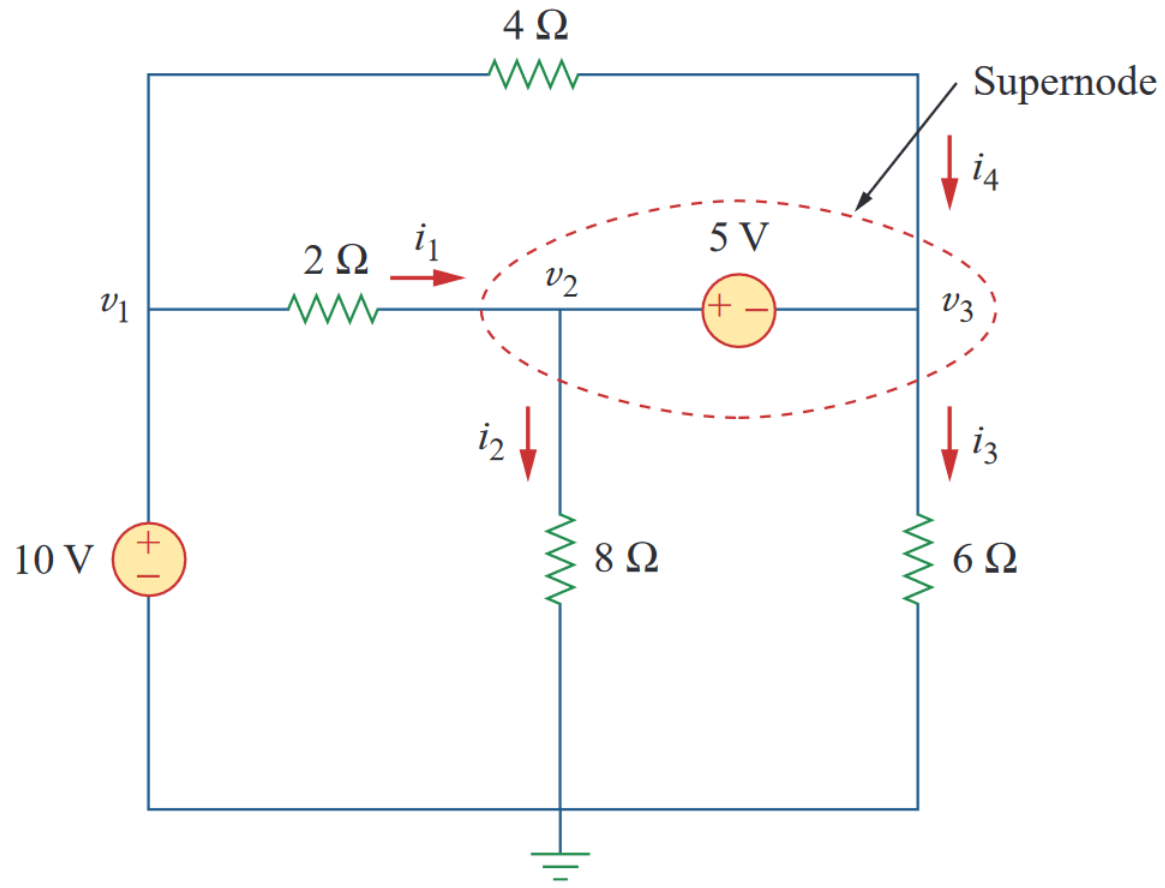

# Example 1- Nodal Analysis

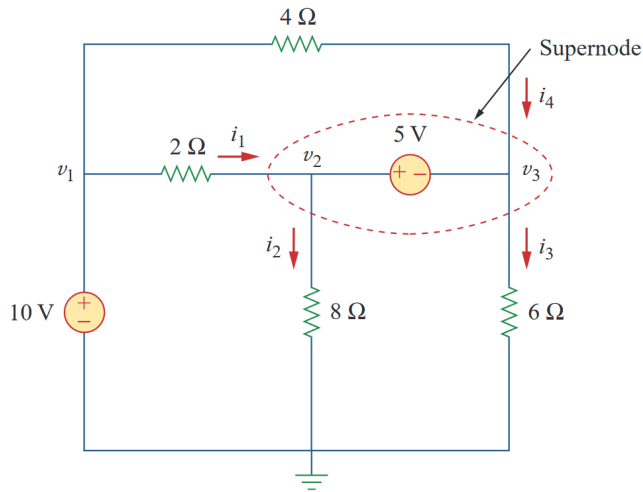


10V Node:  $10 \left( \frac{1}{4} + \frac{1}{2} \right)$


$v_1$  Node:  $v_1 \left( \frac{1}{4} + \frac{1}{6} \right)$  10V

$v_1 + 5$  Node:  $(v_1 + 5) \left( \frac{1}{2} + \frac{1}{6} \right)$  10V
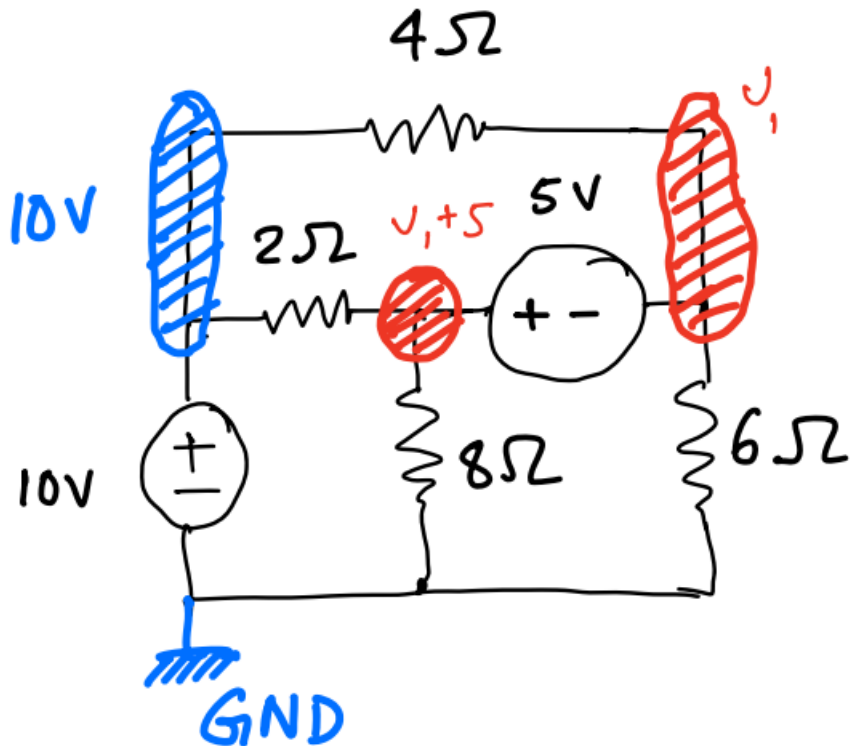
$$v_1 \left( \frac{1}{4} + \frac{1}{6} \right) + (v_1 + 5) \left( \frac{1}{2} + \frac{1}{8} \right) - 10 \left( \frac{1}{2} + \frac{1}{4} \right)$$



# Example 1- Nodal Analysis

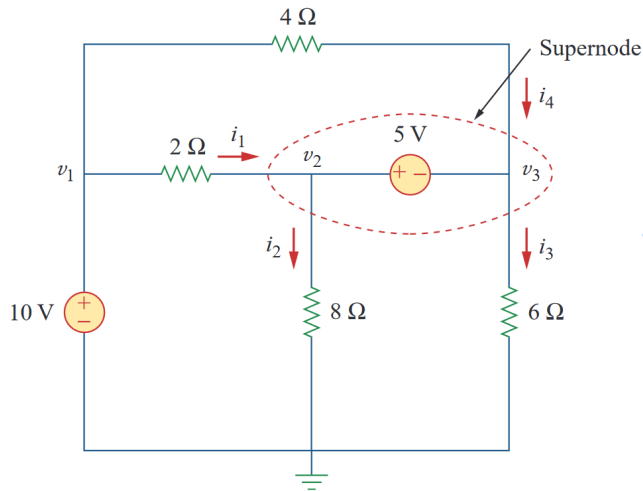


10V Node:  $10 \left( \frac{1}{4} + \frac{1}{2} \right)$

$v_1$  Node:  $v_1 \left( \frac{1}{4} + \frac{1}{6} \right)$


$v_1 + 5$  Node:  $(v_1 + 5) \left( \frac{1}{2} + \frac{1}{8} \right)$
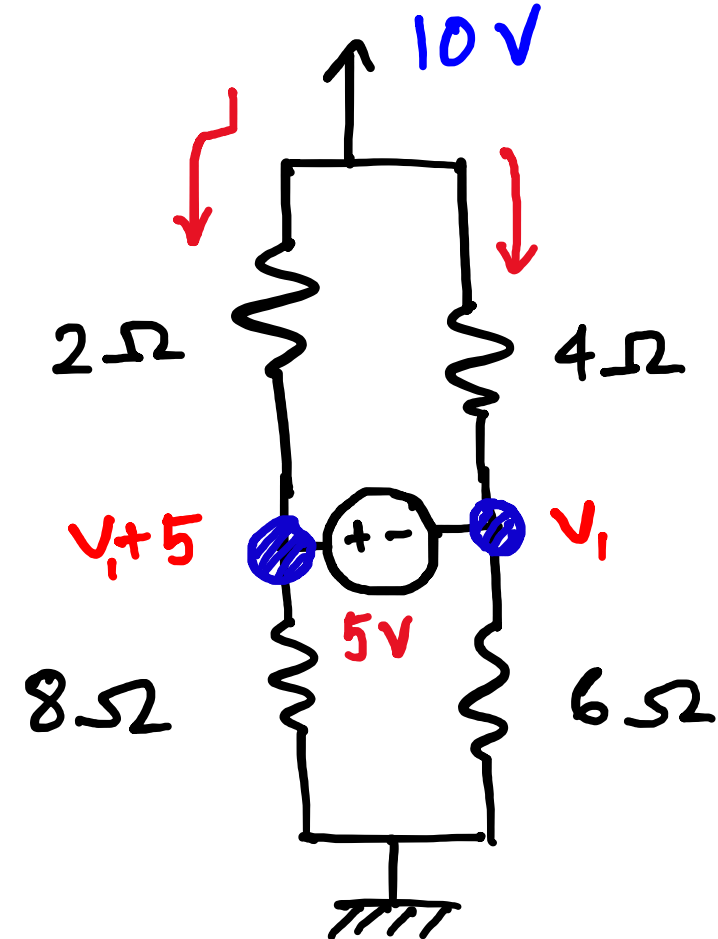
$$v_1 \left( \frac{1}{4} + \frac{1}{6} \right) + (v_1 + 5) \left( \frac{1}{2} + \frac{1}{8} \right) - 10 \left( \frac{1}{2} + \frac{1}{4} \right) = 0$$




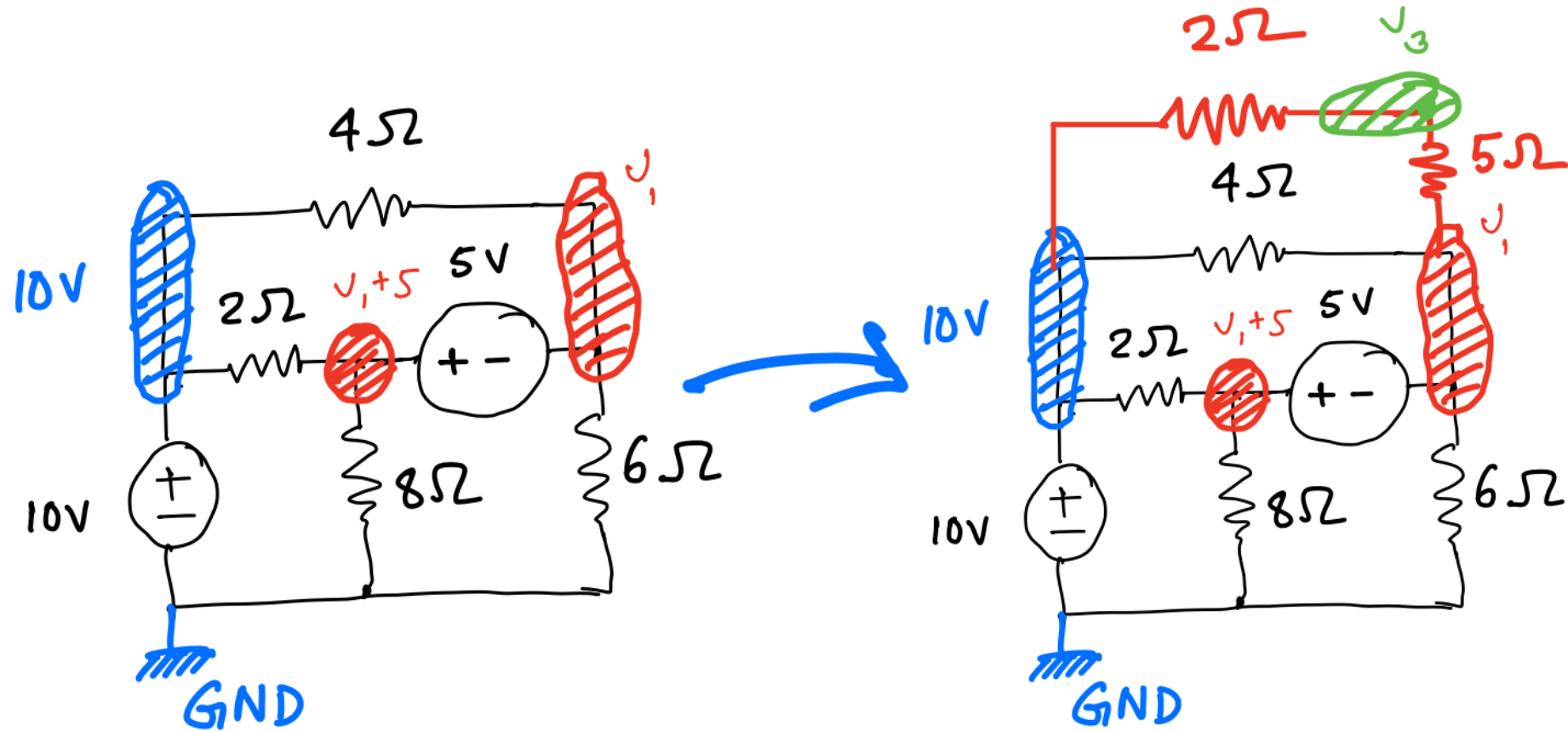
# Example 2- Nodal Analysis – Home Task 1




Find the two node  $v_1$  and  $v_3$  equations!

## Example 3

KCL at node  $v_o$

$$\frac{0.6 - 0.5}{5} = \frac{(0.5 - 0.7) - (-0.5)}{10} + I_1$$

$$I_1 = -0.01 \text{ mA}$$

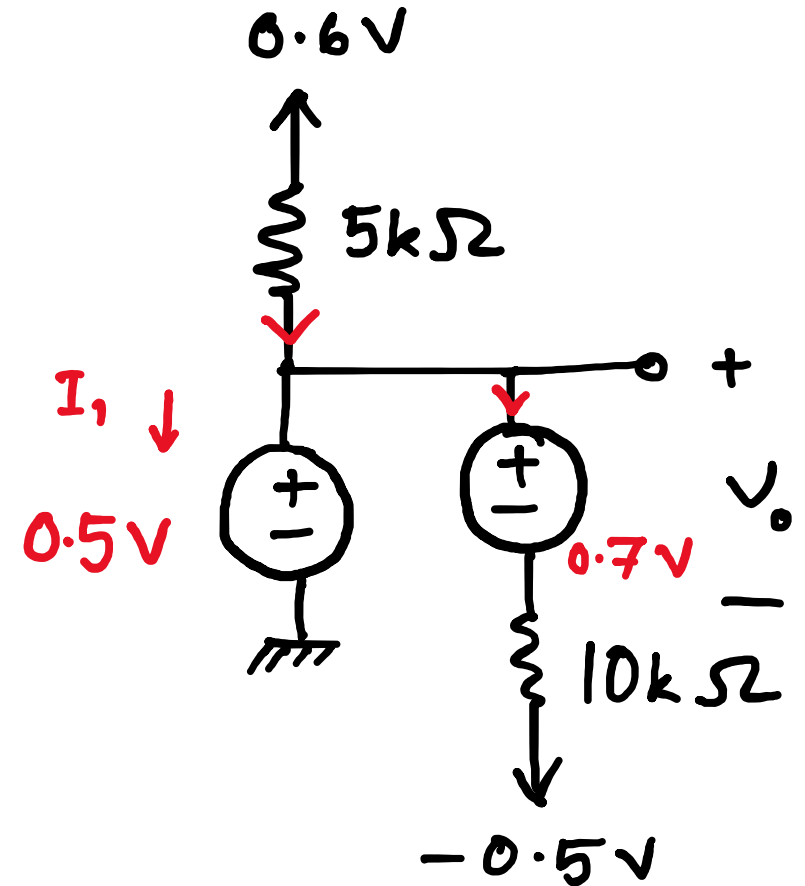


## Example 3

KCL at node  $v_o$

$$\frac{0.6 - 0.5}{5} = \frac{(0.5 - 0.7) - (-0.5)}{10} + I_1$$

$$I_1 = -0.01 \text{ mA}$$

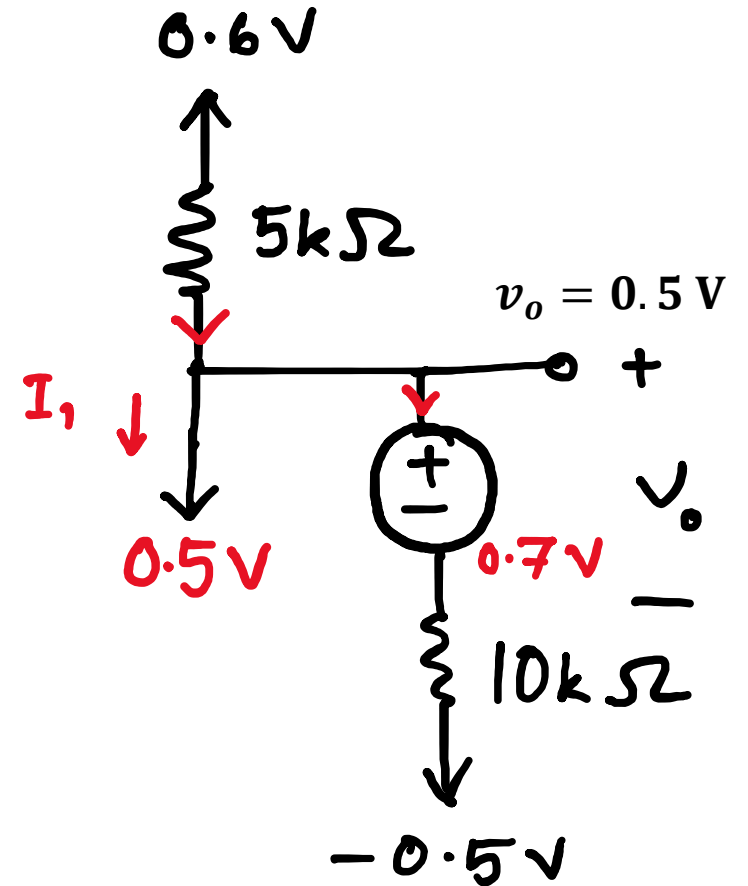

## Example 4

KCL at node  $v_i$


$$\frac{2 - v_i}{1} = \frac{v_i - v_o}{2} + \frac{v_i}{200}$$

$$\frac{301}{200}v_i - \frac{1}{2}v_o = 2$$

KCL at node  $v_o$

$$\frac{v_i - v_o}{2} + \frac{Av_i - v_o}{0.1} = 0$$
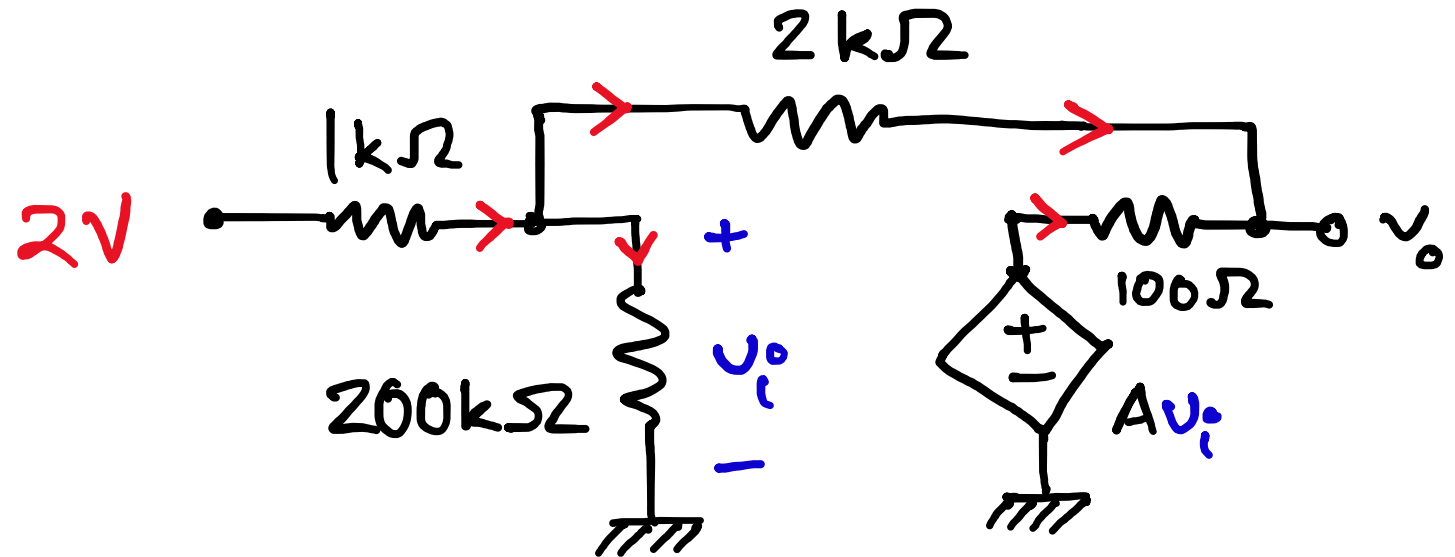
$$(2 \times 10^6 + 0.5)v_i - 10.5v_o = 0$$



$$A = 2 \times 10^5$$

# Example 5

KCL at node  $v_i$


$$\frac{0 - v_i}{5} = \frac{v_i - v_o}{40} + \frac{v_i - 1}{200}$$

$$\frac{23}{100}v_i - \frac{1}{40}v_o = \frac{1}{200}$$

KCL at node  $v_o$

$$\frac{v_i - v_o}{40} + \frac{Av_i - v_o}{0.1} = \frac{v_o}{20}$$
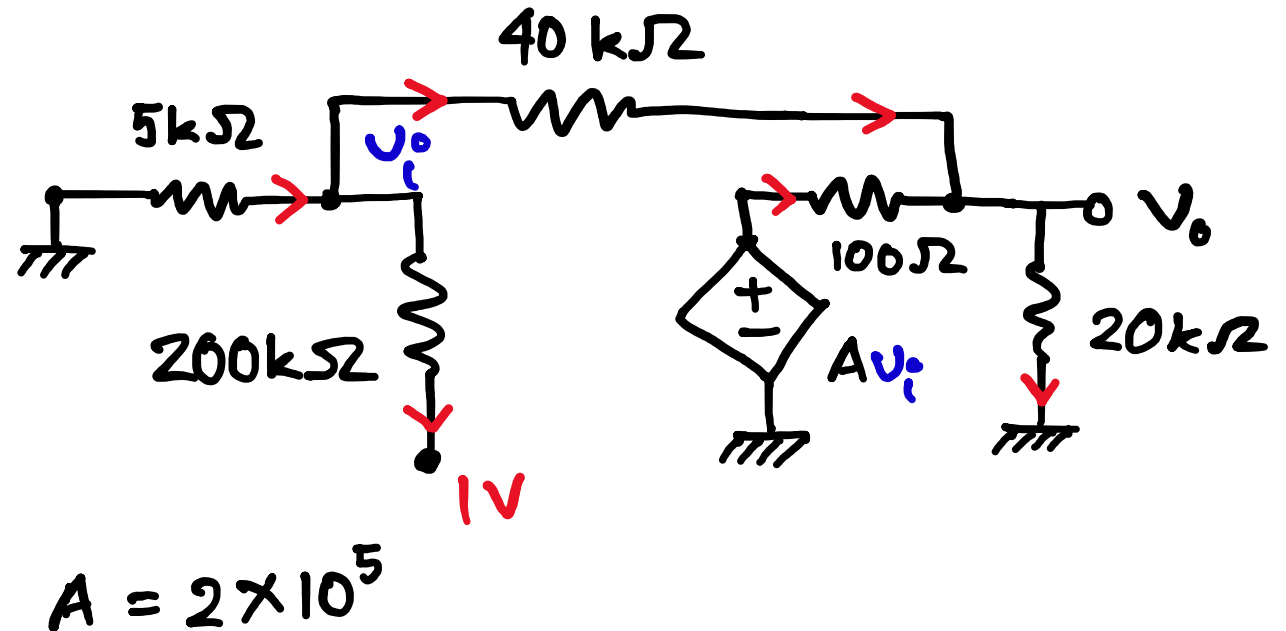
$$(2 \times 10^6 + 0.025)v_i - 10.075v_o = 0$$



# Example 6 – Home Task 2

For  $R = 100\ \Omega$ ,  $R_L = 10\ \text{k}\Omega$ ,  $r_z = 20\ \Omega$ ,  $V_{Z0} = 3\ \text{V}$ , and  $I_Z = 1\ \text{mA}$ .

a. Find  $V_O$

b. Find  $I_L$

c. Find  $I$

d. Find  $V^+$

