

Group No:

Experiment-01

Review of Lab Equipment

CSE251 - Electronic Devices and Circuits Lab

Objective

1. To review the basics of lab equipment for comprehensive understanding

Equipment

1. Breadboard
 2. Digital Multimeter
 3. DC power supply
 4. Oscilloscope
 5. Function Generator
 6. Resistance ($1k\Omega$, $2.2k\Omega$, $2.7k\Omega$)
 7. Chords and Wire
-

Breadboard

A breadboard, also known as a prototyping board, is a device used for building and testing electrical and electronic circuits. It is a reusable platform that allows us to quickly prototype and experiment with different electrical and electronic components without the need for soldering.

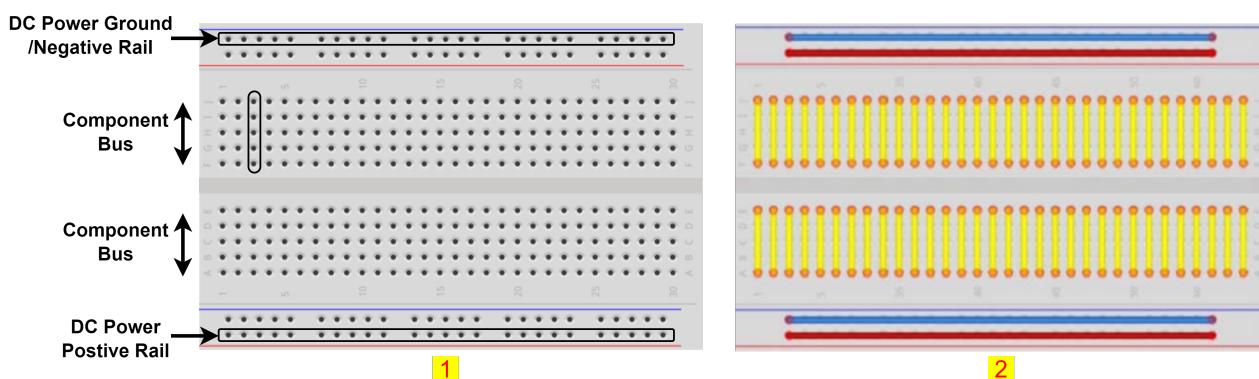


Figure 1: (1) Breadboard (2) Unseen Backside of Breadboard

A typical breadboard consists of a plastic board with a grid of holes and metal clips or sockets that run beneath the holes. The holes are arranged in a pattern that matches the layout of integrated circuits (ICs) and electronic components such as resistors, capacitors, LEDs, and wires. The unseen backside contains interconnections. As a result, component bus is internally short. DC Negative Rail and DC Positive Rail are also internally short.

DC Power Supply

A DC Power Supply is a device that is used to provide a steady and controlled DC voltage to power up a circuit. There are 4 channels in 2 different groups on this device. The display allows us to observe either CH1 or CH3, along with either CH2 or CH4 simultaneously. The buttons on the top-left and top-right corners of the device are used to switch between the channels. Two push buttons are used to operate the two groups in independent, series, or parallel mode (for our lab experiments, we will use them in “independent” mode).

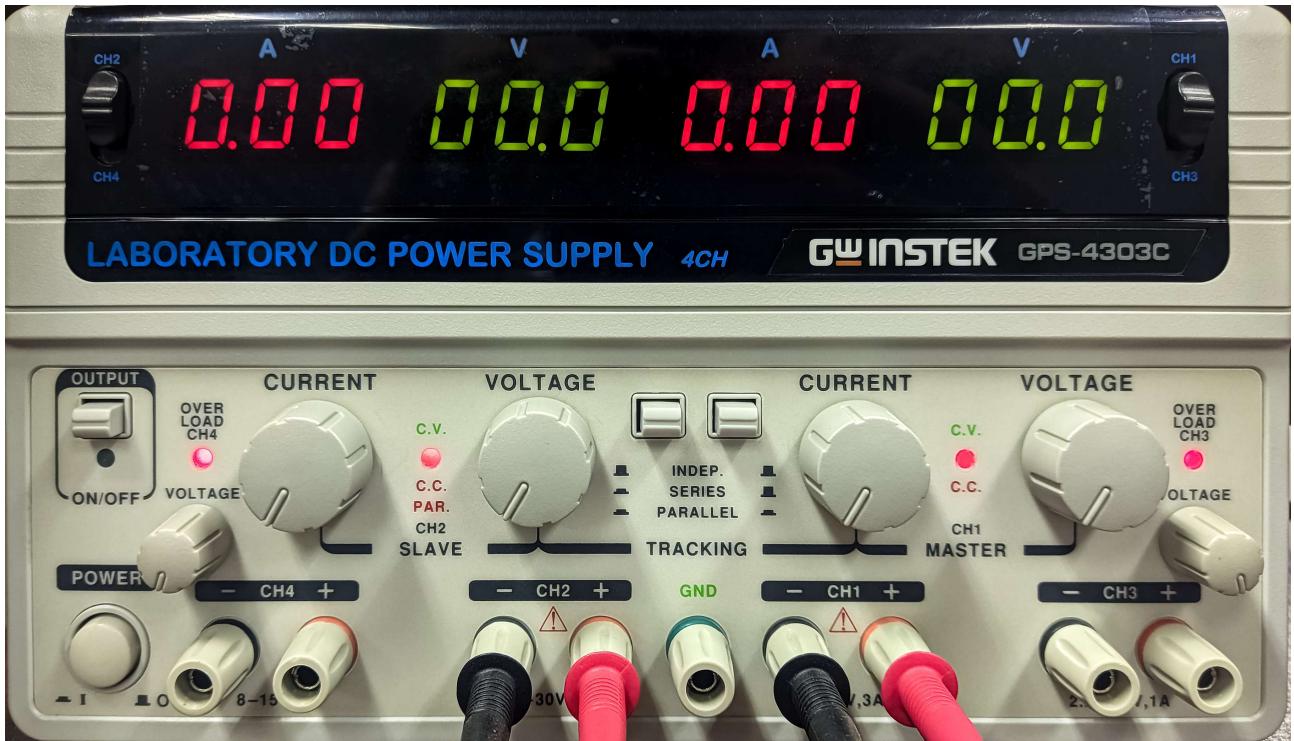


Figure 2: 4-Channel DC Power Supply

To use this device as a voltage source with a desired dc voltage, we need to set the current limit of a channel first. Let's say, we are using CH1. The following steps demonstrate how to use a DC Power Supply:

1. Turn on the device using the power button
2. Check the switches and make sure CH-1 is selected
3. Set the current limit using the current knob (around 0.5 A)
4. Set the desired value of voltage using the voltage knob
5. Once you set the voltage to your desired value push the **Output** button left corner of the knob panel. The power will not be supplied to the external circuit until you push the **Output** button
6. The **red wire** indicates the positive terminal of the power supply and the **black wire** indicates the negative terminal of the power supply

Digital Multimeter

A Digital Multimeter is a versatile electronic instrument used to measure various electrical quantities in circuits. It combines several measurement functions into a single device, making it an essential tool. For example, it can measure - voltage, current, resistance, capacitance etc.

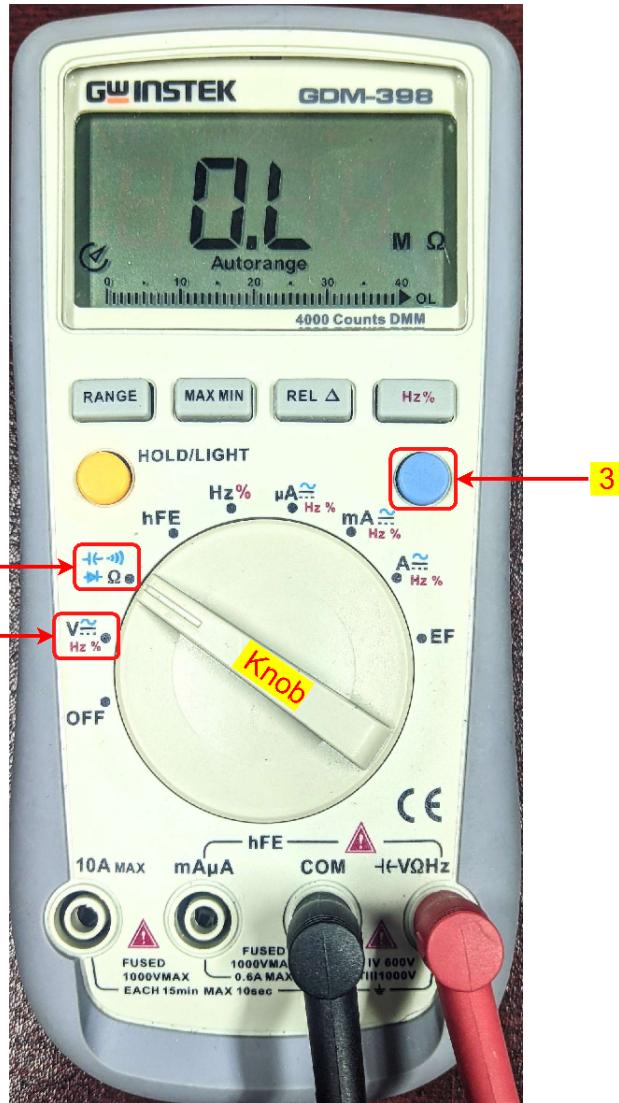


Figure 3: Digital Multimeter

The knob of the multimeter is rotated to change the measuring mode of the device. In position “1”, it can measure voltage. In position “2”, it can measure the resistance, capacitance etc. There is a **Blue Button** indicated by “3” which is used for selecting the required measurement function when there is more than one function at one position of the knob. The red and black wire of the multimeter represents the positive and negative terminal respectively.

For example, voltage can be measured in DC and AC mode. If AC voltage (or current) is to be measured, one must use the multimeter in AC mode. The Blue button on the top-right corner of the multimeter (indicated by “3”) is used to switch between DC and AC mode.

It is very important to check the wires before constructing a circuit. Multimeter can be used to test wires. Following steps can be followed To test wires,

1. Set the knob to position “2” as indicated in the figure above
2. Press the **Blue** button to select the mode
3. If the buzzer sounds continuously, the wire is ok. If the buzzer does not sound continuously, then the wire is damaged and should not be used in the circuit

Oscilloscope

Oscilloscope is a device that enables the visualization and analysis of electrical signals with precision and accuracy. It is a versatile instrument to understand the behavior of circuits.

The primary function of an oscilloscope is to display and measure voltage waveforms over time. It provides a graphical representation of electrical signals in the form of waveforms on a screen, allowing users to observe the amplitude, frequency, phase, and other characteristics of the signal.

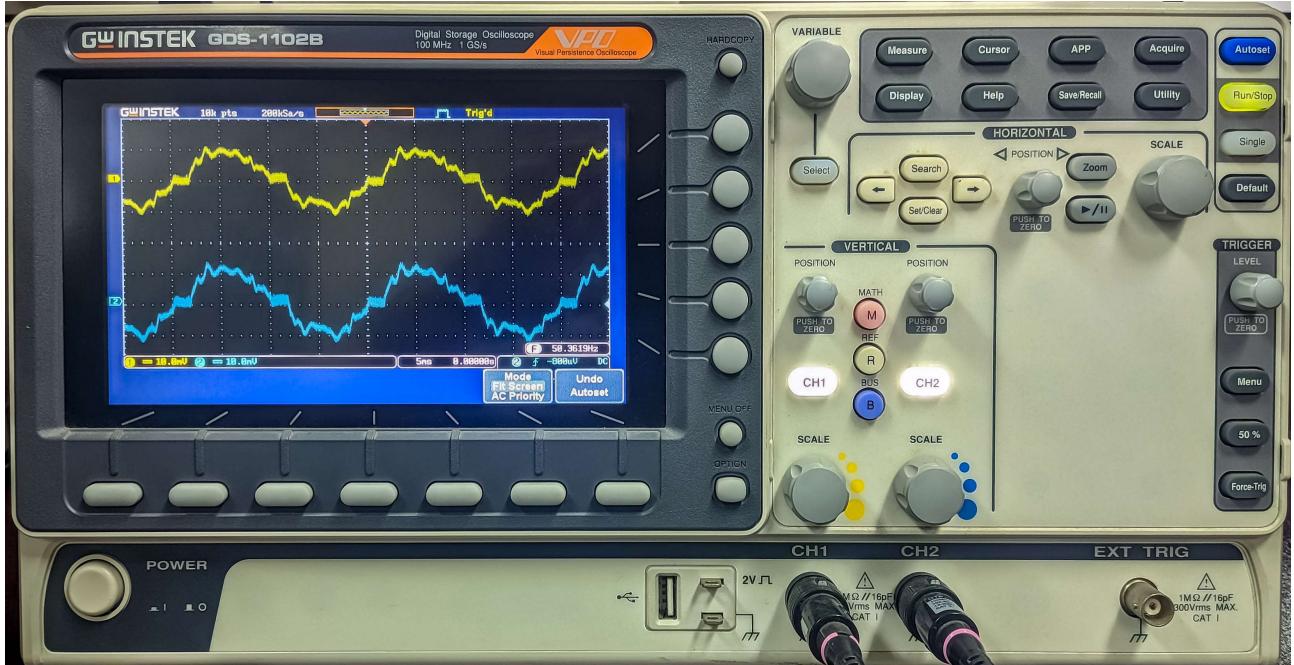


Figure 4: Oscilloscope

There are 2-channels in this oscilloscope that enables us observe 2 voltage waveforms simultaneously. The red and black wire of the probe of a channel represents positive and negative terminal respectively. The negative terminals of the probes are internally shorted. Vertical **Scale** knobs and Horizontal **Scale** knob are used to adjust the scaling of voltage axis and time axis respectively. **Autoset** button is used to automatically scale the waveform(s). The user can also shift the position of the waveforms using the **Position** knobs both in the vertical and horizontal direction. **Measure** button enables the user to measure various quantities from the waveform(s). Oscilloscope also shows the value of voltage/division and time/division. Using these values, we can manually calculate voltage levels and frequency from the waveform(s). Oscilloscope also generates a 2V (p-p) 1 KHz Square Wave to provide a known and standardized test signal for various applications.

Function Generator



Figure 5: Function Generator

A function generator is a versatile instrument that is used to generate various types of electrical waveforms. It produces signals of different frequencies, amplitudes, and wave shapes, such as sine waves, square waves, triangular waves etc. To generate a waveform, one needs to set the frequency to the desired value. This can

be done by rotating the **Frequency** knob. There are also numerical buttons to set the exact frequency of the signal. For example, to generate a signal of 123 MHz / KHz / Hz,

1. Press the buttons 1, 2, 3 one after another. The display will show 123
2. Press **Shift** → Press 8 (for MHz) or, 9 (for KHz) or, 0 (for Hz) → Press the **Output On** button

The **Wave** button can be used to switch between sine, square and triangular waveform. One can also change the amplitude and DC offset of the signal by rotating the **AMPL** and **OFFSET** knob respectively.

Task-01

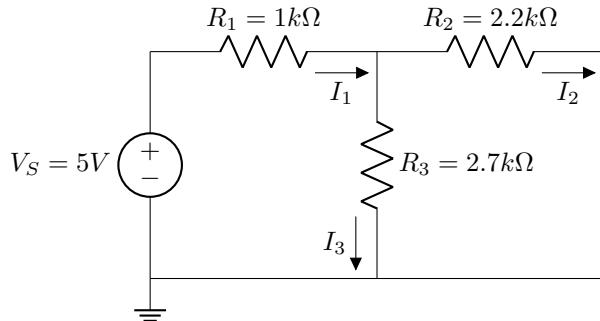


Figure 6: Circuit-1

Procedure

1. Use the DC Power Supply to set $V_S = 5V$ with 0.5A current limit
2. Use the Digital Multimeter to measure the resistances
3. Construct Circuit-1. Now, measure the voltages across the resistances
4. Fill out the table in Data Sheet section to verify KVL and KCL

Task-02

Procedure

1. Construct the same circuit with $V_S = 4V$ (p-p) sine wave. Use Function Generator and Oscilloscope instead of DC Power Supply for this part. Set the frequency of V_S to,
 $f = \text{Last 3-digit of the student ID of any group member}$
2. Connect the CH1/CH2 of the oscilloscope across R_1 . Observe the waveform and capture it using a camera.
Do the same for R_2 .

Task-03: Report

1. Cover page [include course code, course title, name, student ID, group, semester, date of performance, date of submission]
2. Attach the signed Data Sheet
3. Attach the captured images
4. Answer the questions in the “Test Your Understanding” section
5. Add a brief Discussion at the end of the report

Data Sheet

Table for Task-01

R_1	R_2	R_3	V_{R_1}	$V_{R_2} = V_{R_3}$	$I_1 = \frac{V_{R_1}}{R_1}$	$I_2 = \frac{V_{R_2}}{R_2}$	$I_3 = \frac{V_{R_3}}{R_3}$	$V_{R_1} + V_{R_2}$	$I_2 + I_3$

Test Your Understanding

1. For circuit-1, which one is the correct way to connect the 2 channels (CH1 and CH2) of the oscilloscope to observe the voltages V_{R_1} and V_{R_2} ? Justify your answer

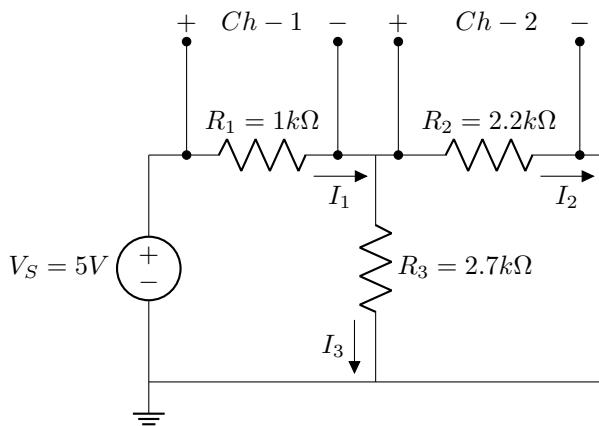


Figure 7: Option-A


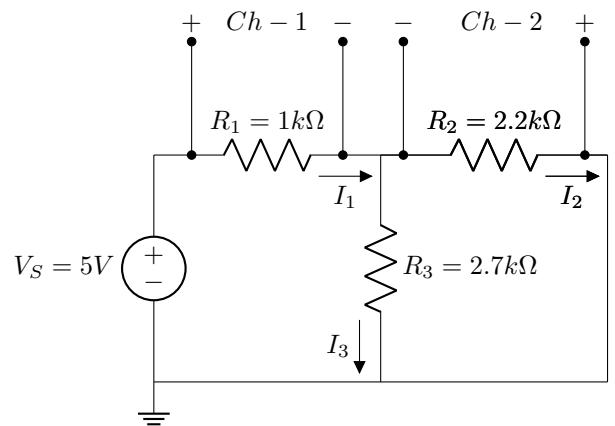


Figure 8: Option-B

Answer:

2. For the following circuit, draw the waveform that should be observed in CH1.

Answer:

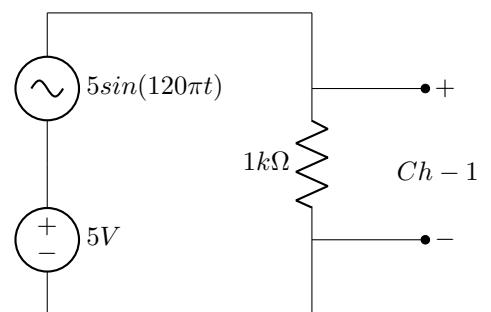

3. We used Ohm's law to measure the current in the circuit instead of using the multimeter as an ammeter. What is the advantage of this method?

Answer: